

1) Consider the circuit shown in Figure 1 below.

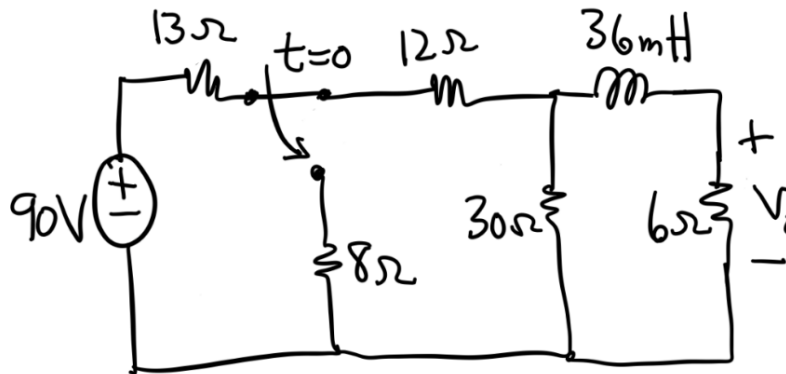


Figure 1. Circuit for Problem 1.

a) The response  $V_o(t)$  for  $t > 0$  can be written as

$$V_o(t) = A + Be^{-ct},$$

where  $A$  and  $B$  are in units of volts and  $c$  has units of rps (i.e., rad/sec;  $c$  is the reciprocal of the time constant). State your by-hand solutions for  $A$ ,  $B$ , and  $c$ , and **list your  $A$ ,  $B$ , and  $c$  values with appropriate units in proper engineering notation format with two decimal places of precision.**

Also, sketch the response. Label the plot axes on your sketch and otherwise make your sketch neat-looking and easy to comprehend.

b) Use the LTSpice verification testbench which has been provided to you to verify your by-hand answers for  $A$ ,  $B$ , and  $c$ . **List the *maxerror* value you attained from the LTSpice verification testbench;** you should ensure that the *maxerror* value listed in the Spice Error Log (ctrl-L) is less than or equal to the value given in the testbench comment. If you do not achieve a *maxerror* less than or equal to the value given in the testbench comment, **something is wrong**, and you should work to resolve the issues with your by-hand solutions for  $A$ ,  $B$ , and  $c$  prior to submitting. Attach a screenshot of the Spice Error Log showing the value of *maxerror* that you attained.

[continued on next page]

2) Consider the circuit shown in Figure 2 below.

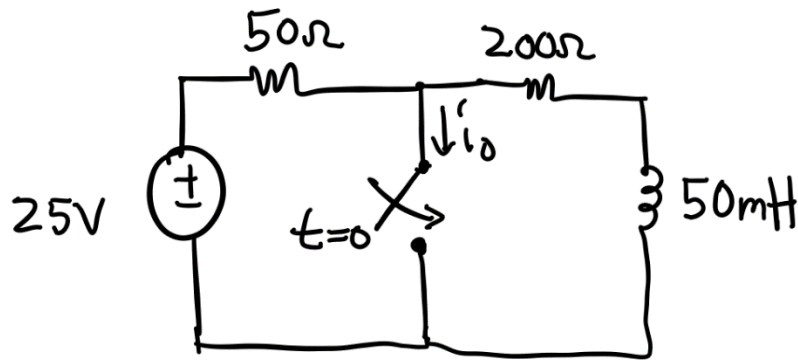


Figure 2. Circuit for Problem 2.

a) The response  $i_0(t)$  for  $t > 0$  can be written as

$$i_0(t) = A + Be^{-ct},$$

where  $A$  and  $B$  are in units of amps and  $c$  has units of rps (i.e., rad/sec;  $c$  is the reciprocal of the time constant). State your by-hand solutions for  $A$ ,  $B$ , and  $c$ , and **list your  $A$ ,  $B$ , and  $c$  values with appropriate units in proper engineering notation format with two decimal places of precision.**

Also, sketch the response. Label the plot axes on your sketch and otherwise make your sketch neat-looking and easy to comprehend.

b) Use the LTSpice verification testbench which has been provided to you to verify your by-hand answers for  $A$ ,  $B$ , and  $c$ . **List the *maxerror* value you attained from the LTSpice verification testbench;** you should ensure that the *maxerror* value listed in the Spice Error Log (ctrl-L) is less than or equal to the value given in the testbench comment. If you do not achieve a *maxerror* less than or equal to the value given in the testbench comment, **something is wrong**, and you should work to resolve the issues with your by-hand solutions for  $A$ ,  $B$ , and  $c$  prior to submitting. Attach a screenshot of the Spice Error Log showing the value of *maxerror* that you attained.

[continued on next page]

3) Consider the circuit shown in Figure 3 below.

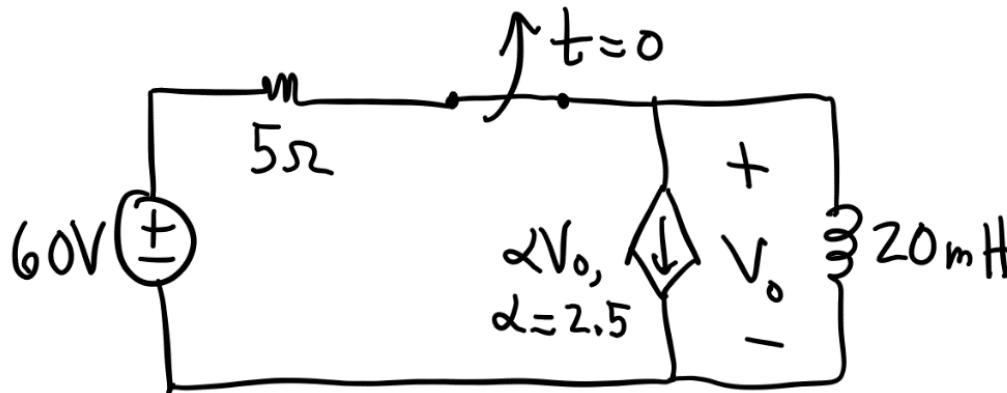


Figure 3. Circuit for Problem 3.

a) The response  $V_o(t)$  for  $t > 0$  can be written as

$$V_o(t) = A + Be^{-ct},$$

where  $A$  and  $B$  are in units of volts and  $c$  has units of rps (i.e., rad/sec;  $c$  is the reciprocal of the time constant). State your by-hand solutions for  $A$ ,  $B$ , and  $c$ , and **list your  $A$ ,  $B$ , and  $c$  values with appropriate units in proper engineering notation format with two decimal places of precision.**

Also, sketch the response. Label the plot axes on your sketch and otherwise make your sketch neat-looking and easy to comprehend.

b) Use the LTSpice verification testbench which has been provided to you to verify your by-hand answers for  $A$ ,  $B$ , and  $c$ . **List the *maxerror* value you attained from the LTSpice verification testbench;** you should ensure that the *maxerror* value listed in the Spice Error Log (ctrl-L) is less than or equal to the value given in the testbench comment. If you do not achieve a *maxerror* less than or equal to the value given in the testbench comment, **something is wrong**, and you should work to resolve the issues with your by-hand solutions for  $A$ ,  $B$ , and  $c$  prior to submitting. Attach a screenshot of the Spice Error Log showing the value of *maxerror* that you attained.

[continued on next page]

4) Consider the circuit shown in Figure 4 below.

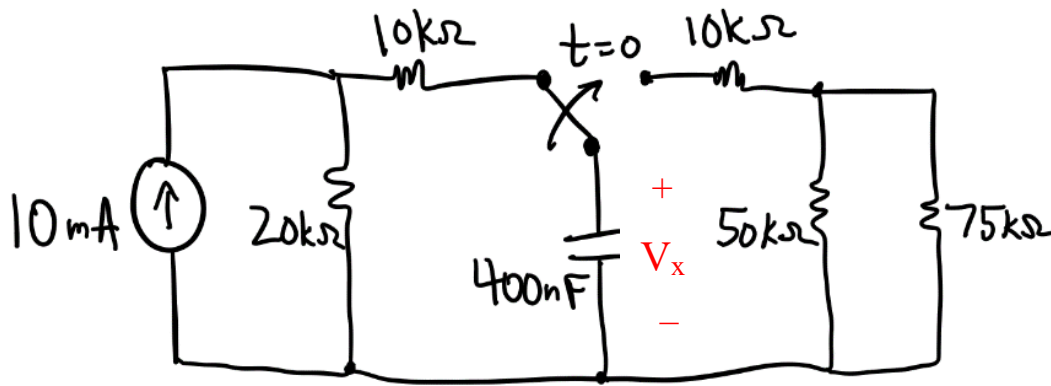


Figure 4. Circuit for Problem 4.

a) The response  $V_x(t)$  for  $t \geq 0$  can be written as

$$V_x(t) = A + Be^{-ct},$$

where  $A$  and  $B$  are in units of volts and  $c$  has units of rps (i.e., rad/sec;  $c$  is the reciprocal of the time constant). State your by-hand solutions for  $A$ ,  $B$ , and  $c$ , and **list your  $A$ ,  $B$ , and  $c$  values with appropriate units in proper engineering notation format with two decimal places of precision.**

Also, sketch the response. Label the plot axes on your sketch and otherwise make your sketch neat-looking and easy to comprehend.

b) Use the LTSpice verification testbench which has been provided to you to verify your by-hand answers for  $A$ ,  $B$ , and  $c$ . **List the *maxerror* value you attained from the LTSpice verification testbench;** you should ensure that the *maxerror* value listed in the Spice Error Log (ctrl-L) is less than or equal to the value given in the testbench comment. If you do not achieve a *maxerror* less than or equal to the value given in the testbench comment, **something is wrong**, and you should work to resolve the issues with your by-hand solutions for  $A$ ,  $B$ , and  $c$  prior to submitting. Attach a screenshot of the Spice Error Log showing the value of *maxerror* that you attained.