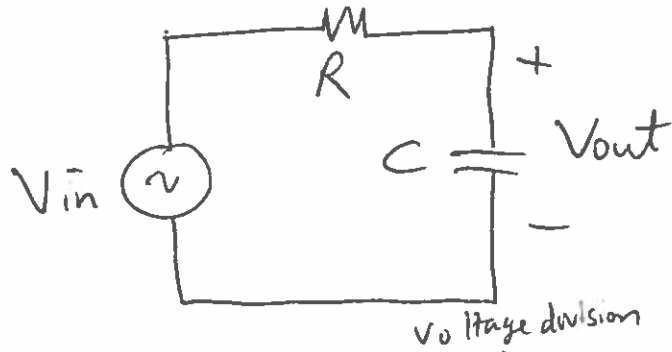


Additional Bode Plot Approximation Example

Sketch the Bode plot approximation (magnitude & phase) of the following circuit, where $H(s) = V_{out}(s)/V_{in}(s)$:



Use voltage division to find $H = V_{out}/V_{in}$; also, recall that $s = j\omega$

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{\frac{1}{sC}}{R + \frac{1}{sC}} = \frac{1}{1 + sRC} = \frac{1}{1 + s/\omega_p}$$

to cancel the $1/sC$ terms

Bode approximation form, where $\omega_p = \frac{1}{RC}$

→ Looking at H , we see that all we have is a pole at $\omega_p = \frac{1}{RC}$, so:

