

# Example

Determine Theremin & Norton ckt models wrt nodes  $\alpha$  &  $\beta$ .

Start w/ Theremin model  $\rightarrow V_{TH}$  open ckt voltage,  $V_{oc}$   
 $\rightarrow R_{TH}$

$$V_{\alpha} - R_3 I_s = 0V \quad (= R_2 i_2 = 0)$$

$$V_{\alpha} = R_3 I_s \quad V_{oc} = V_{\alpha} - V_{\beta} = R_3 I_s$$

$$V_{TH} \stackrel{sd}{=} V_{oc} = R_3 I_s = 72V$$

Now, solve for  $V_{oc} (= V_{TH})$  via mesh analysis:

Mesh count = 2;  $\times$  eqns, at most



KVL, mesh 2

$$-R_1(i_1 - i_2) + R_2(i_2 - i_1) = 0$$

$$\Rightarrow -R_1 I_s + R_1 i_2 + R_2 i_2 - R_2 I_s = 0$$

$$\Rightarrow i_2 [R_1 + R_2] = [R_1 + R_2] I_s \Rightarrow i_2 = I_s$$

ckt is solved

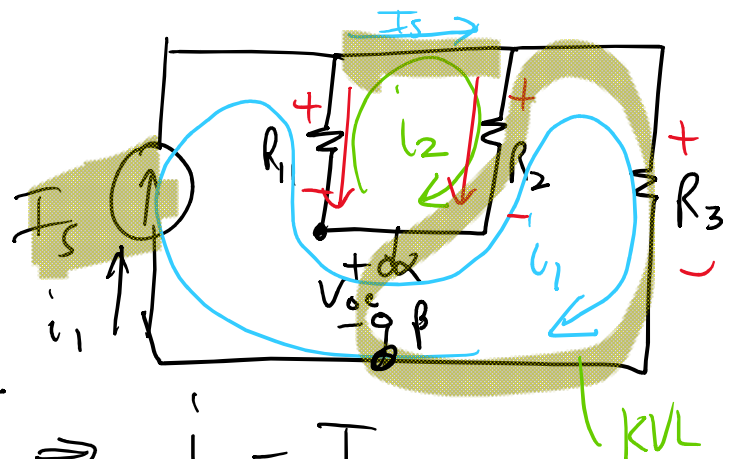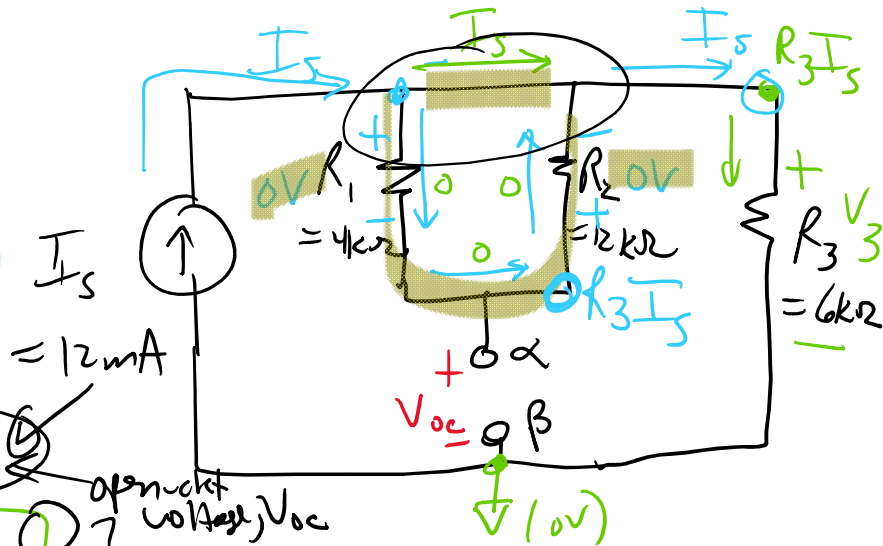





$$2 \cancel{L1} \cancel{R2} \approx \cancel{L1} \cancel{R2} \perp_s \Rightarrow \cancel{V_2} = \perp_s \quad \checkmark \text{ ckt is solved}$$

Now, solve for  $V_{oc}$ :  $-V_{oc} - \underbrace{R_2(i_2 - i_1)}_{=0} + R_3 \overset{0V}{\cancel{i_1}} = 0 \Rightarrow V_{oc} = R_3 I_s$

$$R_{TH} = R_{out}?$$

$$\Rightarrow \underline{V_{TH}^{set} = V_{oc} = 72V}$$

→ Deactivated ckt:

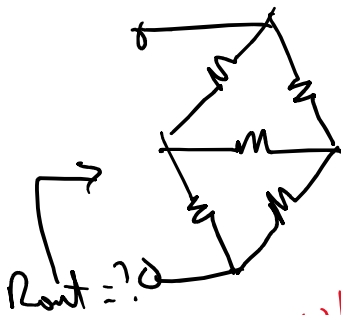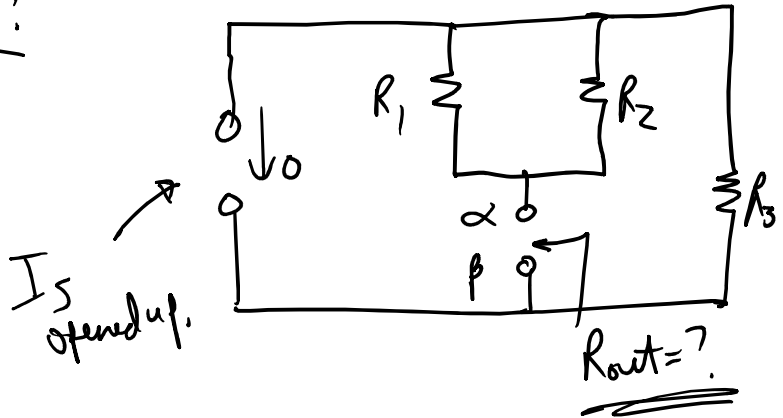
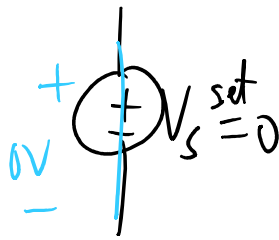
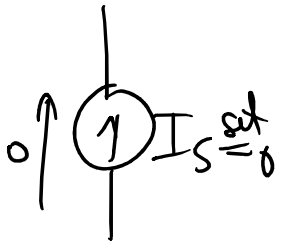


→ I'm going to combine  $R_s$  in series/parallel to get  $R_{out}$ . Why? I see no dep. sources, & no "wheatstone bridges"

*I will choose this one ("easier")*


\* → But we could attach a test source

$$R_{out} = V_T / I_T$$

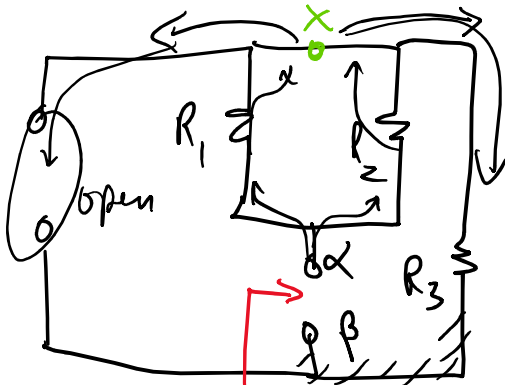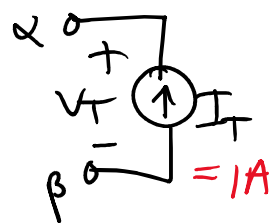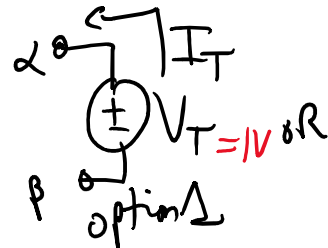

$R_{out}$

$$R_1 // R_2 + R_3$$

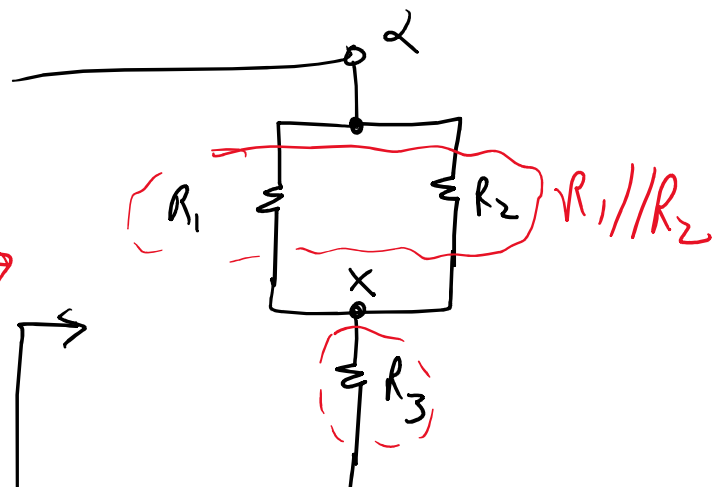

$$R_1 // R_2 + R_3$$



$$R_{out} = R_1 // R_2 + R_3$$

$$= \boxed{4k // 12k} + 6k = \frac{(4k)(12k)}{4k + 12k} + 6k = \frac{12k}{4} + 6k = 9k\Omega$$


$\frac{12k}{3} = 4k$   
 3 12k in parallel  
 4 12k in parallel

$$\Rightarrow R_{TH} \stackrel{\text{set}}{=} R_{out} = 9k\Omega$$


Thvenin model

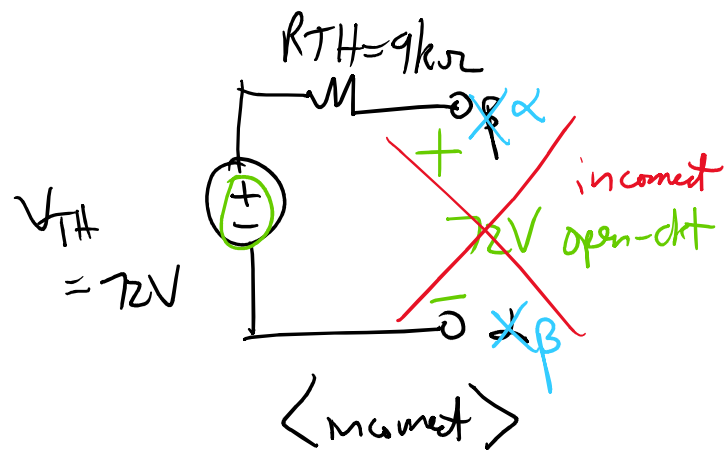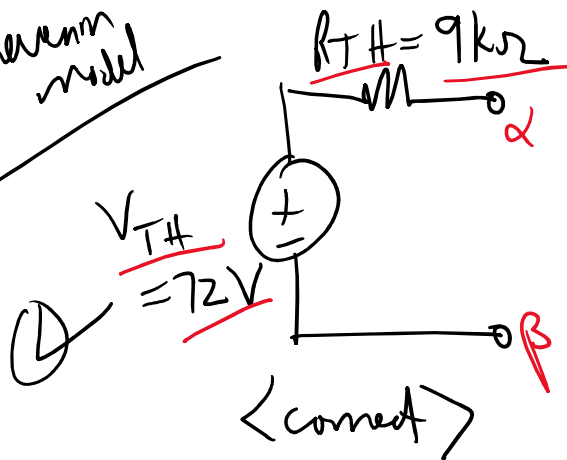

Norton model

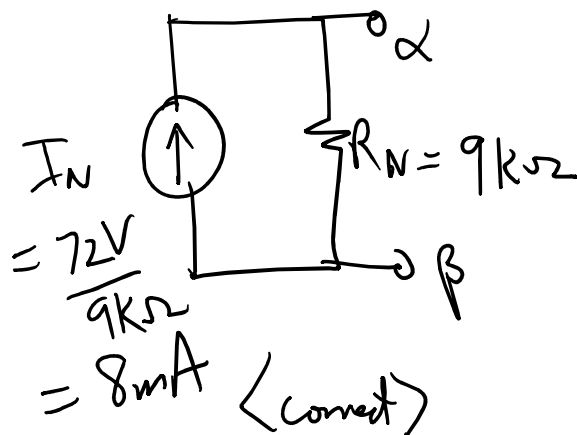


$$I_N = V_{TH} / R_{TH}, R_N = R_{TH}$$

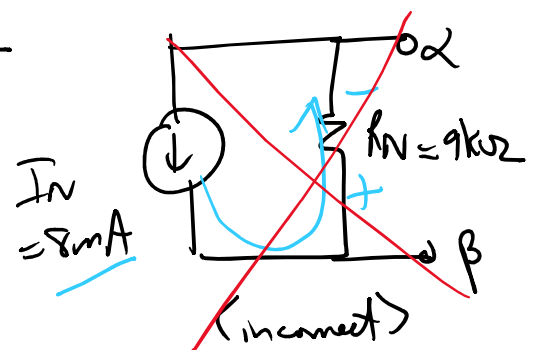

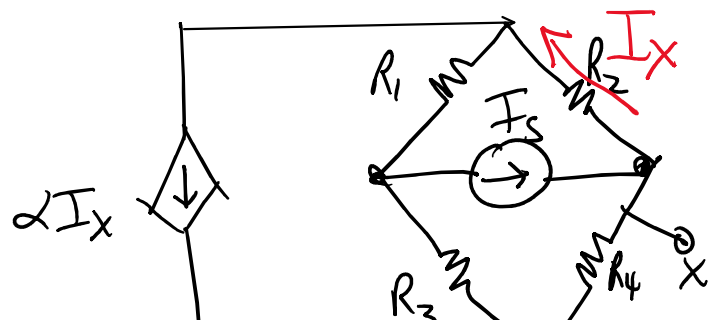
Example

Here,  $R_1 = 2\Omega$ ,  $R_2 = 1\Omega$ ,  
 $R_3 = 2\Omega$ ,  $R_4 = 2\Omega$ ,  $I_S = 3A$ ,



$$R_3 = 2\Omega, R_4 = 2\Omega, I_s = 3A,$$

$$\alpha = 4A/A$$

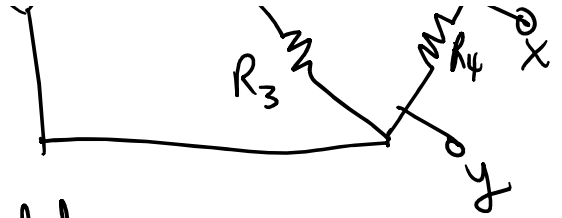

Compute the Thevenin & Norton models  
wrt nodes  $x$  &  $y$ :