

- 1) Consider the circuit shown in Figure 1 below, constructed with an ideal opamp. (NOTE: Verification of your answers with LTSpice, Matlab, etc. is not required for this assignment.)

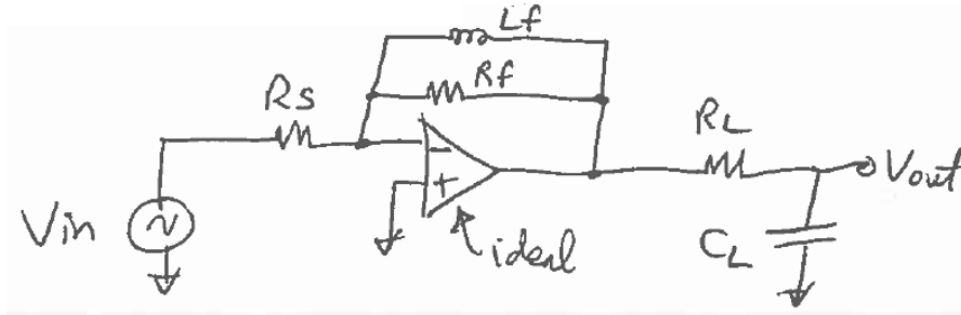


Figure 1. Circuit for Problem 1.

- a) The transfer function from input to output for the above circuit in proper Bode approximation form can be shown to be

$$H(s) = \frac{V_{\text{out}}(s)}{V_{\text{in}}(s)} = \frac{-(s / \omega_{\text{ZDC}})}{(1 + s / \omega_{p1})(1 + s / \omega_{p2})}.$$

Derive analytic expressions for the key angular frequencies ω_{ZDC} , ω_{p1} , and ω_{p2} in terms of the passive components R_s , L_f , R_f , R_L , and/or C_L . **Box your three expressions so they are easy for me to find. Show your work. DO NOT** use the numerical components values given in part (d) for this part!

- b) What is the frequency response magnitude $|V_{\text{out}}/V_{\text{in}}|$ at DC, i.e., at $\omega = 0$? **Box your numerical result so that it is easy for me to find. DO NOT** use the numerical components values given in part (d) for this part!
- c) What is the frequency response magnitude $|V_{\text{out}}/V_{\text{in}}|$ at very high frequencies, i.e., as $\omega \rightarrow \infty$? **Box your numerical result so that it is easy for me to find. DO NOT** use the numerical components values given in part (d) for this part!

[continued on next page]

- d) Now, for this part, let the passive component values be as follows:
 $R_s = 100 \, \Omega$, $R_f = 1 \, \text{k}\Omega$, $R_L = 1 \, \text{k}\Omega$, $L_f = 15.92 \, \text{mH}$, $C_L = 1.59 \, \text{nF}$ (**but, again, do not use these numbers for the above parts!**).

The Bode plot approximation sketch of the circuit of Figure 1 with the above numerical values is shown in Figure 2 below.

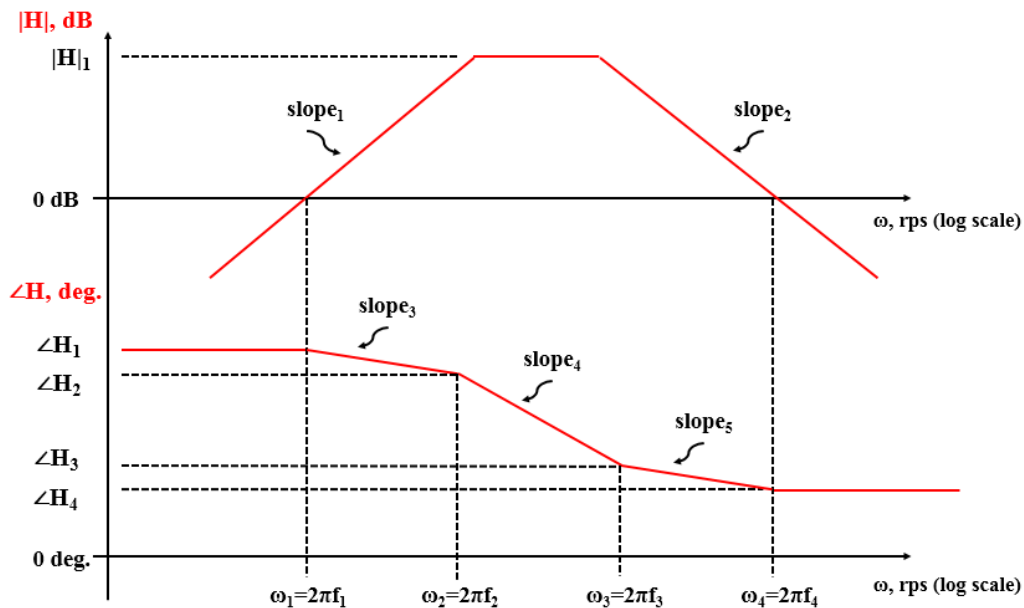



Figure 2. Bode plot approximation for Problem 1, part (d).

Referring to Figure 2 above, **determine the numerical values of the following** (note that you are being asked to provide these numerical values which are *valid for the Bode plot approximation*, not the high-accuracy Bode plot from either LTSpice or Matlab; so expect zero credit if you simulate this circuit and grab these values from the simulated plot):

- $|H|_1$ (with units of dB)
- slope_1 and slope_2 (with units of dB/decade)
- slope_3 , slope_4 , and slope_5 (with units of degrees/decade)
- $\angle H_1$, $\angle H_2$, $\angle H_3$, and $\angle H_4$ (with units of degrees)
- f_1 , f_2 , f_3 , and f_4 (with units of Hz)

Include units with your numerical answers (*that is why the units are listed*). You should first sketch the Bode approximation plot (by-hand) and then simply get the above values from your by-hand sketch. *Show your work.*

1.)

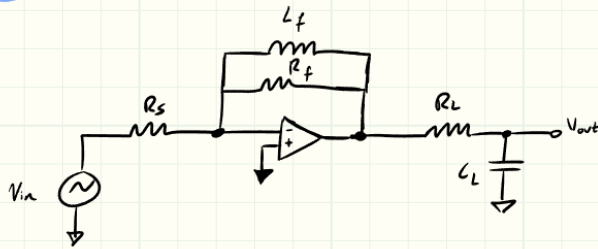

a.)
$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{-(s/\omega_{20})}{(1+s/\omega_{p1})(1+s/\omega_{p2})} \quad \downarrow$$

$$\frac{-R_f L_f s}{R_f + L_f s} = H(s) = \frac{-R_f L_f s}{R_f L_f s} \cdot \frac{1}{R_f s} = \frac{-R_f (L_f s)}{R_f (1 + L_f s/R_f)} \cdot \frac{1}{R_s}$$

$$= \frac{-L_f s/R_s}{(s + L_f/R_s)} = \frac{-L_{ss}}{s} \cdot \frac{s}{(s + L_f/R_s)} = \frac{-L_{ss}}{(s + L_f/R_s)} = \frac{-s/R_s/L_f}{1 + s/R_s/L_f}$$

$\omega_{20} = \frac{R_s}{L_f}, \quad \omega_{p1} = R_f/L_f, \quad \omega_{p2} = 1/R_L C_L$

$H(s)_{out} = \frac{V_{out}}{V_{in}} = \frac{L_f}{R_L + L_f C_L s}$

$R_L = H(s) = \frac{1}{1 + s R_L} = \frac{1}{1 + s/\omega_{p2}}$

$\omega_{p2} = 1/R_L C_L$

$$= \frac{-\frac{s}{R_L/L_f}}{\left(1 + \frac{s}{R_f/L_f}\right)\left(1 + \frac{s}{1/R_L C_L}\right)}$$

b.)
$$\frac{-\frac{s}{\omega_{20} R_L}}{\left(1 + \frac{s}{\omega_{p1}}\right)\left(1 + \frac{s}{1/R_L C_L}\right)} \Bigg|_{\omega=0}$$

$$= \frac{-\frac{s}{(0) R_L}}{\left(1 + \frac{s}{0}\right)\left(1 + \frac{s}{0}\right)} = \frac{-0}{1 \cdot 1} = 0V$$

c.)
$$\frac{-\frac{s}{\omega_{20} R_L}}{\left(1 + \frac{s}{\omega_{p1}}\right)\left(1 + \frac{s}{\omega_{p2}}\right)} \Bigg|_{\omega=\infty}$$

$$= \frac{\left(\frac{\infty}{\omega_{20} R_L}\right)}{(1 + \infty)(1 + \infty)} = \frac{1}{\infty} = 0V$$

d.) $\omega_1 = \frac{R_s}{L_f} = \frac{100}{15.92m} = 6281.4 \text{ rps}$

$f_1 = \frac{\omega_1}{2\pi} = \frac{6281.4}{2\pi} = 999.7 \text{ Hz}$

$f_1 = 1 \text{ kHz}$

$\omega_2 = \frac{R_f}{L_f} = \frac{1000}{15.92m} = 62814.1 \text{ rps}$

$f_2 = \frac{\omega_2}{2\pi} = \frac{62814.1}{2\pi} = 9997.2 = 10 \text{ kHz}$


$f_2 = 10 \text{ kHz}$

$\angle H_1 = 180^\circ + 90^\circ = 270^\circ$

$\angle H_2 = 180^\circ + 90^\circ - 45^\circ = 225^\circ$

$\angle H_3 = 180^\circ + 90^\circ - 90^\circ - 45^\circ = 135^\circ$

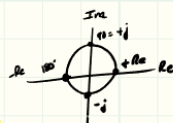$\angle H_4 = 180^\circ + 90^\circ - 90^\circ - 90^\circ = 90^\circ$



$\omega_3 = \frac{1}{R_L C_L} = \frac{1}{(1000)(1.59n)} = 628930.8 \text{ rps}$

$f_3 = \frac{\omega_3}{2\pi} = \frac{628930.8}{2\pi} = 100097 \approx 100 \text{ kHz}$

$f_3 = 100 \text{ kHz}$

$\omega_4 = \omega_3 \times 10 = 628930.8 \times 10 = 6289308$


$f_4 = \frac{\omega_4}{2\pi} = \frac{6289308}{2\pi} = 9879221.9 \approx 1000 \text{ kHz}$

$f_4 = 1000 \text{ kHz} \text{ or } 1 \text{ MHz}$

$|H_2| = \left| \frac{-R_f}{R_s} \right| = \left| \frac{-1000}{100} \right| = 10$

$20 \log_{10} (10) = 20 \log_{10} (10) = 20 \text{ dB}$

$|H_2| = 20 \text{ dB}$

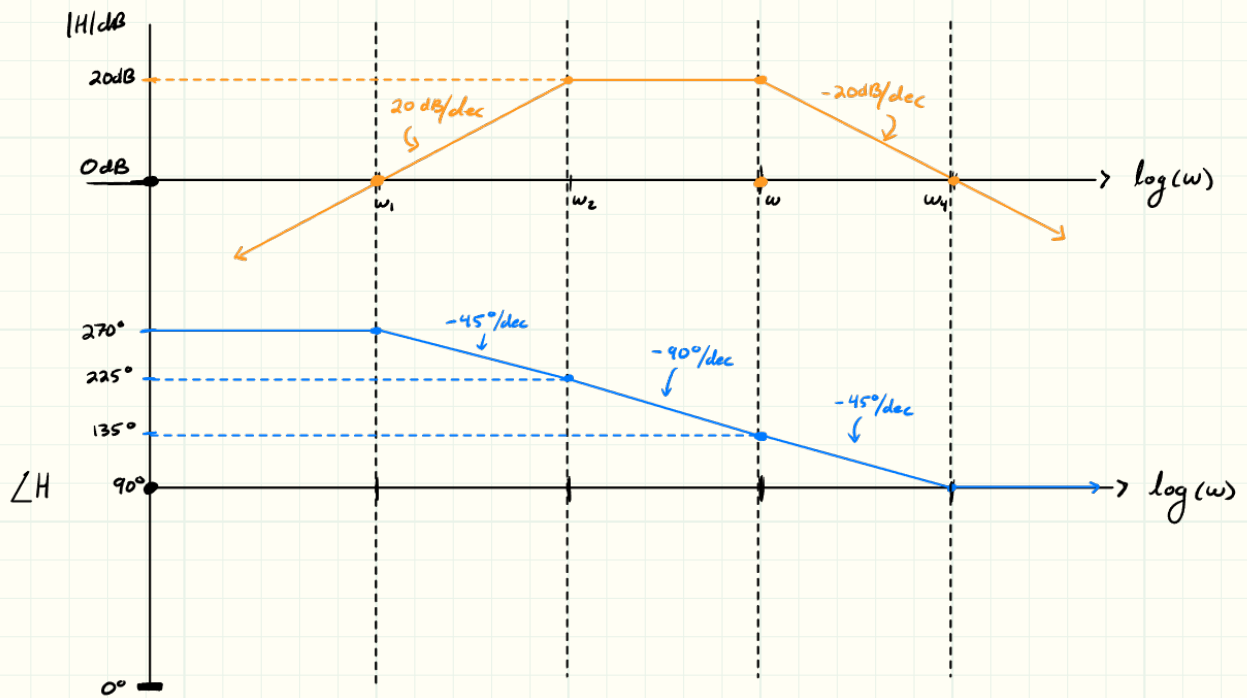

$$m_3 = \angle H_2 - \angle H_1$$

$$225 - 270$$

$$m_3 = -45^\circ/dec$$

