

- 1) (a) The impedance Z of the circuit shown below in Figure 1 is purely real (*i.e.*, *purely resistive*) at a frequency $f = 60$ Hz.

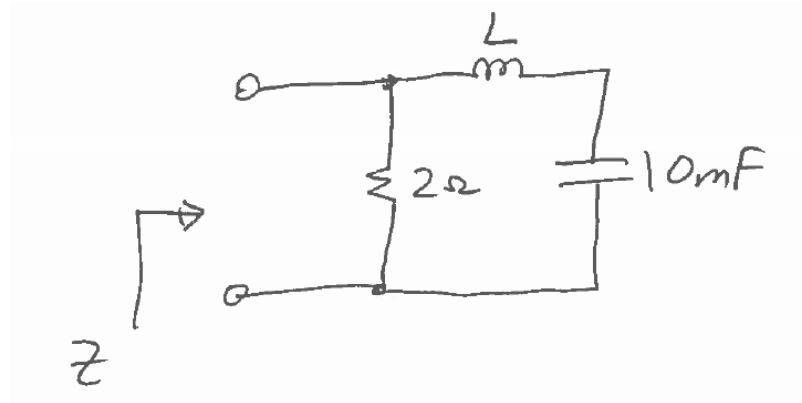


Figure 1. Circuit for Problem 1, part (a).

(i) In units of henrys, what is the value of L ? Solve this by hand. Report your L value with appropriate units in proper engineering notation format with two decimal places of precision. *Show your work.*

(ii) Run the LTSpice verification testbench file for this problem and use the .meas results to verify your by-hand work; note that the comments in the testbench are there for you to read, comprehend, and do stuff with. Attach supporting evidence that you actually verified your by-hand work and that the results agree very well.

[continued on next page]

(Problem 1, continued)

(b) Consider the circuit shown in Figure 2 below.

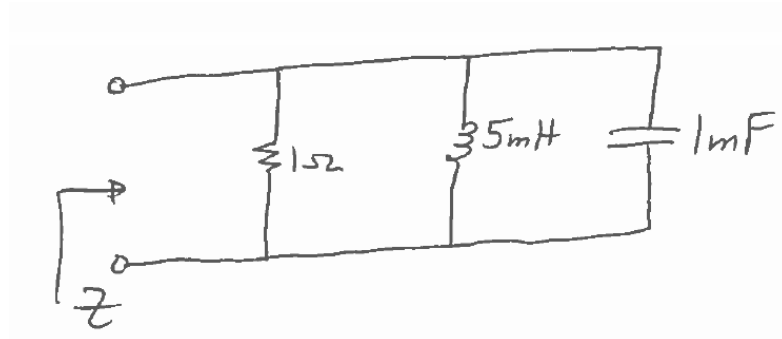



Figure 2. Circuit for Problem 1, part (b).

(i) Find the frequency, both ω in units of rps and f in units of Hz, at which the impedance Z is purely resistive. Solve this by hand. Report your two frequency values with appropriate units in proper engineering notation format with two decimal places of precision. *Show your work.*

(ii) Run the LTSpice verification testbench file for this problem and use the .meas results to verify your by-hand work; note that the comments in the testbench are there for you to read, comprehend, and do stuff with. Attach supporting evidence that you actually verified your by-hand work and that the results agree very well.

[continued on next page]

1.a)

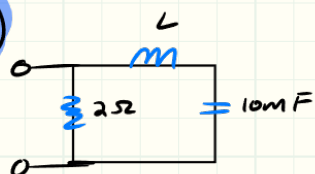

Purely Real impedance

$$f = 60 \text{ Hz}$$

$$Z_L = Z_C$$

$$j\omega L = \frac{1}{j\omega C}$$

$$\omega L = \frac{1}{\omega C}$$


$$\omega L = \frac{1}{\omega C}$$

$$L = \frac{1}{(\omega C)^2}$$

$$L = \frac{1}{(\omega(60))^2 (10 \times 10^{-3})}$$

$$L = 703.62 \mu\text{H}$$

1.b)

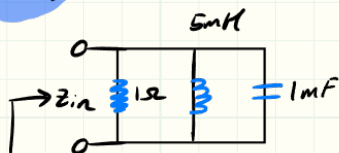

$$Z_{in} = 0$$

$$Z_L + Z_C = 0$$

$$\frac{-j}{\omega C} + \omega L = 0$$

$$\omega L = \frac{1}{\omega C}$$

$$\omega^2 LC = 1$$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$\omega = \frac{1}{\sqrt{(5 \times 10^{-3})(1 \times 10^{-3})}}$$

$$\omega = 447.21 \text{ rad/s}$$

$$f = \frac{\omega}{2\pi}$$

$$f = \frac{447.21}{2\pi}$$

$$f = 71.17 \text{ Hz}$$

```

SPICE Output Log: G:\My Drive\School\Electrical\ECT\HW\HW7\hw7_prob1a.log
ITSpice 24.0.12 for Windows
Circuit: * G:\My Drive\School\Electrical\ECT\HW\HW7\hw7_prob1a.asc
Start Time: Sat Nov 22 16:05:12 2025
solver = Normal
Maximum thread count: 12
tnom = 27
temp = 27
method = modified trap
.OP point found by inspection.

freqval: ph(v(vzeq))=0 AT 59.5693200366
zeqval: v(vzeq)=(0.00385731780048,-89.6124123573°) at 59.5693200366
reqval: re(v(vzeq))=(2.60933235147e-05,0°) at 59.5693200366

Total elapsed time: 0.138 seconds.
  
```

```

SPICE Output Log: G:\My Drive\School\Electrical\ECT\HW\HW7\hw7_prob1b.log
ITSpice 24.0.12 for Windows
Circuit: * G:\My Drive\School\Electrical\ECT\HW\HW7\hw7_prob1b.asc
Start Time: Sat Nov 22 16:08:00 2025
solver = Normal
Maximum thread count: 12
tnom = 27
temp = 27
method = modified trap
.OP point found by inspection.

freqval: ph(v(vzeq))=0 AT 71.1796537316
zeqval: v(vzeq)=(0.999924090883,3.18281169982e-05°) at 71.1796537316
reqval: re(v(vzeq))=(0.999924090883,0°) at 71.1796537316

Total elapsed time: 0.148 seconds.
  
```

2) Consider the time-domain circuit shown in Figure 3 below.


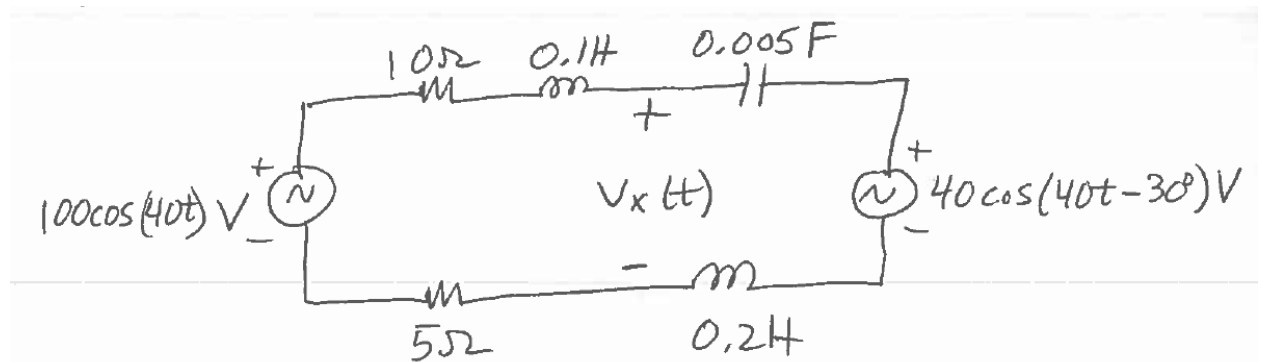


Figure 3. Circuit for Problem 2.

(i) Find $V_x(t)$, and also state the phasor value of V_x . Solve this by hand. Include units with your two answers. Write the phasor value of V_x in both rectangular form and polar form, and make it easy to distinguish your phasor-domain and time-domain answers. Your time-domain result should be written as a valid time-domain cosine waveform, and there should not be any “j”s or angle signs in your answer for $V_x(t)$, either. Expect zero credit for hard-to-decipher, incorrect work. *Show your work.*

(ii) Run the LTSpice verification testbench file for this problem and use the .ac report results to verify your by-hand work for the phasor voltage V_x in polar form; note that the comments in the testbench are there for you to read, comprehend, and do stuff with. Attach supporting evidence that you actually verified your by-hand work and that the results agree very well.

[continued on next page]

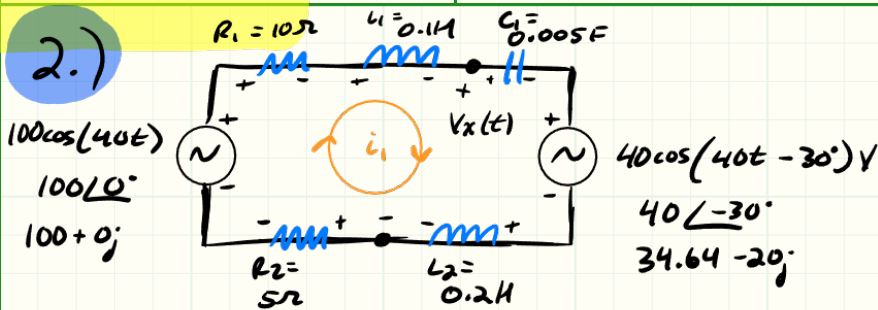

$$\begin{aligned}
 Z_{R1} &= 10\Omega \\
 Z_{R2} &= 5\Omega \\
 Z_{C1} &= j(40)(0.005) = 4j\Omega \\
 Z_{L2} &= j(40)(0.2) = 8j\Omega \\
 Z_C &= 1/j(40)(0.005) = -5j\Omega
 \end{aligned}$$

KVL @ i_1

$$-40\angle 0^\circ + Z_{R1}i_1 + Z_{C1}i_1 + Z_Ci_1 + 40\angle -30^\circ + Z_{L2}i_1 + Z_{R2}i_1 = 0$$

$$i_1 [Z_{R1} + Z_{C1} + Z_C + Z_{L2} + Z_{R2}] = 100 - (34.63 - 20j)$$

$$i_1 = \frac{(100 - (34.64 - 20j))}{[10 + 4j - 5j + 8j + 5]} = \frac{65.358 + 20j}{(15 + 7j)}$$

$$i = 4.088 - 0.574j$$

$$4.129\angle -8^\circ$$

$$V_x(t) = Z_{C1} \cdot i + 40\angle -30^\circ$$

$$V_x(t) = [Z_C + Z_{L2}]i + [34.64 - 20j]$$

$$V_x(t) = [-5j + 8j](4.088 - 0.574j) + [34.64 - 20j]$$

$$V_x(t) = 36.366 - 7.733j + 37.179\angle -12.005^\circ$$

$$V_x(t) = 37.179\cos(40t - 12.005^\circ) V$$

* G:\My Drive\School\Electrical\ECT\HW\HW7\hw7_prob2.asc

--- AC Analysis ---

frequency:	6.3662	Hz	
V(n001):	mag: 100	phase: 0°	voltage
V(n002):	mag: 100	phase: 2.03555e-15°	voltage
V(n003):	mag: 59.3889	phase: 5.55473°	voltage
V(vxpos):	mag: 57.7924	phase: -10.5761°	voltage
V(n004):	mag: 60.4902	phase: 9.35969°	voltage
V(vxneg):	mag: 20.646	phase: -8.00266°	voltage
V(n005):	mag: 38.9549	phase: 49.992°	voltage
V(vx):	mag: 37.1787	phase: -12.0049°	voltage
I(C1):	mag: 4.12921	phase: 171.997°	device_current
I(L1):	mag: 4.12921	phase: -8.00266°	device_current
I(L2):	mag: 4.12921	phase: 171.997°	device_current
I(R1):	mag: 4.12921	phase: -8.00266°	device_current
I(R2):	mag: 4.12921	phase: 171.997°	device_current
I(E1):	mag: 0	phase: 0°	device_current
I(V1):	mag: 4.12921	phase: 171.997°	device_current
I(V2):	mag: 4.12921	phase: -8.00266°	device_current
I(V3):	mag: 4.12921	phase: -8.00266°	device_current

3) Consider the time-domain circuit shown in Figure 4 below.


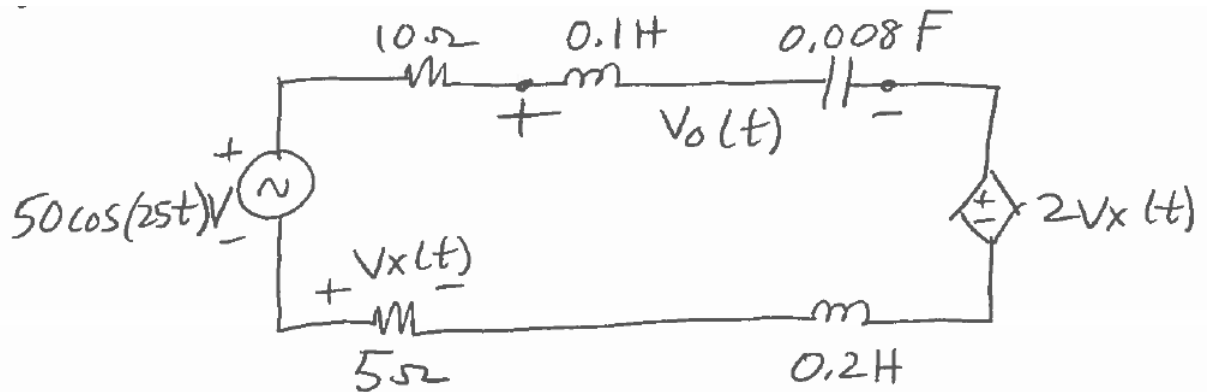


Figure 4. Circuit for Problem 3.

- i) Find $V_o(t)$, and also state the phasor value of V_o . Solve this by hand. Include units with your two answers. Write the phasor value of V_o in both rectangular form and polar form, and make it easy to distinguish your phasor-domain and time-domain answers. Your time-domain result should be written as a valid time-domain cosine waveform, and there should not be any “j”s or angle signs in your answer for $V_o(t)$, either. Expect zero credit for hard-to-decipher, incorrect work. *Show your work.*
- ii) Run the LTSpice verification testbench file for this problem and use the .ac report results to verify your by-hand work for the phasor voltage V_o in polar form; note that the comments in the testbench are there for you to read, comprehend, and do stuff with. Attach supporting evidence that you actually verified your by-hand work and that the results agree very well.

[continued on next page]

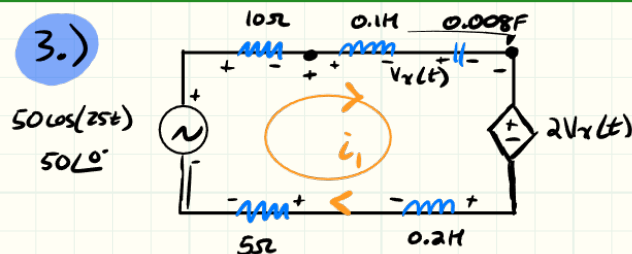

$$\omega = 25$$

$$Z_{L1} = j\omega L = j(25)(0.1) = 2.5j$$

$$Z_{L2} = j\omega L = j(25)(0.2) = 5j$$

$$Z_C = 1/j\omega C = 1/j(25)(0.008) = -5j$$

KVL @ loop i_1

$$-50 + Z_{R1}i_1 + Z_{L1}i_1 + Z_Ci_1 + 2V_x(t) + Z_{L2}i_1 + Z_{R2}i_1 = 0$$

$$i_1 [Z_{R1} + Z_{L1} + Z_C + Z_{L2} + Z_{R2}] + 2(-Z_{R2}) = 50$$

$$i_1 [10 + 2.5j - 5j + 5j + 5] + 2(-5) = 50$$

$$i_1 [5 + 2.5j] = 50$$

$$i_1 = 50 / (5 + 2.5j) = 8 - 4j$$

$$V_o(t) = Z_{eq} \cdot i_1$$

$$V_o(t) = [Z_{L1} + Z_C](8 - 4j)$$

$$V_o(t) = [2.5j - 5j](8 - 4j)$$

$$V_o(t) = -10 - 20j$$

$$V_o(t) = 22.36 \angle -116.565^\circ$$

$$V_o(t) = 22.36 \cos(25t - 116.565^\circ)$$

* G:\My Drive\School\Electrical\ECT\HW\HW7\hw7_prob3.asc

--- AC Analysis ---

frequency:	3.97887	Hz		
V(n001):	mag:	22.3607	phase:	-116.565° voltage
V(vxpos):	mag:	63.2456	phase:	-161.565° voltage
V(n002):	mag:	22.3607	phase:	-116.565° voltage
V(n1):	mag:	92.1954	phase:	167.471° voltage
V(n003):	mag:	100	phase:	-180° voltage
V(n2):	mag:	89.4427	phase:	153.435° voltage
V(vxneg):	mag:	44.7214	phase:	-116.565° voltage
V(vout):	mag:	22.3607	phase:	-116.565° voltage
I(C1):	mag:	8.94427	phase:	153.435° device_current
I(L1):	mag:	8.94427	phase:	-26.5651° device_current
I(L2):	mag:	8.94427	phase:	153.435° device_current
I(R1):	mag:	8.94427	phase:	-26.5651° device_current
I(R2):	mag:	8.94427	phase:	153.435° device_current
I(E1):	mag:	8.94427	phase:	-26.5651° device_current
I(E2):	mag:	0	phase:	0° device_current
I(V1):	mag:	8.94427	phase:	153.435° device_current
I(V2):	mag:	8.94427	phase:	-26.5651° device_current

4) Consider the phasor-domain circuit shown in Figure 5 below.


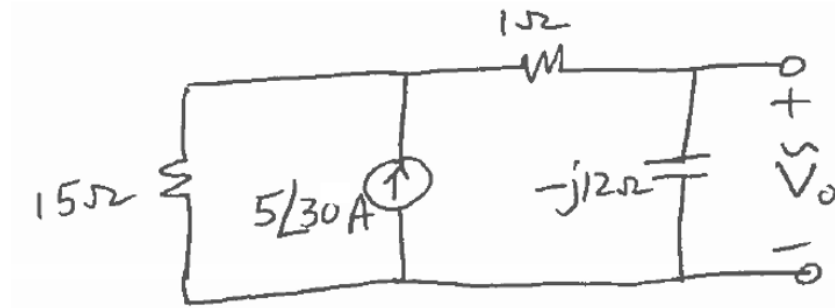


Figure 5. Circuit for Problem 4.

- i) Find the phasor voltage V_o . Solve this by hand. Write the phasor value of V_o in both rectangular form and polar form, and include units with both your rectangular and polar form answers. Expect zero credit for hard-to-decipher, incorrect work. *Show your work.*
- ii) Run the LTSpice verification testbench file for this problem and use the .ac report results to verify your by-hand work for the phasor voltage V_o in polar form; note that the comments in the testbench are there for you to read, comprehend, and do stuff with. Attach supporting evidence that you actually verified your by-hand work and that the results agree very well.

[continued on next page]

4.)

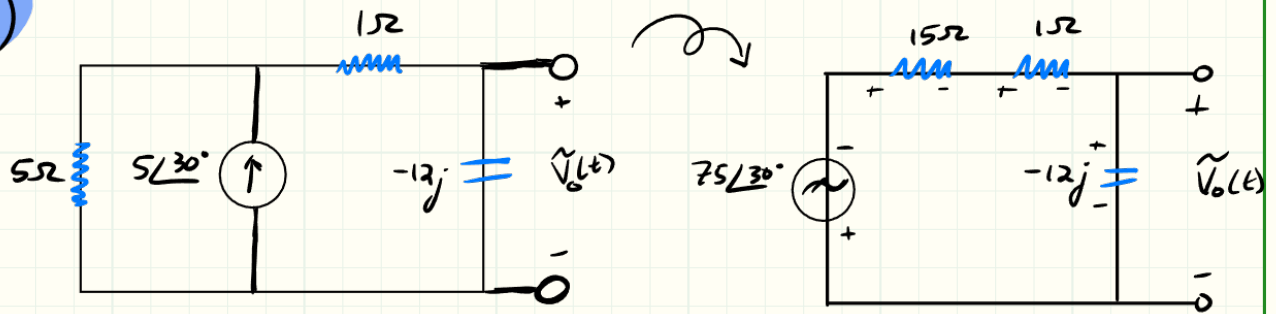

$$Z_{eq} = 15\Omega + 15\Omega - 12j$$

$$Z_{eq} = 16 - 12j$$

$$V_o = \tilde{V}_{in} \cdot \left(\frac{Z_c}{Z_c + (R_1 + R_2)} \right)$$

$$V_o = 75\angle 30^\circ \cdot \left(\frac{-12j}{-12j + (15 + 15)} \right)$$

$$V_o = \left[\frac{-12j}{16 - 12j} \right] [64.952 + 37.5j]$$

$$V_o = 41.383 - 17.677j$$

$$V_o = 45\angle -23.13^\circ \text{ V}$$

* G:\My Drive\School\Electrical\ECT\HW\HW7\hw7_prob4.asc

--- AC Analysis ---

frequency:	7.95775	Hz		
V(n001):	mag:	45.1554	phase:	-18.3669° voltage
V(vout):	mag:	44.9994	phase:	-23.1307° voltage
I(C1):	mag:	3.75003	phase:	66.8693° device_current
I(I1):	mag:	5	phase:	30° device_current
I(R1):	mag:	3.01036	phase:	-18.3669° device_current
I(R2):	mag:	3.75003	phase:	-113.131° device_current

5) Consider the phasor-domain circuit shown in Figure 6 below.


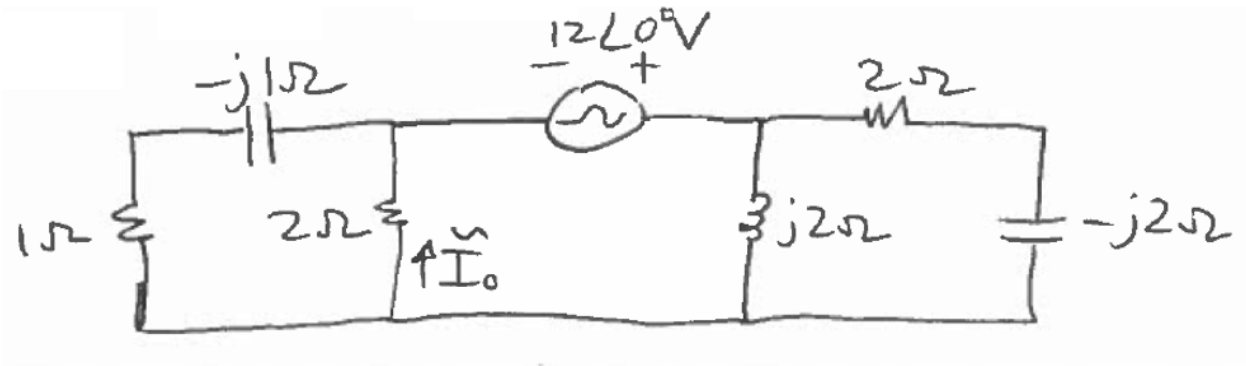


Figure 6. Circuit for Problem 5.

- i) Apply nodal analysis to determine the phasor-domain current I_0 . Solve this by hand. Write the phasor value of I_0 in both rectangular form and polar form, and include units with both your rectangular and polar form answers. Expect zero credit for hard-to-decipher, incorrect work. *Show your work.*
- ii) Run the LTSpice verification testbench file for this problem and use the .ac report results to verify your by-hand work for the phasor voltage I_0 in polar form; note that the comments in the testbench are there for you to read, comprehend, and do stuff with. Attach supporting evidence that you actually verified your by-hand work and that the results agree very well.

[continued on next page]

5.)

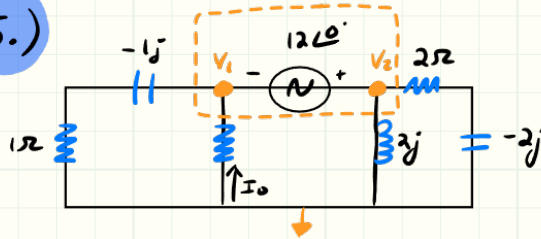

$$V_2 - V_1 = 12$$

$$V_2 = V_1 + 12$$

$$\tilde{I}_o = -\frac{V_1}{2} = \frac{-(-1.846 + 2.769j)}{2}$$

$$\tilde{I}_o = 0.963 - 1.385j$$

$$\tilde{I}_o = 1.664 \angle -56.31^\circ \text{ A}$$

KCL @ Supernode

$$\frac{V_1}{1-j} + \frac{V_1}{2} + \frac{V_2}{2j} + \frac{V_2}{2-2j} = 0$$

$$V_1 \left(1 + \frac{1}{2}j\right) + V_2 \left(\frac{1}{4} - \frac{1}{4}j\right) = 0$$

$$V_1 (1 + \frac{1}{2}j) + (V_1 + 12) \left(\frac{1}{4} - \frac{1}{4}j\right) = 0$$

$$V_1 (1 + \frac{1}{2}j) + V_1 \left(\frac{1}{4} - \frac{1}{4}j\right) + (3 - 3j) = 0$$

$$V_1 (1.25 + 0.25j) + (3 - 3j) = 0$$

$$V_1 = \frac{-(3 - 3j)}{(1.25 + 0.25j)} = -1.846 + 2.769j$$

* G:\My Drive\School\Electrical\ECT\HW\HW7\hw7_prob5.asc

--- AC Analysis ---

frequency:	7.95775	Hz			
V(n003):	mag:	10.5247	phase:	15.2551°	voltage
V(n002):	mag:	3.3282	phase:	123.69°	voltage
V(n001):	mag:	2.35339	phase:	168.69°	voltage
V(n005):	mag:	3.3282	phase:	123.69°	voltage
V(n004):	mag:	7.44208	phase:	-29.7449°	voltage
I(C1):	mag:	2.35339	phase:	168.69°	device_current
I(C2):	mag:	3.72104	phase:	-119.745°	device_current
I(L1):	mag:	5.26235	phase:	-74.7449°	device_current
I(R1):	mag:	2.35339	phase:	168.69°	device_current
I(R2):	mag:	1.6641	phase:	123.69°	device_current
I(R3):	mag:	3.72104	phase:	-119.745°	device_current
I(V1):	mag:	3.72104	phase:	150.255°	device_current
I(V2):	mag:	1.6641	phase:	-56.3099°	device_current

6) Consider the phasor-domain circuit shown in Figure 7 below.


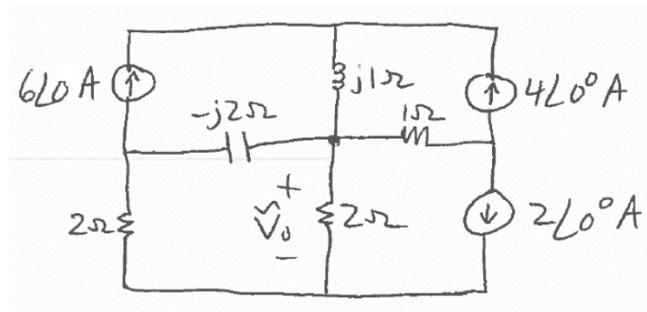


Figure 7. Circuit for Problem 6.

- i) Use mesh analysis to find the phasor-domain voltage V_o . Solve this by hand. Write the phasor value of V_o in both rectangular form and polar form, and include units with both your rectangular and polar form answers. Expect zero credit for hard-to-decipher, incorrect work. *Show your work.*
- ii) Run the LTSpice verification testbench file for this problem and use the .ac report results to verify your by-hand work for the phasor voltage V_o in polar form; note that the comments in the testbench are there for you to read, comprehend, and do stuff with. Attach supporting evidence that you actually verified your by-hand work and that the results agree very well.

[continued on next page]

6.)

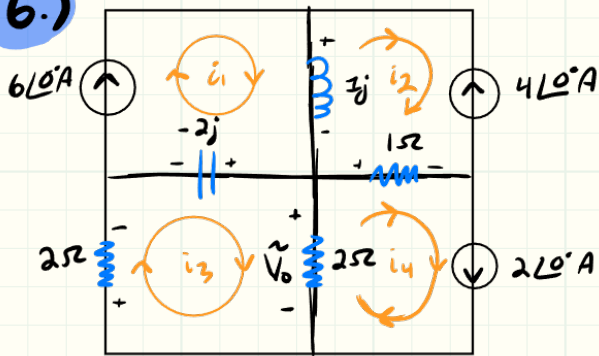

$$\begin{aligned} i_1 &= 6\angle 0^\circ \\ i_2 &= -4\angle 0^\circ \\ i_4 &= 2\angle 0^\circ \end{aligned}$$

KVL @ i_3

$$+(2\Omega)(i_3) + (2j)(i_1 - i_3) + (2\Omega)(i_3 - i_4) = 0$$

$$2i_3 + 2ji_1 - 2ji_3 + 2i_3 - 2i_4 = 0$$

$$(2j)i_1 + (4 - 2j)i_3 + (-2)i_4 = 0$$

$$(2j)(6) + (4 - 2j)i_3 + (-2)(2) = 0$$

$$12j + (4 - 2j)i_3 - 4 = 0$$

$$i_3 = \frac{(4 - 12j)}{(4 - 2j)}$$

$$i_3 = 2 - 2j$$

$$\tilde{V}_o = Z \cdot (i_3 - i_4)$$

$$\tilde{V}_o = (2\Omega)[(2 - 2j) - (2)]$$

$$\tilde{V}_o = -4j$$

$$\tilde{V}_o = 4\angle -90^\circ$$

$$\tilde{I}_o = -2j \text{ or } 2\angle -90^\circ$$

* G:\My Drive\School\Electrical\ECT\HW\HW7\hw7_prob6.asc

--- AC Analysis ---

frequency:	7.95775	Hz		
V(n002):	mag: 5.65685	phase: 135°	voltage	
V(n001):	mag: 6	phase: 90°	voltage	
V(vout):	mag: 4	phase: -90°	voltage	
V(n003):	mag: 7.2111	phase: -146.31°	voltage	
I(C1):	mag: 4.47214	phase: 26.5651°	device_current	
I(L1):	mag: 10	phase: 5.08889e-15°	device_current	
I(I1):	mag: 6	phase: 0°	device_current	
I(I2):	mag: 4	phase: 0°	device_current	
I(I3):	mag: 2	phase: 0°	device_current	
I(R1):	mag: 2.82843	phase: 135°	device_current	
I(R2):	mag: 2	phase: -90°	device_current	
I(R3):	mag: 6	phase: 180°	device_current	

7) For the circuit shown below in Figure 8:


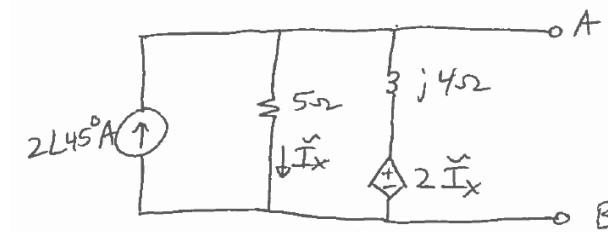


Figure 8. Circuit for Problem 7.

- (a) Find the phasor-domain Thevenin model parameters V_{TH} and Z_{TH} with respect to nodes A and B. Solve this by hand, and *show your work*. Verify your by-hand work in LTSpice. Attach supporting evidence that you actually verified your by-hand work and that the results agree very well.
- (b) Find the value of Z_L that, when connected to nodes A and B, dissipates the maximum amount of power from the above circuit. Solve this by hand, and *show your work*. While LTSpice verification is not required for this part, you must get this part right in order to be eligible for any credit on this entire problem.
- (c) With the constraint that the load be purely resistive, find the value of R_L that, when connected to nodes A and B, dissipates the maximum amount of power from the above circuit. Solve this by hand, and *show your work*. While LTSpice verification is not required for this part, you must get this part right in order to be eligible for any credit on this entire problem.
- (d) Compute the *average power* delivered to the load for parts (b) and (c). Note that there are **two** by-hand answers for this part; thus, you should make it *really easy* for me to figure out which average load power quantity is for the load of part (b) and which average load power quantity is for the part (c) load. Solve this by hand, and *show your work*. Verify your by-hand work in LTSpice. Attach supporting evidence that you actually verified your by-hand work and that the results agree very well. Again, there are two quantities that need verifying in LTSpice, so make it clear that you verified both of them.

7.)

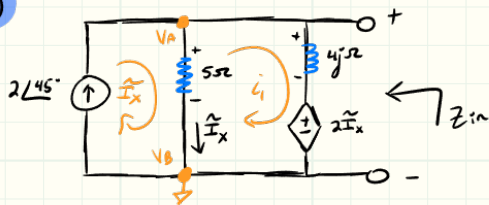

a.) $(V_1 - \tilde{I}_x) = (2\angle 45^\circ - \tilde{I}_x)$

KVL @ I_1

$$5(\tilde{I}_x) - (2\angle 45^\circ - \tilde{I}_x)j4 - 2\tilde{I}_x = 0$$


$$3\tilde{I}_x + 4j\tilde{I}_x = 2\angle 45^\circ \cdot 4j$$

$$\tilde{I}_x = \frac{(2\angle 45^\circ \cdot 4j)}{(3 + 4j)}$$

$$V_{TH} = 5 \cdot \tilde{I}_x = 5 \cdot (0.226 + 1.584j)$$

$$V_{TH} = 1.130 + 7.920j$$

$$V_{TH} = 8\angle 81.87^\circ$$

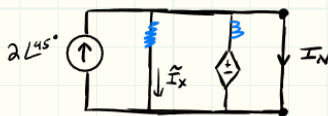

Current takes path of least Resistance $\tilde{I}_N = 2\angle 45^\circ$

$$Z_{TH} = \frac{V_{TH}}{I_N} = \frac{8\angle 81.87^\circ}{2\angle 45^\circ}$$

$$Z_{TH} = 3.2 + 2.4j$$

$$Z_{TH} = 4\angle 36.87^\circ$$

$$\begin{aligned} V_{TH} &= 1.13 + 7.92j \\ V_{TH} &= 8\angle 81.87^\circ \\ Z_{TH} &= 3.2 + 2.4j \\ Z_{TH} &= 4\angle 36.87^\circ \end{aligned}$$

b.) Z_L at max

$$Z_L = -Z_{TH}$$

$$Z_L = -3.2 - 2.4j$$


c.) load Purely Resistance

$$R_L = \sqrt{R_{TH}^2 + Z_{TH}^2}$$

$$R_L = \sqrt{(3.2)^2 + (2.4)^2}$$

$$R_L = 4\Omega$$

d.)

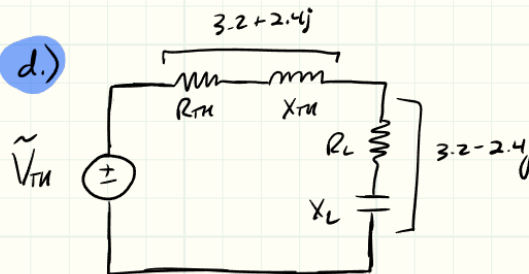

for part b

$$P_{avg} = \frac{1}{2} |I_L|^2 R_L$$

$$I_L = \frac{V_{TH}}{Z_{TH} + Z_L}; R_L = R_{TH}$$

$$P_{avg} = \frac{1}{2} \frac{|V_{TH}|^2}{4R_{TH}} = \frac{|V_{TH}|^2}{8R_{TH}}$$

$$|V_{TH}| = \sqrt{(1.314)^2 + (7.9191)^2}$$

$$R_{TH} = \text{Re}\{Z_L\} = \text{Re}\{3.2 + 2.4j\}$$

$$R_{TH} = 3.2\Omega$$

$$P_{avg} = \frac{181^2}{8(3.2)} =$$

$$P_{avg} = 2.5W$$

for part c

$$P_{avg} = \frac{1}{2} |I_L|^2 R_L$$

$$I_L = \frac{V_{TH}}{Z_{TH} + Z_L} = \frac{V_{TH}}{(R_{TH} + R_L) + jZ_{TH}}$$

$$P_{avg} = \frac{1}{2} \frac{|V_{TH}|^2 R_L}{(R_{TH} + R_L)^2 + Z_{TH}^2}$$

$$|V_{TH}| = 8V$$

$$R_{TH} = \text{Re}\{Z_L\} = \text{Re}\{3.2 + 2.4j\}$$

$$R_{TH} = 3.2\Omega$$

$$Z_{TH} = \text{Im}\{Z_L\} = \text{Im}\{3.2 + 2.4j\}$$

$$Z_{TH} = 2.4\Omega$$

$$R_L = 4\Omega$$

$$P_{avg} = \frac{1}{2} \frac{181^2 (4)}{(3.2 + 4)^2 + 2.4^2}$$

$$P_{avg} = \frac{256}{2(57.6)}$$

$$P_{avg} = 2.22W$$

Part a.)

```
* G:\My Drive\School\Electrical\ECT\HW\HW7\hw7_prob7a.asc
--- AC Analysis ---
frequency:      7.95775      Hz
V(vout):      mag:      8 phase:      81.8699°      voltage
V(n001):      mag: 8.88178e-16 phase:      180°      voltage
V(n003):      mag:      3.2 phase:      81.8699°      voltage
V(vzout):      mag:      4 phase:      36.8699°      voltage
V(n002):      mag: 4.44089e-16 phase:      180°      voltage
V(n004):      mag:      1.6 phase:      36.8699°      voltage
I(H1):      mag:      1.2 phase:      -8.1301°      device_current
I(H2):      mag:      0.6 phase:      -53.1301°      device_current
I(L1):      mag:      1.2 phase:      -8.1301°      device_current
I(L2):      mag:      0.6 phase:      -53.1301°      device_current
I(I1):      mag:      2 phase:      45°      device_current
I(I2):      mag:      0 phase:      0°      device_current
I(I3):      mag:      1 phase:      0°      device_current
I(R1):      mag:      1.6 phase:      81.8699°      device_current
I(R2):      mag:      0.8 phase:      36.8699°      device_current
I(V1):      mag:      1.6 phase:      81.8699°      device_current
I(V2):      mag:      0.8 phase:      36.8699°      device_current
```

Part b.)

```
SPICE Output Log: G:\My Drive\School\Electrical\ECT\HW\HW7\hw7_prob7d.log
LTspice 24.0.12 for Windows
Circuit: * G:\My Drive\School\Electrical\ECT\HW\HW7\hw7_prob7d.asc
Start Time: Sat Nov 22 16:14:31 2025
13: both pins shorted together -- ignoring.
solver = Normal
Maximum thread count: 12
tnom = 27
temp = 27
method = modified trap
WARNING: Less than two connections to node vrlckt1. This node is used by e1.
WARNING: Less than two connections to node vrlckt2. This node is used by e2.
Direct Newton iteration for .op point succeeded.

pload1: MAX(v(vrlckt1)*i(v3)/2)=2.50026047011 FROM 0 TO 0.5
pload2: MAX(v(vrlckt2)*i(v4)/2)=2.21992772377 FROM 0 TO 0.5

Total elapsed time: 0.402 seconds.
```