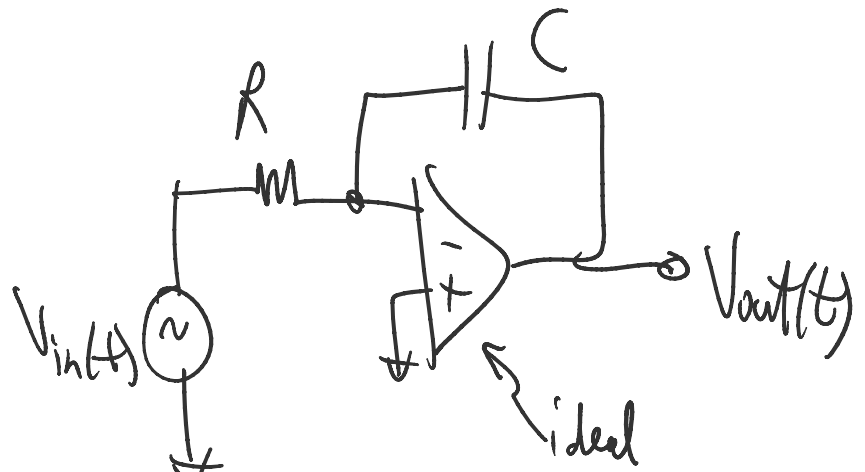



Example



$$V_{in}(t) = \cos(\omega_0 t) = \cos(2\pi f_0 t), f_0 = 5 \text{ kHz}$$

$$R = 100 \Omega, C = 1 \mu\text{F} \Rightarrow \text{Determine } V_{out}(t) \text{ via phasor analysis}$$

phasor domain ckt

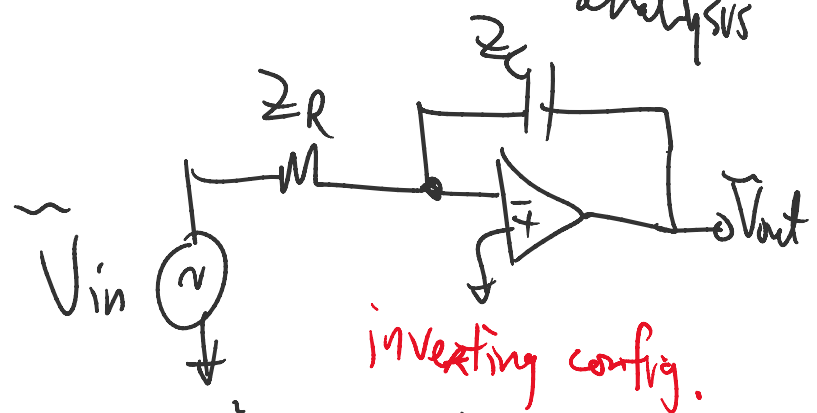

$$\tilde{V}_{in} = 1 \angle 0^\circ \text{ V}$$

$$Z_R = 100 \Omega (= R), Z_C = \frac{j}{\omega_0 C} = \frac{j}{2\pi(5\text{k})(1\mu)} \approx -j31.83 \Omega$$

$$A_V = \frac{\tilde{V}_{out}}{\tilde{V}_{in}} = \frac{-Z_C}{Z_R} = \frac{-j31.83}{100} = \frac{31.83 \angle 90^\circ}{100 \angle 0^\circ}$$

$$= 318.31 \text{ m} \angle +90^\circ \text{ V/V}$$


$\tilde{V}_{in} \rightarrow \tilde{V}_{out}$

$$\tilde{V}_{out} = (A_V) (\tilde{V}_{in}) = (318.31m \angle 90^\circ) (1 \angle 0^\circ)$$

$$\frac{(V/V)}{(V/V)} \approx 318.31m \angle 90^\circ V$$

$$V_{out}(t) = \mathcal{P}^{-1} \{ \tilde{V}_{out} \} = 318.31 \cos(\omega t + 90^\circ) mV$$

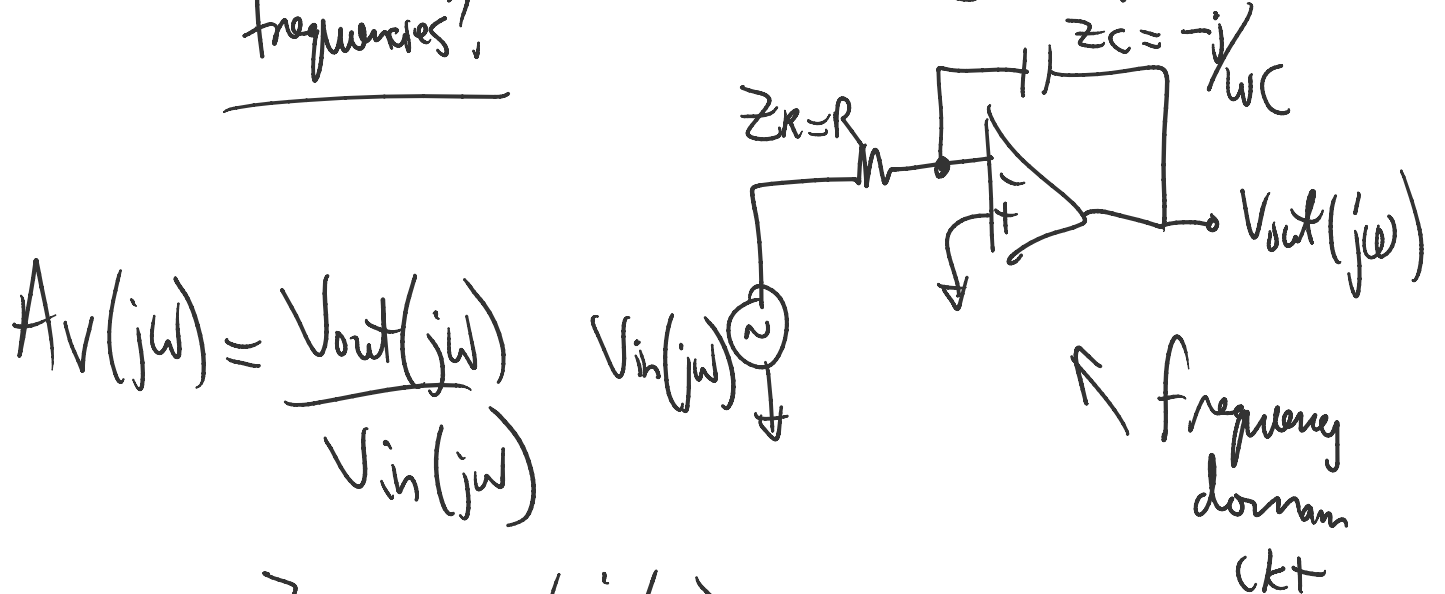How will this ckt behave over a range of frequencies?




$$A_V(j\omega) = \frac{V_{out}(j\omega)}{V_{in}(j\omega)}$$

$$= -\frac{Z_C}{Z_R} = -\frac{(-j/\omega C)}{R} = \frac{+j}{\omega R C} = \frac{1}{\omega R C} \angle +90^\circ$$

$\frac{V/V}{V/V}$

$$|A_V| = \frac{1}{\omega R C}, \angle A_V = +90^\circ$$


$\frac{V/V}{V/V}$

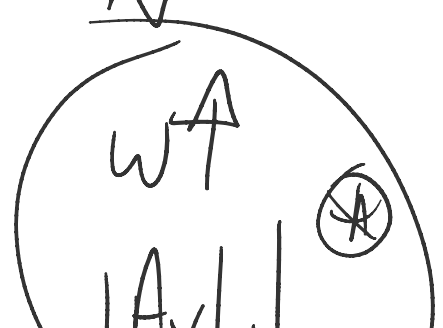

V/V

$|A_v| \downarrow$

Bode response

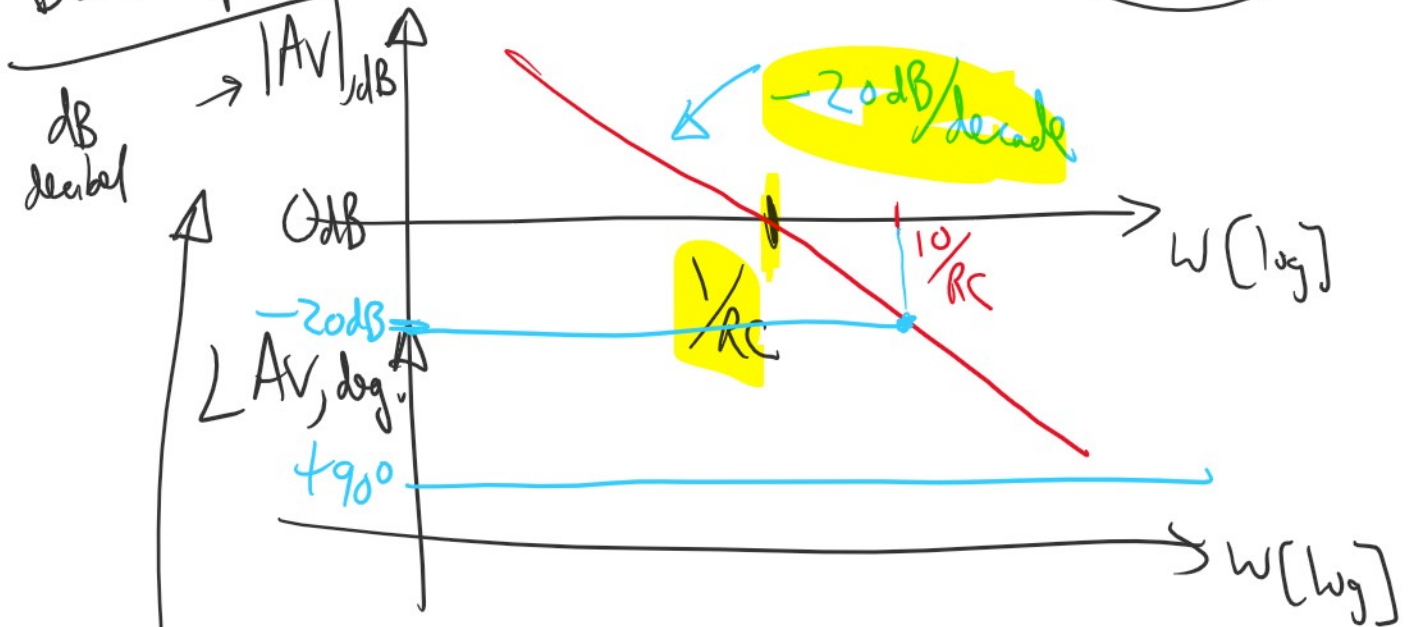

$$20 \log_{10}(|A_v|)$$

$$\frac{1}{\omega RC} \stackrel{\text{set}}{=} 1 \text{ V/V} \Rightarrow \omega = \frac{1}{RC}$$

$$|A_v| = \frac{1}{\omega RC}$$