

1) Consider the circuit shown in Figure 1.


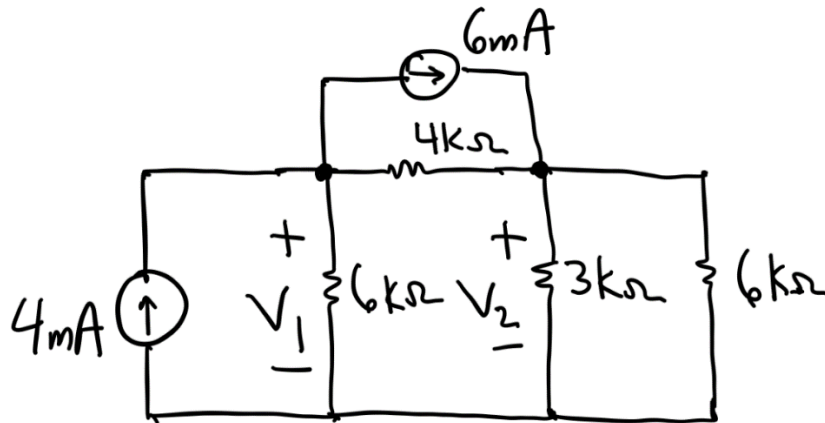


Figure 1. Circuit for Problem 1.

- a) Find both V_1 and V_2 by the node voltage method.
- b) Verify your by-hand answers for V_1 and V_2 in LTSpice. Write out the answers you got from LTSpice and attach any supporting evidence that you actually simulated the circuit to verify your work. The answers you write out for this part should be the same as the results you provided in part (a); if they don't match **by both sign and magnitude**, expect zero credit. Also, expect zero credit 1) if your by-hand and simulated results agree but the results are incorrect, 2) if you do not perform the LTSpice verification altogether, 3) if you only do the LTSpice verification but not the by-hand solution, or 4) if you do not label the voltage nodes and have LTSpice compute the values of V_1 and V_2 for you.

Make sure to include appropriate units with your numerical answers and list your answers in proper engineering notation format with 2 decimal places of precision! **That means no fractions, no square roots, no instances of π , etc.** Note that this applies to all problems in this course, not just this one!

[continued on next page]

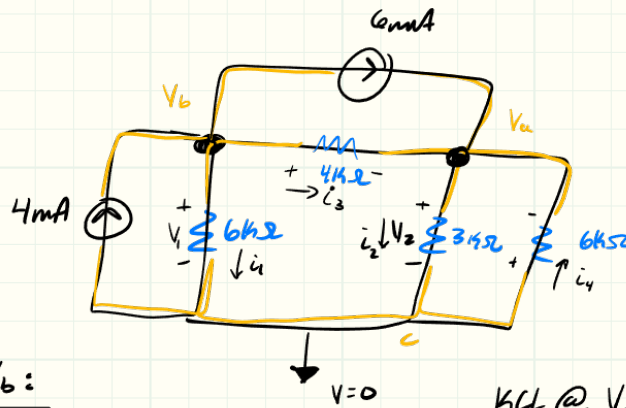

KCL @ V_b :

$$4mA - 6mA - i_3 - i_1 = 0$$

$$-2mA - i_3 - i_1 = 0$$

$$2mA = -\frac{V_b - V_a}{R_3} - \frac{V_b - 0}{R_1}$$

$$2mA = -\frac{1}{R_3}(V_b - V_a) - \frac{1}{R_1}(V_b)$$

$$2mA = -\frac{1}{R_3}(V_b) + \frac{1}{R_3}(V_a) - \frac{1}{R_1}(V_b)$$

① $2mA = \left(\frac{1}{R_3}\right)V_a + \left(-\frac{1}{R_1} - \frac{1}{R_3}\right)V_b \rightarrow \text{into matrix}$

KCL @ V_a :

$$6mA + i_3 - i_2 + i_4 = 0$$

$$6mA + \frac{V_b - V_a}{R_3} - \frac{V_a - 0}{R_2} + \frac{0 - V_a}{R_4} = 0$$

$$6mA + \frac{1}{R_3}(V_b - V_a) - \frac{1}{R_2}(V_a) - \frac{1}{R_4}(V_a) = 0$$

$$6mA + \frac{1}{R_3}(V_b) - \frac{1}{R_3}(V_a) - \frac{1}{R_2}(V_a) - \frac{1}{R_4}(V_a) = 0$$

② $6mA = \left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_2}\right)V_a - \left(\frac{1}{R_3}\right)V_b \rightarrow \text{into matrix}$


$$\begin{bmatrix} 2mA \\ 6mA \end{bmatrix} = \begin{bmatrix} G_3 & -G_1 - G_3 \\ G_2 + G_3 + G_4 & -G_3 \end{bmatrix} \begin{bmatrix} V_a \\ V_b \end{bmatrix} \quad \begin{cases} G_1 = 0.0001666 \\ G_2 = 0.0003333 \\ G_3 = 0.00025 \\ G_4 = 0.0001666 \end{cases}$$

$$\begin{bmatrix} V_a \\ V_b \end{bmatrix} = \begin{bmatrix} 0.00025 & -0.000416 \\ 0.00075 & -0.00025 \end{bmatrix}^{-1} \begin{bmatrix} 0.002 \\ 0.006 \end{bmatrix}$$

$$\begin{aligned} V_a &= 8V, & V_b &= 0V \\ V_1 &= (V_b - 0) \rightarrow V_1 = 0V - 0 = 0V \\ V_2 &= (V_a - 0) \rightarrow V_2 = 8V - 0 = 8V \end{aligned}$$

$$V_1 = 0V$$

$$V_2 = 8V$$

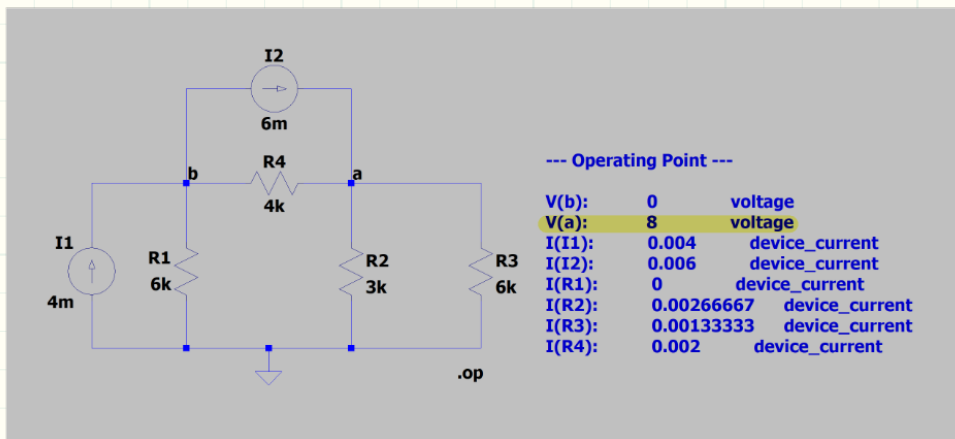

2) Consider the circuit shown in Figure 2.


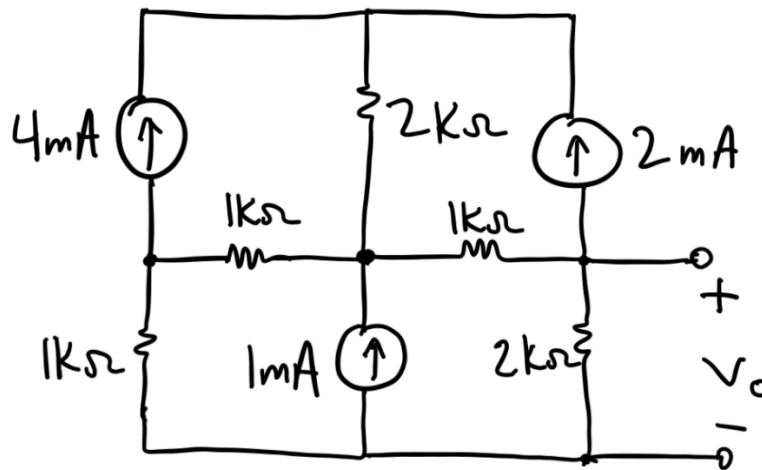


Figure 2. Circuit for Problem 2.

a) Find V_o using the node voltage method.

b) Verify your by-hand answer for V_o LTSpice. **Write out the answer you got from LTSpice** and attach any supporting evidence that you actually simulated the circuit to verify your work. The answer you write out for this part should be the same as the result you provided in part (a); if it doesn't match **by both sign and magnitude**, expect zero credit. Also, expect zero credit 1) if your by-hand and simulated results agree but the results are incorrect, 2) if you do not perform the LTSpice verification altogether, 3) if you only do the LTSpice verification but not the by-hand solution, or 4) if you do not label the voltage nodes and have LTSpice compute the value of V_o for you.

[continued on next page]

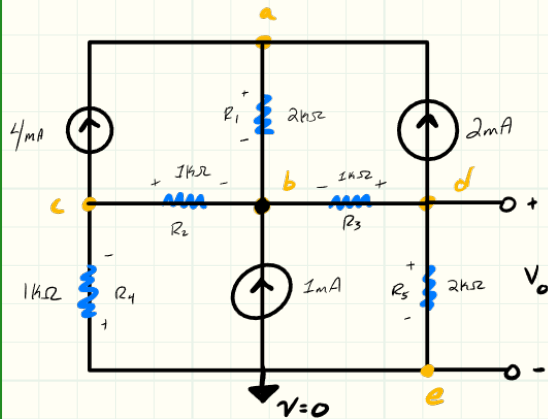

$$a.) \quad 4mA + 2mA - i_1 = 0$$

$$i_1 = 6mA$$

$$6mA = G_1 (V_a - V_b)$$

$$6mA = (G_1) V_a - (G_1) V_b$$

$$b.) \quad i_1 + i_2 + i_3 = 1mA$$

$$1mA = G_1(V_a - V_b) + G_2(V_c - V_b) + G_3(V_d - V_b)$$

$$1mA = G_1 V_a - G_1 V_b + G_2 V_c - G_2 V_b + G_3 V_d - G_3 V_b$$

$$1mA = (G_1) V_a + (-G_1 - G_2 - G_3) V_b + (G_2) V_c + (G_3) V_d$$

$$1mA = (-G_1) V_a + (G_1 + G_2 + G_3) V_b + (-G_2) V_c + (-G_3) V_d$$

$$c.) \quad i_4 - 4mA - i_2 = 0$$

$$\begin{bmatrix} 0.006A \\ -0.001A \\ -0.004A \\ -0.002A \end{bmatrix} = \begin{bmatrix} G_1 & -G_1 & 0 & 0 \\ -G_1 & (G_1+G_2+G_3) & -G_2 & -G_3 \\ 0 & -G_2 & (G_2+G_4) & 0 \\ 0 & -G_3 & 0 & (G_3+G_5) \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \\ V_d \end{bmatrix} \quad \begin{cases} G_1 = 0.0005 \\ G_2 = 0.001 \\ G_3 = 0.001 \\ G_4 = 0.001 \\ G_5 = 0.0005 \end{cases}$$

$$4mA = -i_2 + i_4$$

$$4mA = -G_2(V_c - V_b) + G_4(0 - V_c)$$

$$4mA = -G_2 V_c + G_2 V_b - G_4 V_c$$

$$4mA = (G_2) V_b + (-G_2 - G_4) V_c$$

$$-4mA = (-G_2) V_b + (G_2 + G_4) V_c$$

$$\begin{bmatrix} V_a \\ V_b \\ V_c \\ V_d \end{bmatrix} = \begin{bmatrix} 0.0005 & -0.0005 & 0 & 0 \\ -0.0005 & 0.0025 & -0.001 & -0.001 \\ 0 & -0.001 & 0.002 & 0 \\ 0 & -0.001 & 0 & 0.0015 \end{bmatrix}^{-1} \begin{bmatrix} 0.006 \\ 0.001 \\ -0.004 \\ -0.002 \end{bmatrix}$$

$$V_a = 16.4V \quad V_b = 4.4V \quad V_c = 0.2V \quad V_d = 1.6V$$

$$V_o = V_d - V_e$$

$$V_o = 1.6V - 0$$

$$V_o = 1.6V$$

$$d.) \quad -2mA - i_5 - i_3 = 0$$


$$2mA = -i_5 - i_3$$

$$2mA = -G_5(V_d - 0) - G_3(V_d - V_b)$$

$$2mA = -G_5 V_d - G_3 V_d + G_3 V_b$$

$$2mA = (G_3) V_b + (-G_3 - G_5) V_d$$

$$-2mA = (-G_3) V_b + (G_3 + G_5) V_d$$

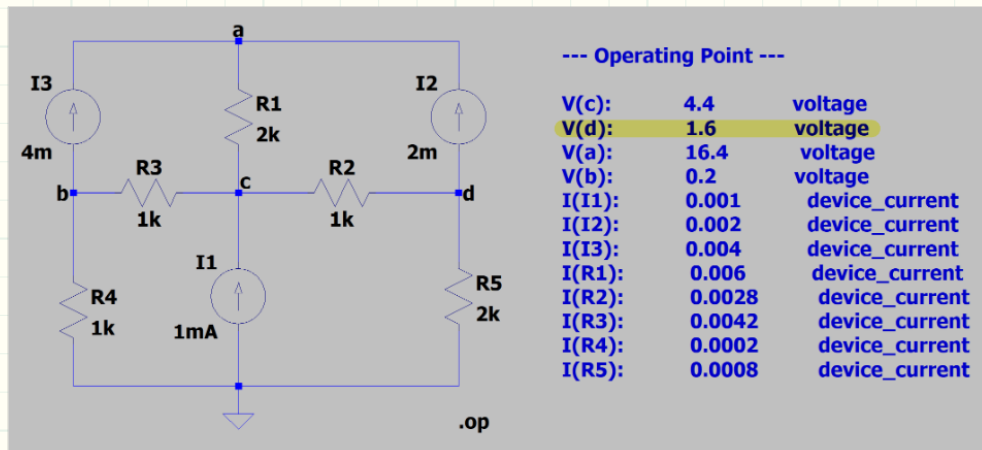

3) Consider the circuit shown in Figure 3.


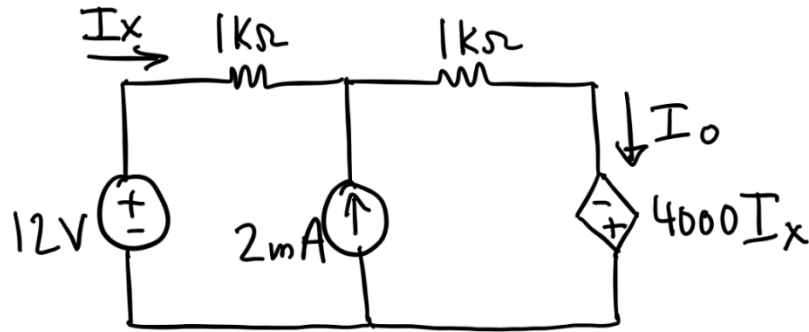


Figure 3. Circuit for Problem 3.

a) Find I_0 using the node voltage method.

b) Verify your by-hand answer for I_0 in LTSpice. **Write out the answer you got from LTSpice** and attach any supporting evidence that you actually simulated the circuit to verify your work. The answer you write out for this part should be the same as the result you provided in part (a); if it doesn't match **by both sign and magnitude**, expect zero credit. Also, expect zero credit 1) if your by-hand and simulated results agree but the results are incorrect, 2) if you do not perform the LTSpice verification altogether, 3) if you only do the LTSpice verification but not the by-hand solution, or 4) if you do not use a properly oriented 0-V voltage source ammeter to capture the I_0 current in simulation.

[continued on next page]

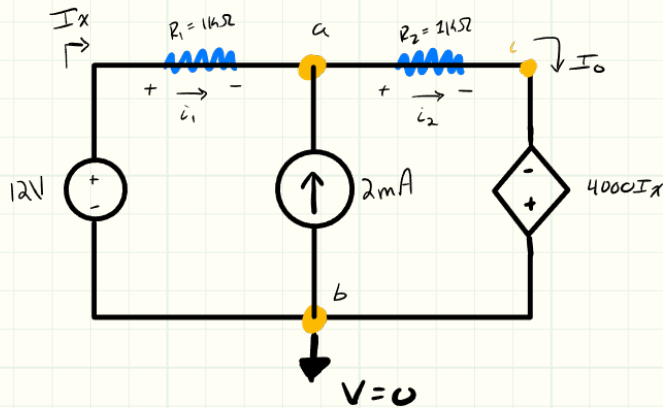

$$\left[\begin{aligned} I_x &= \frac{12V - V_a}{1000} \\ (0V - V_c) &= 4000 I_x \end{aligned} \right]$$

$$-V_c = 4000 I_x$$

$$V_c = -4000 \left[\frac{12V - V_a}{1000} \right]$$

$$V_c = \frac{-4000(12V - V_a)}{1000}$$

$$V_c = -4(12V - V_a)$$

$$V_c = 4V_a - 48V$$

KVL @ V_a :

$$i_1 + 2mA = i_2$$

$$\frac{12V - V_a}{R_1} + 2mA = \frac{V_a - V_c}{R_2}$$

$$\frac{12V - V_a}{R_1} - \frac{V_a - V_c}{R_2} = -0.002$$

$$\frac{1}{1k\Omega} [12V - V_a - V_a + V_c] = -0.002$$

$$12V - 2V_a + V_c = -2A$$

$$12V - 2V_a + (4V_a - 48V) = -2A$$

$$2V_a - 36V = -2V$$

$$2V_a = 34V$$

$$V_a = 17V$$

Solving I_0

$$V_c = 4V_a - 48V$$


$$V_c = 4(17V) - 48V$$

$$V_c = 20V$$

$$I_0 = i_2 = \frac{V_a - V_c}{R_2}$$

$$I_0 = \frac{17V - 20V}{1000\Omega} = -0.003A$$

$$I_0 = -3mA$$

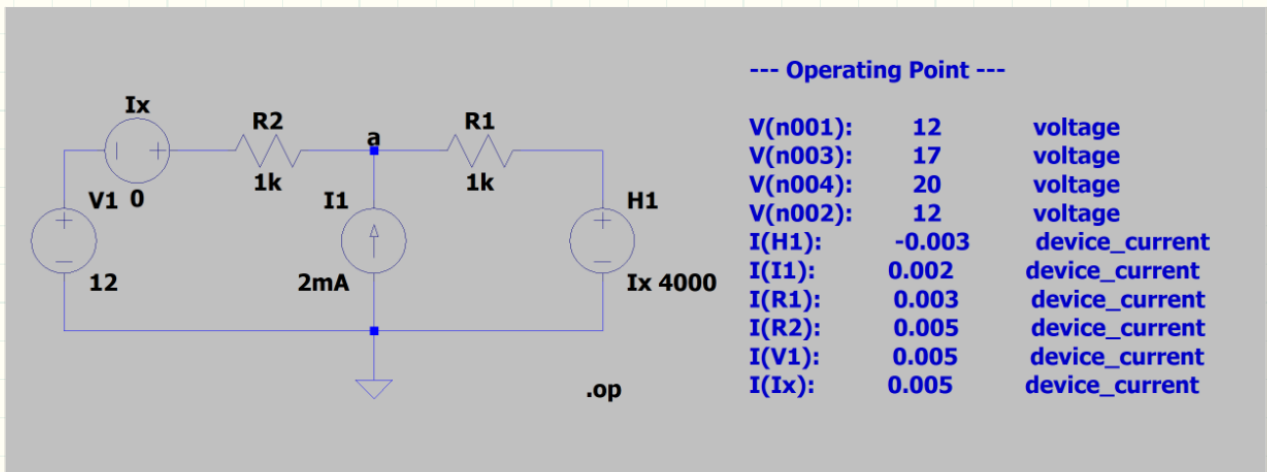

4) Consider the circuit shown in Figure 4.


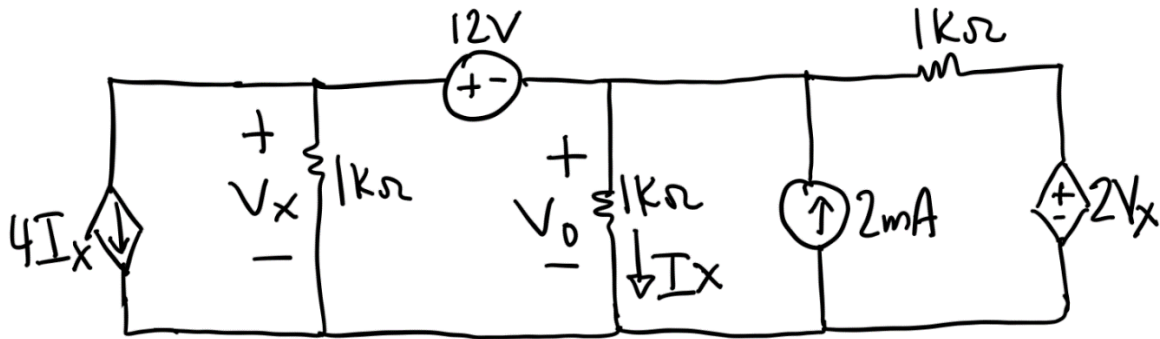


Figure 4. Circuit for Problem 4.

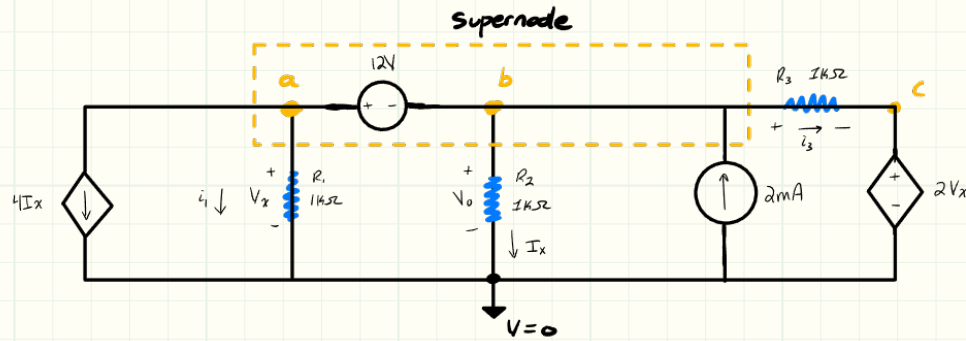- a) Find V_0 using the node voltage method.
- b) Verify your by-hand answer for V_0 LTSpice. **Write out the answer you got from LTSpice** and attach any supporting evidence that you actually simulated the circuit to verify your work. The answer you write out for this part should be the same as the result you provided in part (a); if it doesn't match **by both sign and magnitude**, expect zero credit. Also, expect zero credit 1) if your by-hand and simulated results agree but the results are incorrect, 2) if you do not perform the LTSpice verification altogether, 3) if you only do the LTSpice verification but not the by-hand solution, or 4) if you do not label the voltage nodes and have LTSpice compute the value of V_0 for you.



KCL @ Supernode:

$$4I_x + i_1 + I_x + i_3 = 2mA$$

$$5I_x + i_1 + i_3 = 2mA$$

$$5I_x + \left[\frac{V_x}{R_1} \right] + \left[\frac{V_b - 2V_x}{R_3} \right] = 2mA$$

$$V_x = V_a ; R_1 = R_2 = R_3 = 1k\Omega ; V_a - 12V = V_b$$

$$5I_x + \frac{V_a}{R_1} + \frac{(V_a - 12) - 2V_a}{R_3} = 2mA$$

$$5I_x + \frac{V_a}{R} + \frac{-V_a - 12}{R} = 2mA$$

$$5I_x - \frac{12}{R} = 2mA$$


$$I_x = \frac{2mA + 12/R}{5}$$

$$I_x = 0.0028A \quad V = IR$$

$$I_x = 2.8mA \quad V_o = I_x \cdot R_2$$

$$V_o = 0.0028A \cdot 1000\Omega$$

$$V_o = 2.8V$$

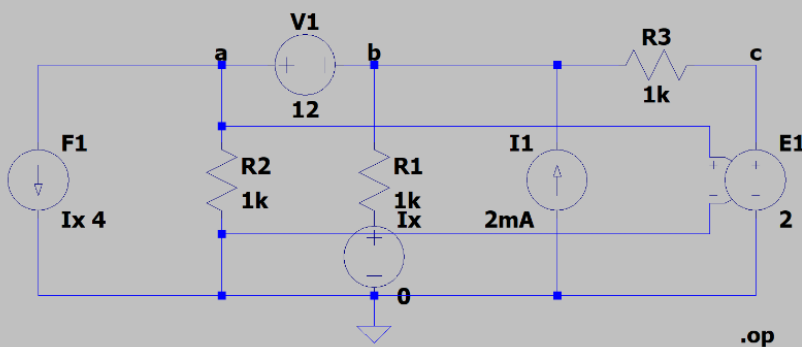

--- Operating Point ---

V(a):	14.8	voltage
V(c):	29.6	voltage
V(b):	2.8	voltage
V(p001):	0	voltage
I(F1):	0.0112	device_current
I(I1):	0.002	device_current
I(R1):	0.0028	device_current
I(R2):	0.0148	device_current
I(R3):	0.0268	device_current
I(E1):	-0.0268	device_current
I(V1):	-0.026	device_current
I(Ix):	0.0028	device_current