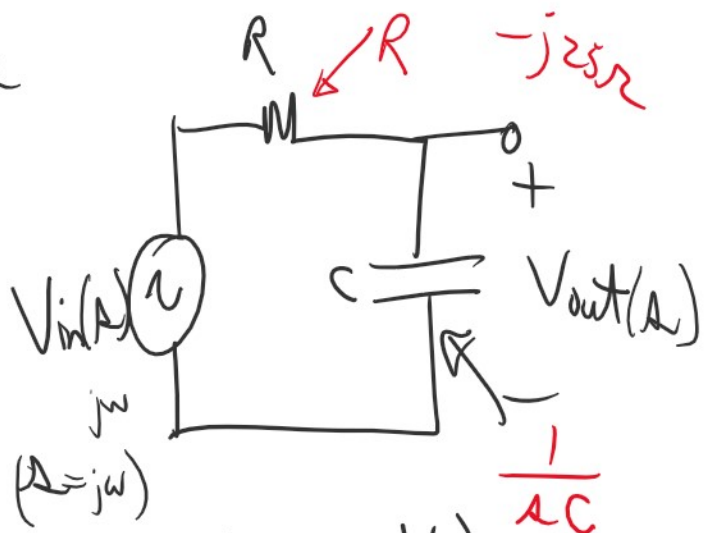


Consider the frequency response of an RC filter:



transfer function: how much of the input "transfers" to the output

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)}$$

pole/zero view

frequency response $\Rightarrow H(j\omega) = \frac{V_{out}(j\omega)}{V_{in}(j\omega)}$

what type of filter? LFF, HFF, BPF

$$\Rightarrow H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{1/sC}{1/sC + R} = \frac{1}{1 + sRC} = \frac{1}{1 + s/\omega_p}$$

\uparrow
TF

proper Bode approx form

$\omega_p = 1/RC$

Freq. response $H(j\omega) = \frac{V_{out}(j\omega)}{V_{in}(j\omega)} = \frac{1}{1 + j\omega RC}$

Suppose $V_{in}(t) = 2 \cos(10t + 20^\circ) + 10 \cos(1000t - 40^\circ) \text{ V}$

$V_{out}(t) = 2 |H(j\omega_1)| \cos(10t + 20^\circ + \angle H(j\omega_1)) + 10 |H(j\omega_2)| \cos(1000t - 40^\circ + \angle H(j\omega_2))$

$\omega_1 = 10 \text{ rad/s}$ $\omega_2 = 1000 \text{ rad/s}$

$$V_{out}(t) = 2 \underbrace{|H(j\omega_1)|}_{\substack{0 < x < 1 \\ x \geq 1}} \cos(\omega_1 t + 20^\circ - \underbrace{\angle H(j\omega_1)}_{\substack{\approx 0 \\ \Delta \phi \approx 100m}}) + \dots$$

$$\dots + 10 \underbrace{|H(j\omega_2)|}_{\substack{\Delta \phi \approx 100m}} \cos(\omega_2 t - 40^\circ + \underbrace{\angle H(j\omega_2)}_{\substack{-130^\circ}})$$

$$|H(j\omega)| = \left| \frac{1}{1 + j\omega RC} \right| = \frac{|1|}{|1 + j\omega RC|} = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

$$\angle H(j\omega) = \angle \frac{1}{1 + j\omega RC} = \underbrace{\angle(1)}_{\angle(0^\circ)} - \angle(1 + j\omega RC)$$

$$1 \angle 0^\circ$$

$$= 0^\circ - \tan^{-1}\left(\frac{\omega RC}{1}\right) = -\tan^{-1}(\omega RC)$$

$$R = 1k\Omega, C = 1\mu F$$

$$|H(j\omega_1)| = \frac{1}{\sqrt{1 + [(10)(1k)(1\mu)]^2}} \approx 999.95mV/V$$

$(\approx 1V/V) \leftarrow 0dB$

$$\angle H(j\omega_1) = -\tan^{-1}((10)(1k)(1\mu)) = -572.94mdeg$$

$(\approx 0^\circ)$

$|H|_{\omega_1} \quad |$


$$|H(j\omega_2)| = \frac{1}{\sqrt{1 + [(100k)(1k)(1\mu)]^2}}$$

$$\approx 9.9995 \text{ mV/V} (\approx 10 \text{ mV/V})$$

$$\angle H(j\omega_2) = -\tan^{-1}((100k)(1k)(1\mu))$$

$$\approx -89.4271^\circ (\approx -90^\circ)$$

$$(\approx 0^\circ)$$

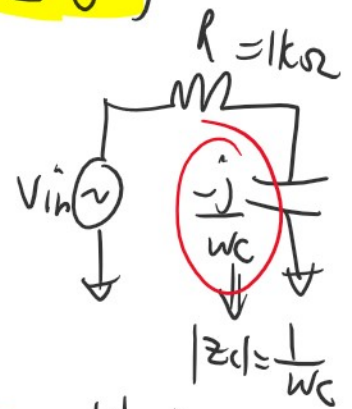

$$\omega_1 = 10 \text{ rad/s} \quad \omega_2 = 100 \text{ krad/s}$$

$$|Z_C| = 100k\Omega \quad |Z_C| = 10\Omega$$

Bode response
of an RC filter

