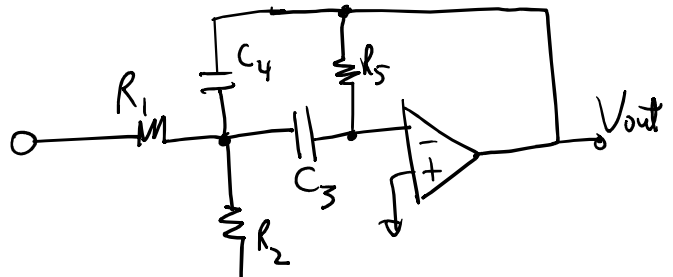


Bode Example


Derive TF (transfer function) V_{in}

$$H(\omega) = V_{out}(\omega) / V_{in}(\omega), \neq$$

Sketch Bode approximation of frequency response $H(j\omega)$



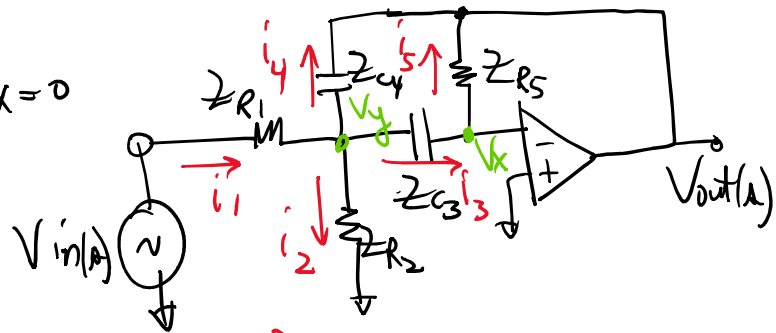Sol'n V_X is driven to ground by negative feedback $\Rightarrow V_X = 0$
 $\Rightarrow V_X$ is a virtual ground.



KCL @ V_y : $i_1 = i_2 + i_3 + i_4$

$$\Rightarrow Y_{R1}(V_{in} - V_y) = Y_{R2}V_y + Y_{C3}(V_y - V_X) + Y_{C4}(V_y - V_{out})$$

$$\Rightarrow V_y = \frac{Y_{R1}V_{in} + Y_{C4}V_{out}}{Y_{R1} + Y_{R2} + Y_{C3} + Y_{C4}} \quad (1)$$

KCL @ V_X : $i_3 = i_5 \Rightarrow Y_{C3}(V_y - V_X) = Y_{R5}(V_X - V_{out})$

$$\Rightarrow V_y = -\frac{Y_{R5}}{Y_{C3}} V_{out} \quad (2) \Rightarrow \text{Now set the RHSs of (1) \& (2) equal to eliminate } V_y$$

$$\Rightarrow \frac{Y_{R1}V_{in} + Y_{C4}V_{out}}{Y_{R1} + Y_{R2} + Y_{C3} + Y_{C4}} \stackrel{\text{set}}{=} -\frac{Y_{R5}}{Y_{C3}} V_{out} \rightarrow \text{do some algebra ... \& get } \frac{V_{out}(\omega)}{V_{in}(\omega)} = H(\omega)$$

$$\Rightarrow H(\omega) = \frac{V_{out}(\omega)}{V_{in}(\omega)} = \frac{-\omega \left(\frac{1}{R_1 C_4} \right)}{\omega^2 + \omega \left(\frac{C_3 + C_4}{R_1} \right) + \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_5} \right)} \quad (3)$$

$$V_{in}(A) \frac{1}{A^2 + A \left(\frac{C_3 + C_4}{R_5 C_3 C_4} \right) + \left(\frac{G_1 + G_2}{R_5 C_3 C_4} \right)} \quad (5)$$

This $H(A)$ has the form

$$H(A) = \frac{-\alpha \omega_0 A}{A^2 + 2 \frac{1}{Q} \omega_0 A + \omega_0^2} \quad \text{OR} \quad \frac{-\alpha \omega_0 A}{A^2 + \frac{\omega_0}{Q} A + \omega_0^2}$$

where $\alpha \omega_0 = \frac{1}{R_5 C_3 C_4}$ *Recall that $Q = \frac{1}{2\zeta}$*

Compare

\Rightarrow Note that $H(A)$ is not yet in proper Bode approximation form.
(more soon.)
What kind of filter is this?

① $\lim_{A \rightarrow 0} H(A) = 0 \leftarrow$ attenuates low frequencies, so this can't be a LPF or BSF

② $\lim_{A \rightarrow \infty} H(A) = \frac{1}{A} = 0 \leftarrow$ attenuates high frequencies as well, so this can't be a HPF, either

\rightarrow this must be a BPF

Now, let's put $H(A)$ into proper Bode form:

$$H(A) = \frac{-\alpha \omega_0 A}{A^2 + 2 \frac{1}{Q} \omega_0 A + \omega_0^2} = \frac{-\alpha \omega_0 A}{A^2 + \frac{\omega_0}{Q} A + \omega_0^2}$$

Factor ω_0^2 out of denominator:

$$\Rightarrow H(A) = \frac{-(\alpha \cancel{\omega_0} / \cancel{\omega_0^2}) A}{(\cancel{A} / \omega_0)^2 + 2 \frac{1}{Q} (\cancel{A} / \omega_0) + 1} = \frac{-\left[\frac{A}{(\omega_0 / \alpha)} \right]}{\left(\frac{A}{\omega_0} \right)^2 + 2 \frac{1}{Q} \left(\frac{A}{\omega_0} \right) + 1}$$

Suppose $R_1 = 49k\Omega$, $R_2 = 1k\Omega$, $R_5 = 98k\Omega$, $C_3 = C_4 = 427.3763 \text{ pF}$

From (3) above,

$$\rightarrow \omega_0 = \sqrt{\frac{G_1 + G_2}{R_5 C_3 C_4}} \approx \underbrace{238.7611 \text{ krps}}_{\omega_0} \left(\approx 2\pi \underbrace{(38 \text{ kHz})}_{f_0} \right)$$

$$\rightarrow \alpha \omega_0 = \frac{1}{R_1 C_4} \Rightarrow \alpha = \frac{(1/R_1 C_4)}{\omega_0} = G_1 \sqrt{\frac{R_5 C_3}{C_4 (G_1 + G_2)}}$$

$$\rightarrow \underbrace{\omega_0 / \alpha}_{\substack{\uparrow \\ \text{0dB Crossing} \\ \text{frequency of} \\ \text{Zero @ } \omega_c \text{ term}}} = \frac{\sqrt{\frac{G_1 + G_2}{R_5 C_3 C_4}}}{G_1 \sqrt{\frac{R_5 C_3}{C_4 (G_1 + G_2)}}} = \frac{R_1 (G_1 + G_2)}{R_5 C_3} = \frac{1 + R_1/R_2}{R_5 C_3}$$

$$\Rightarrow \omega_0 / \alpha \approx 1.1938 \text{ Mrps} (= 2\pi (190 \text{ kHz}))$$


$$\rightarrow Q = \frac{1}{2\zeta} = \frac{\sqrt{\frac{(G_1 + G_2)}{R_5 C_3 C_4}}}{\left(\frac{C_3 + C_4}{R_5 C_3 C_4} \right)} = \frac{\sqrt{(G_1 + G_2) R_5 C_3 C_4}}{C_3 + C_4}$$

$$\Rightarrow Q = 5 \quad \& \quad \zeta = \frac{1}{2Q} = 0.1$$

underdamped!


Let's sketch the underdamped denominator term first:

1.1 dB

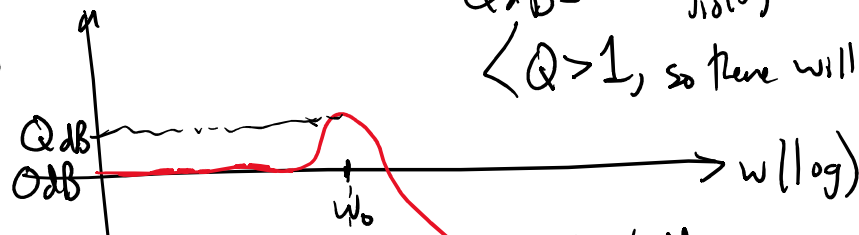

$$Q_{dB} = 20 \log_{10}(5) \approx 13.98 \text{ dB}$$

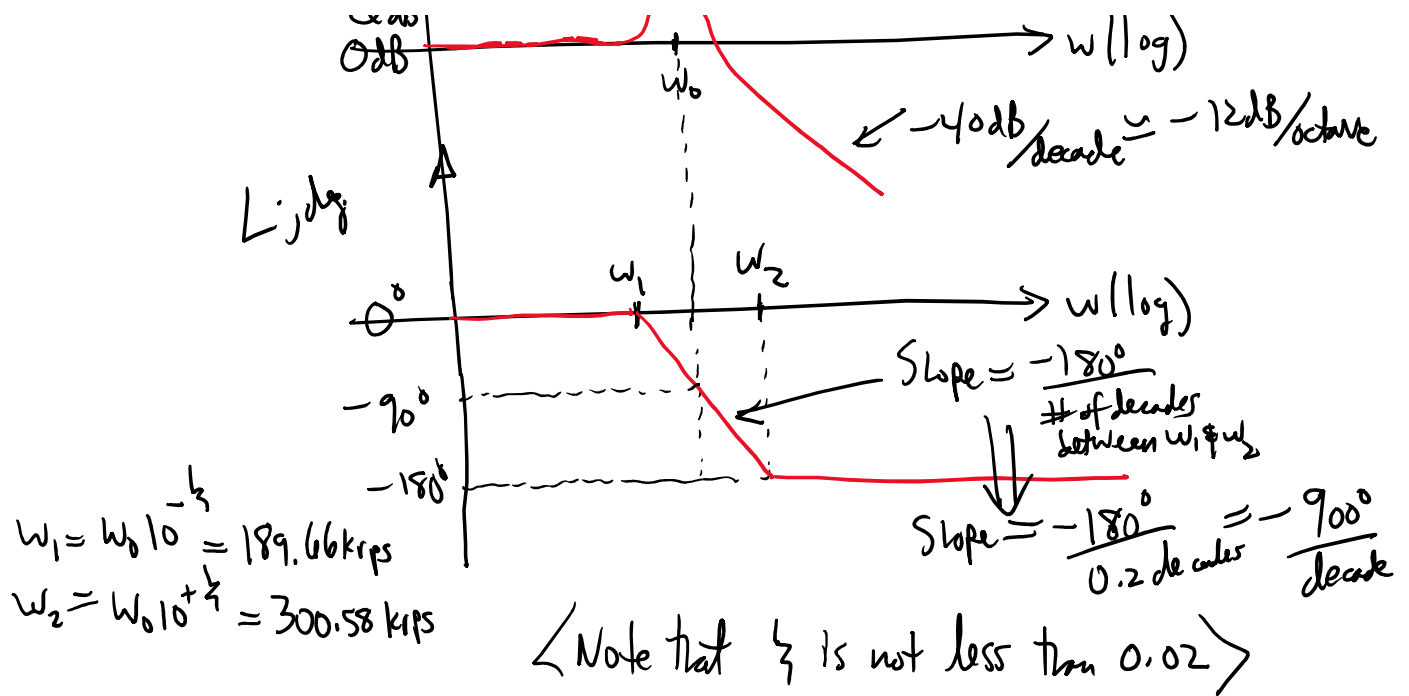$\langle Q > 1$, so there will be gain peaking



⇒ Now let's sketch the zero @ DC term: ← I'll also include the phase due to the minus sign of $H(s)$ here, too.

