

One more eqn:

$$\alpha = G_1 \sqrt{\frac{R_5 C_3}{C_4 (G_1 + G_2)}}$$

$$A_0 = \alpha Q$$

$$K = 1 \angle \pm 180^\circ$$


what, f? (K > 1)

zero @ DC w/ 0dB crossing @ $\omega_0/2$

$$H(s) =$$

$$\frac{-K(\omega/\omega_0)}{\{(\omega/\omega_0)^2 + \frac{1}{Q}(\omega/\omega_0) + 1\}}$$

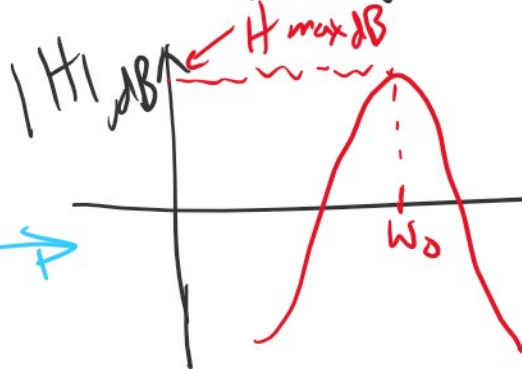for the given component values, this has complex conjugate pair roots.



$Q > 1$ (?) maybe

resonance

What, exactly, is Q, & what can I determine about this from the freq. response?


quality factor

$$Q = \frac{1}{2\zeta}$$




$$Q = \frac{F_c}{\Delta f_{3dB}}$$

Recall


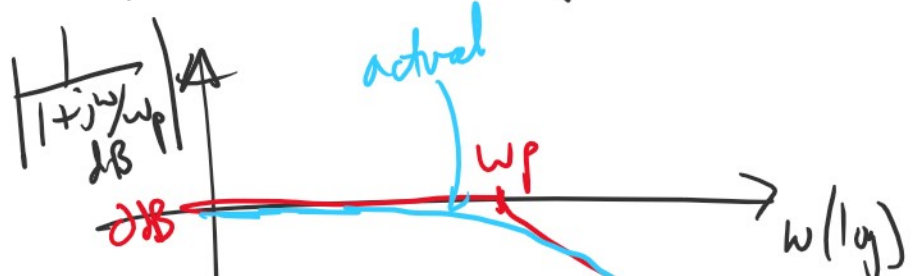


Recall
pole term
(zero term)

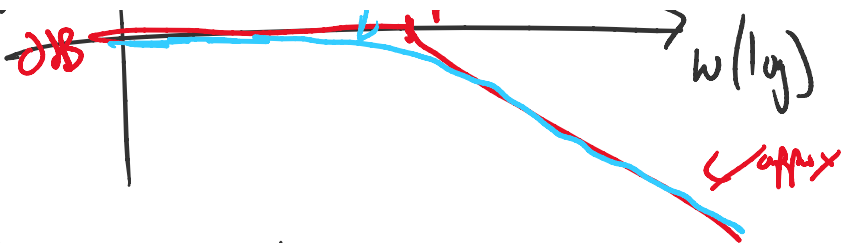


$$\left| \frac{1}{1 + j\omega/\omega_p} \right| = \frac{1}{|1 + j|} = \frac{1}{\sqrt{1^2 + 1^2}} = \frac{1}{\sqrt{2}}$$
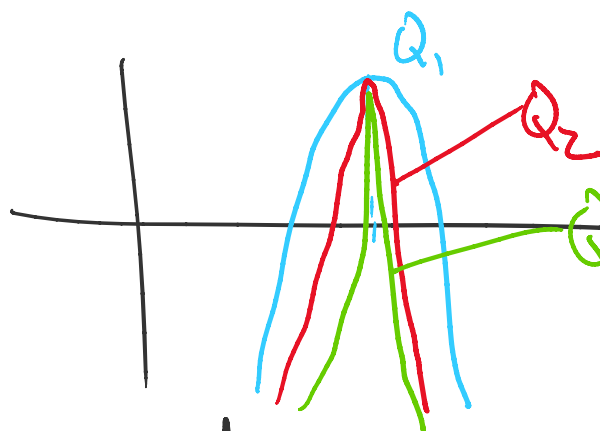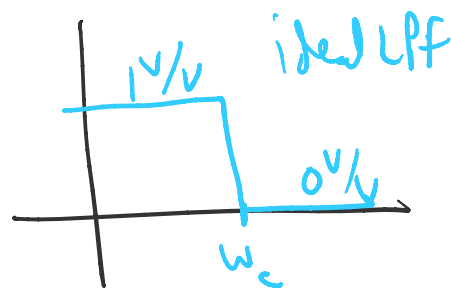
$$20 \log_{10} \left(\frac{1}{\sqrt{2}} \right) \approx -3 \text{ dB}$$



$Q_3 > Q_2 > Q_1$

selective

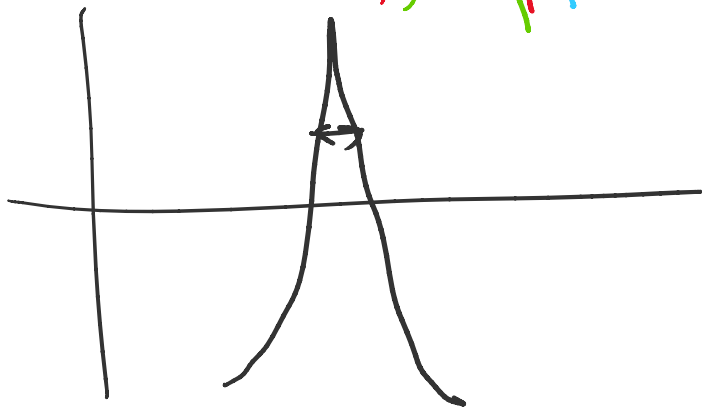

$$H(j\omega) = \frac{V_{out}(j\omega)}{V_{in}(j\omega)}$$

① 1/0°