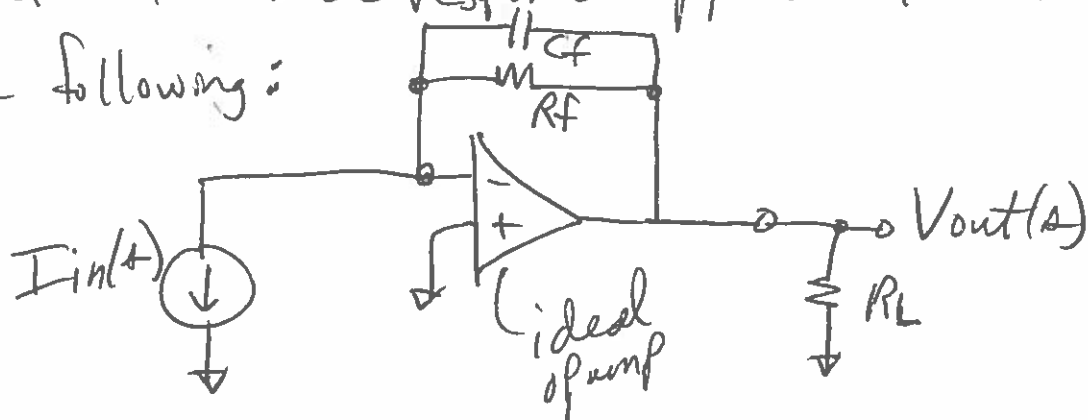


(Yet Another) Bode Example:

1

Sketch the Bode response approximation of the following:



→ Define transfer function $H(s)$ as ratio of output voltage $V_{out}(s)$ to input current $I_{in}(s)$:

$$H(s) = \frac{V_{out}(s)}{I_{in}(s)} \Rightarrow \text{Note that } V_{out}(s) = \underline{Z_f(s) I_{in}(s)}$$

$$\begin{aligned} \text{So, } H(s) &= Z_f(s) = R_f \parallel \left(\frac{1}{sC_f} \right) \\ &= \frac{R_f \left(\frac{1}{sC_f} \right)}{R_f + \frac{1}{sC_f}} = \frac{R_f}{1 + sR_fC_f} = \frac{R_f}{\left(1 + s/\omega_{p1} \right)} \end{aligned}$$

$$\Rightarrow H(s) = \frac{K}{\left(1 + s/\omega_{p1} \right)}, \quad K = R_f, \quad \omega_{p1} = \frac{1}{R_fC_f}$$

What does the Bode response approximation of this ckt look like? (cont'd) →


→ Let $R_f = 1k\Omega$, $C_f = 10pF$. Then

2/

$$K = R_f = 1k\Omega \Rightarrow K_{dB} = 20\log_{10}(1k) = 60dB, \text{ and}$$

$$\omega_{p1} = \frac{1}{R_f C_f} = \frac{1}{(1k)(10p)} = 100Mrps \approx 2\pi(15.92MHz)$$

→ The Bode approximation looks like:

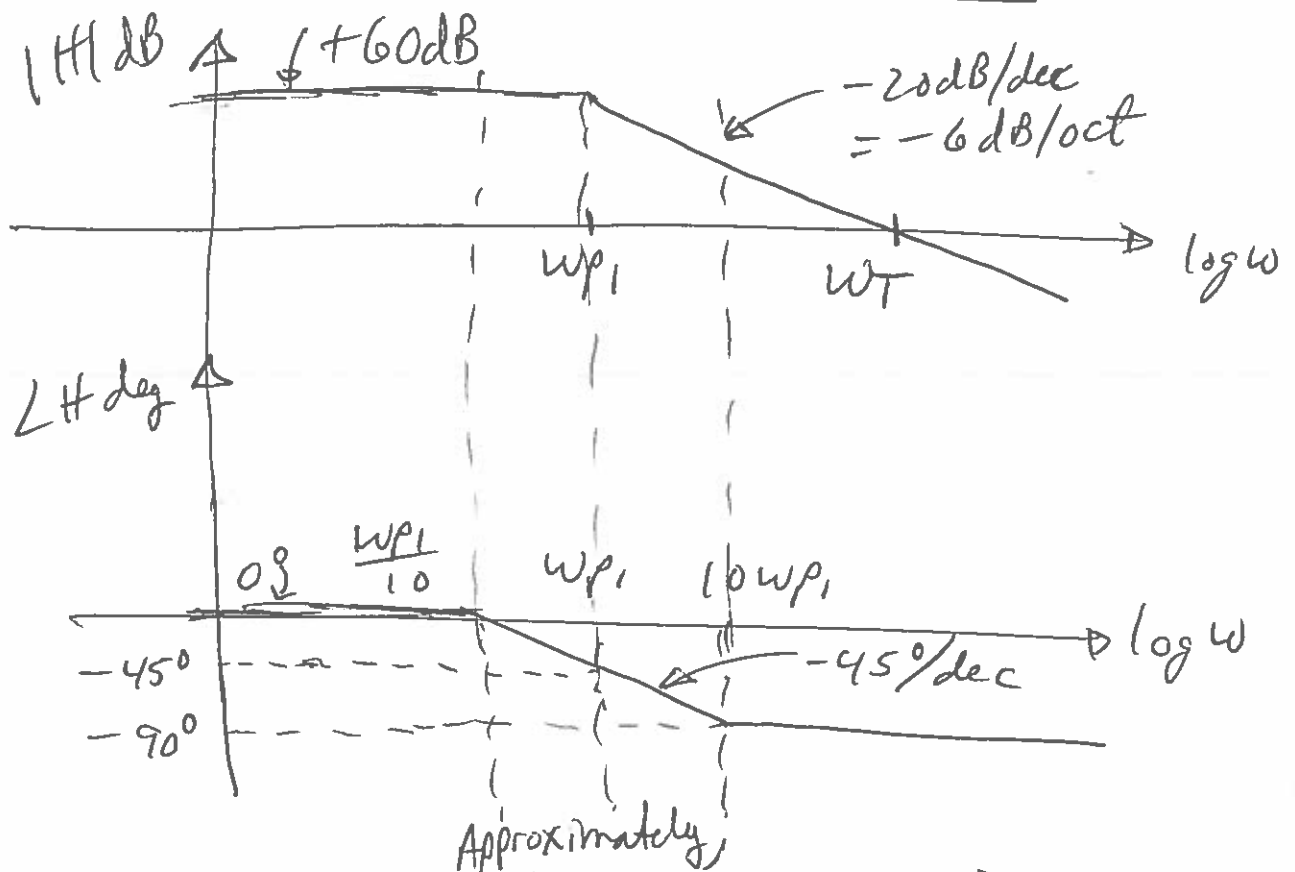

→ Additional question: What is ω_T ?

Here, ω_T is defined as the frequency at which $|H(j\omega)|$ falls to $0dB$, approximately.

$$\begin{aligned} \text{(Answer: } \omega_T &\approx 3 \text{ decades higher than } \omega_{p1}) \\ &= 10^3 \omega_{p1} = 100Grps \end{aligned}$$