


Response of 1st-order RL & RC ckt <Chpt. 7>

49

Natural response of RL ckt ("Natural response" means source is removed)

Consider the following ckt \Rightarrow

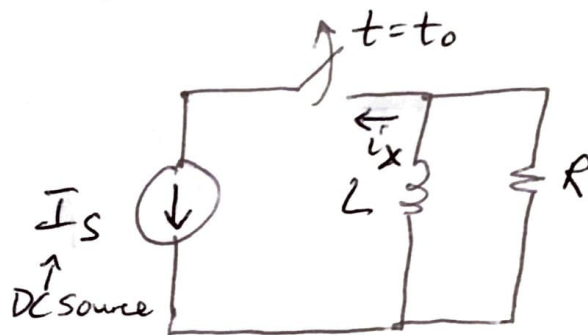Suppose that, prior to opening the switch at time t_0 , the ckt was in the shown state for a very long time.




For the $t \ll t_0$ ckt, we have

$$V_R = V_L = V \text{ (R \& L are in parallel)}$$

$$\Rightarrow V_R = V = R i_R \text{ \& } V_L = V = L \frac{di_L}{dt}$$

$t \ll t_0$ ckt \Rightarrow

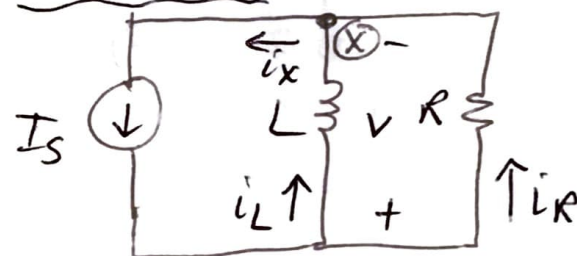

\Rightarrow Since ~~the~~ ckt was in shown state for a very long time & I_S is a DC source, we have that $\frac{di_L}{dt} = 0 \leftarrow$ The inductor current is not changing wrt time anymore


\Rightarrow Since $\frac{di_L}{dt} = 0$, we have that $V = L \frac{di_L}{dt} = 0$

\Rightarrow Since $V = 0$, $V_R = V = R i_R = 0 \Rightarrow i_R = V/R = 0/R = 0$

\Rightarrow KCL @ node (X) says that $i_L + i_R = i_x = I_S$, & since $i_R = 0$, we have that $i_L + i_R = I_S \Rightarrow i_L = I_S$


$$\boxed{i_R = 0 \text{ \& } i_L = I_S}$$

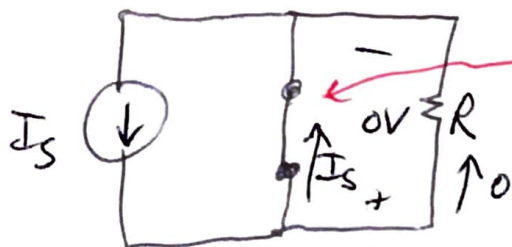\Rightarrow Key takeaway: Inductor "looks like" a short after a very long time in a DC ckt, i.e., we can model the $t \ll t_0$ ckt as



inductor modeled as a short in the DC steady-state ckt at $t \ll t_0$.

Now, let's open the switch at t_0 :

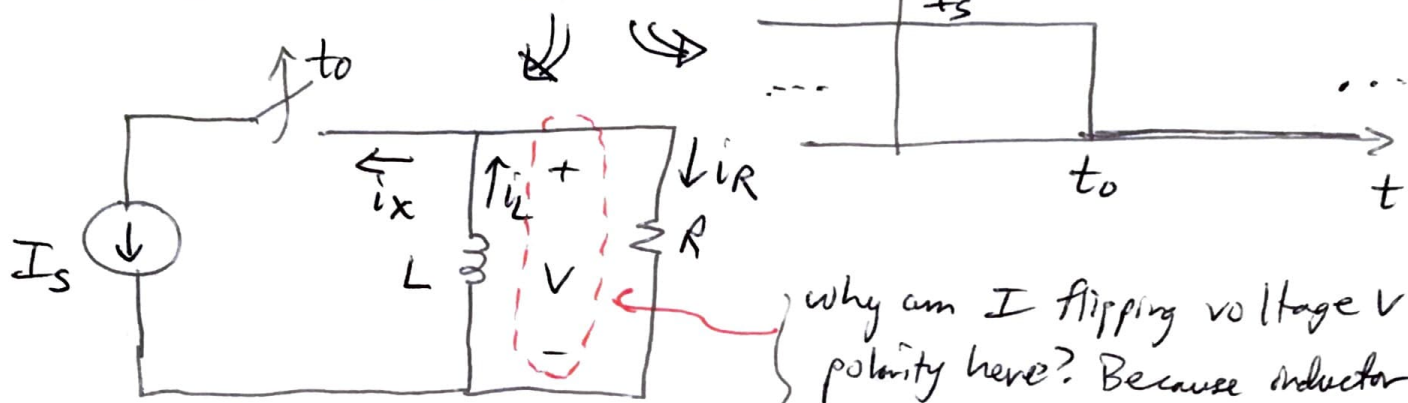

why am I flipping voltage V polarity here? Because inductor is releasing energy to the ckt after switch is opened up.


Side note

⇒ When ^{DC} inputs of 1st order RC & RL ckt (& 2nd-order RLC ckt in Chpt. 8) are removed from a ckt, we call the resulting response the "natural response"

⇒ Conversely, when DC inputs are applied, we call the resulting response the "step response"

OK, here's the ckt after the switch is opened

$i_L = i_R$; what is i_L ?

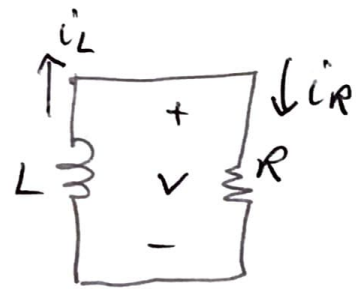

First, some notation: (1) $i_L(t_0^-)$ means the current in the inductor just before the switch is opened (or closed, or whatever); (2) $i_L(t_0^+)$ means the current in the inductor just after the switch is opened (or closed, or whatever); (3) $i_L(\infty)$ means the current in the inductor after a very long time has passed since the switch was opened (or closed, or whatever).

⇒ Now, $i_L(t_0^-) = I_s$ (from previous analysis, right before switch was opened)


$i_L(t_0^+) = ?$ ⇒ $V = L \frac{di_L}{dt}$ ← for $\frac{di_L}{dt}$ to exist, i_L cannot change in value instantaneously from time t_0^- to time t_0^+

⇒ So, we have that current in an inductor cannot change instantaneously and that $i_L(t_0^+) = i_L(t_0^-) = I_s$

⇒ At $t = t_0^+$, we can model the inductor as a constant current source ⇒ circuit model at $t = t_0^+$

What is $v(t_0^+)$? What is $v(t_0^-)$?

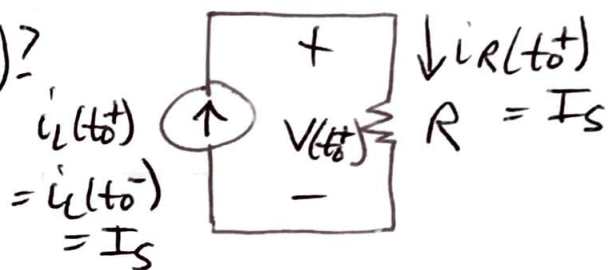
From previous analysis, $v(t_0^-) = 0$
 & from ckt to the right, we have that $v(t_0^+) = RI_S$



⇒ Now, what happens when ckt with switch opened stays in that state for a very long time? (i.e., as $t \rightarrow \infty$)

$$\Rightarrow \frac{di_L}{dt} = 0, v(\infty) = L \frac{di_L}{dt} = 0$$
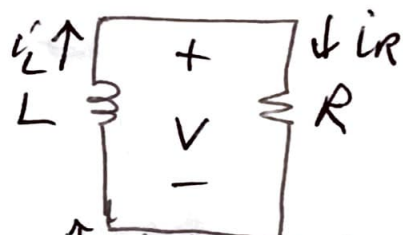
$$i_R(\infty) = \frac{v(\infty)}{R} = 0, \text{ \& by KCL } i_L = i_R = 0$$



↑ inductor looks like a short

So, we know the details of ckt response @ times

t_0^- , t_0^+ , and $t \rightarrow \infty$. How do we determine, say, $i_L(t)$

for time values between t_0^+ & $t \rightarrow \infty$? ⇒ ^{solve} Differential equation:

At $t \geq t_0^+$, $i_L = i_R = i \dots$ let's

analyze the $t \geq t_0^+$ ckt:

KVL around the loop ⇒ $V_L + V_R = 0$

$$\Rightarrow L \frac{di}{dt} + Ri = 0 \quad (1)$$

$$\Rightarrow L \frac{di}{dt} = -Ri \Rightarrow \frac{L di}{i} = -R dt$$

$$\Rightarrow \frac{di}{i} = -\frac{R}{L} dt \Rightarrow \int_{i(t_0)}^{i(t)} \frac{dx}{x} = -\frac{R}{L} \int_{t_0}^t dr \Rightarrow \ln \left[\frac{i(t)}{i(t_0)} \right] = -\frac{R}{L} [t - t_0]$$


$$\Rightarrow i(t) = i(t_0) \exp[-(t - t_0)/\tau], t \geq t_0^+, \tau = \frac{L}{R} \equiv \text{time constant for RL ckt}$$



Note that (1) does not contain any derivative terms higher than first-order, which is why we say that this is a first-order RL ckt

So, $i_L(t)$ can be graphed as follows:

52

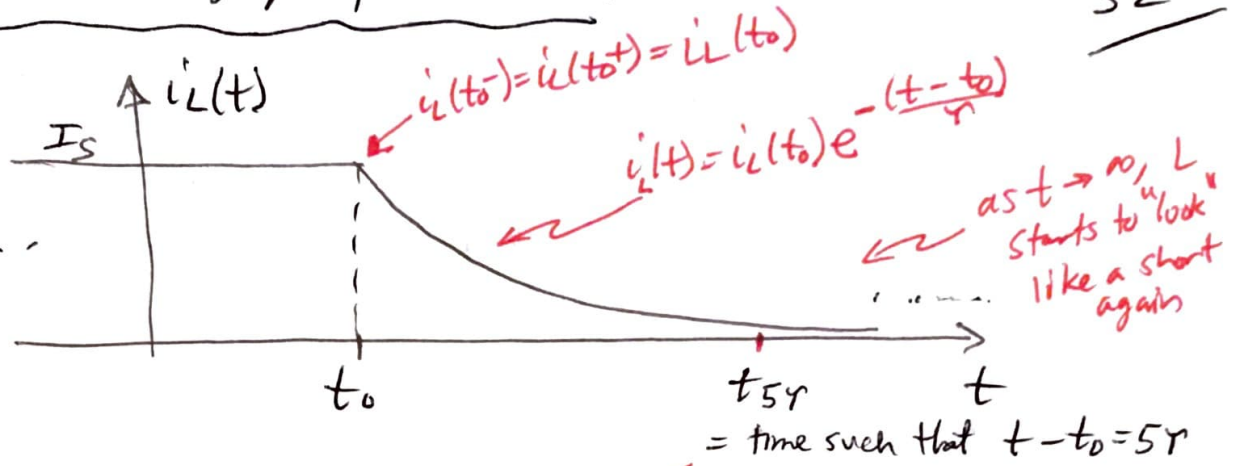

\Rightarrow time constant $\tau = \frac{L}{R}$ [sec] tells us how "fast" or "slow"

The exponential decay happens

\Rightarrow "low" τ , "fast" decay

\Rightarrow "high" τ , "slow" decay

Can also get $V(t) = L \frac{di_L}{dt} = R i_L(t)$

$\Rightarrow V(t) = R i_L(t_0) \exp\left[-\frac{(t-t_0)}{\tau}\right]$


\Rightarrow Rule of Thumb: A natural/step response will decay to \approx the final/steady-state value in 5τ ($5\tau = 5$ time constants)

What about the natural response of an RC ckt?

① $t < t_0$ ckt \Rightarrow

$\left\langle \frac{dV_C}{dt} = 0 \right\rangle$


$i_C(t_0^-) = 0, i_R(t_0^-) = V_S/R$

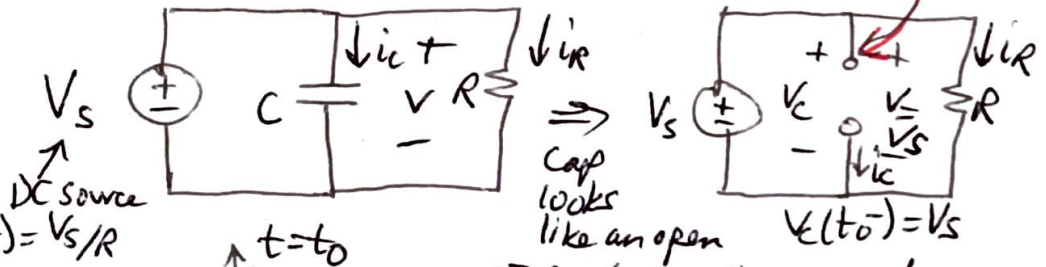

② $t = t_0^+$ ckt \Rightarrow




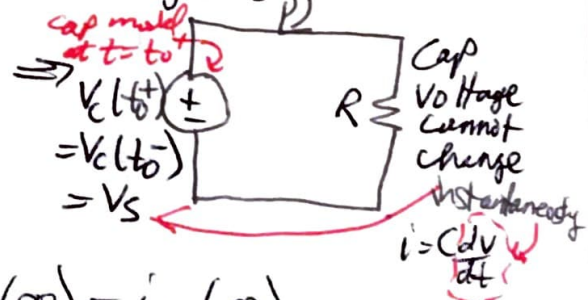\Rightarrow Constant Voltage Source cut switching time



③ $t \rightarrow \infty$ ckt \Rightarrow

$\frac{dV_C}{dt} = 0 \Rightarrow$

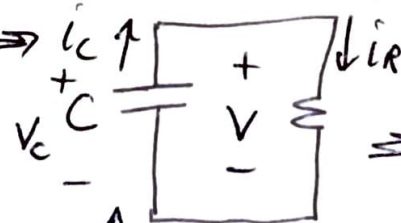

$\Rightarrow i_C(\infty) = i_R(\infty) = 0$


$\& V(\infty) = 0$

cap looks like an open

④ For time $t > t_0$: Derive & solve differential equation 53


KCL @ (X): $i_C + i_R = 0$

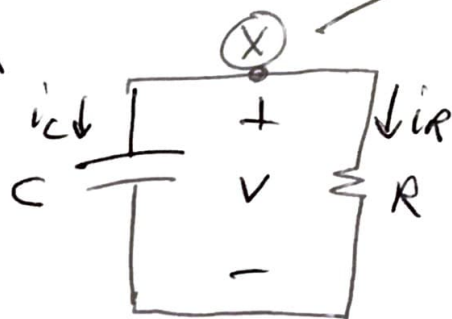$\Rightarrow C \frac{dv}{dt} + \frac{v}{R} = 0$





Solve $\Rightarrow V(t) = V(t_0) \exp[-(t-t_0)/\tau]$, $t \geq t_0$, $\tau = RC$

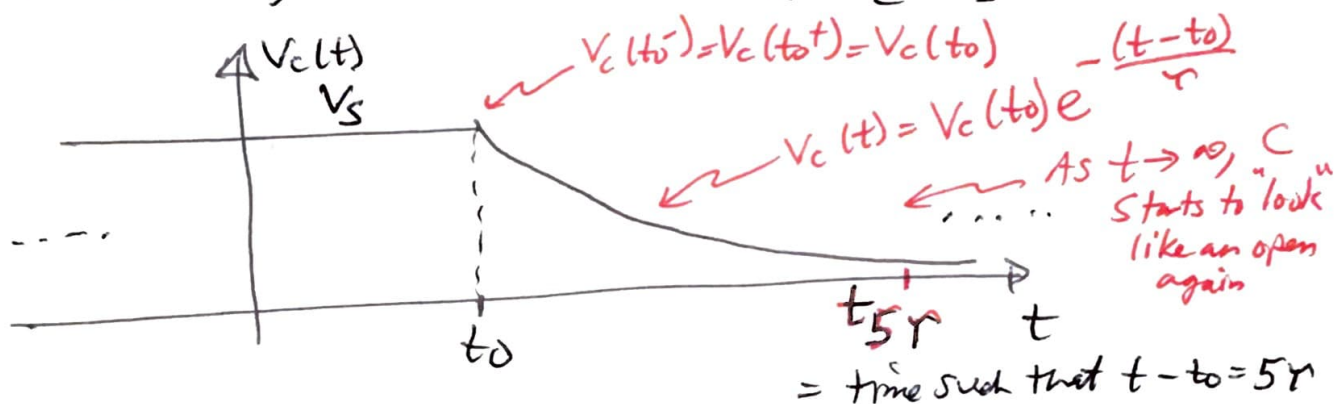\Rightarrow For RC ckt, time constant $\tau = RC$ [sec]



(Can also get $i_R(t) = C \frac{dv}{dt} = \frac{v_C(t)}{R} = \frac{V_C(t_0)}{R} \exp\left[-\frac{(t-t_0-t_0)}{\tau}\right]$, $t > t_0$)

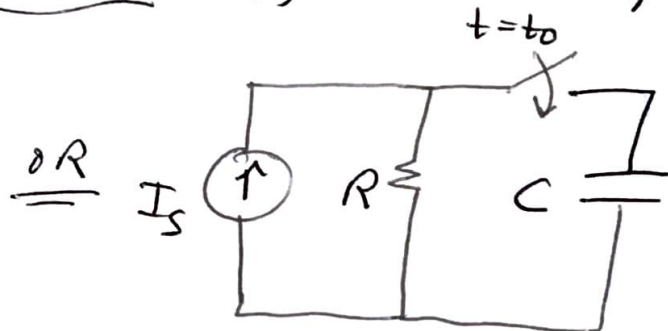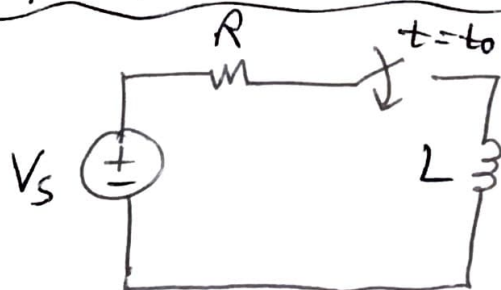Step response of RC or RL ckt: e.g., ckt of this type



How to solve? Rather than treating these as a special case, let's discuss the general approach for finding either the natural response OR the step response of an RC OR RL ckt.

② General form of solution 54

$$\Rightarrow x(t) = x(\infty) + [x(t_0^+) - x(\infty)] e^{-\left[\frac{t-t_0}{\tau}\right]}$$

where $x(t)$ is the current or voltage of interest.

① Pick x : For RC ckt, convenient to choose cap voltage.
For RL ckt, convenient to choose inductor current.
 \Rightarrow Determine $x(t_0^-)$


② Determine $x(t_0^+)$, i.e., initial value

③ Determine $x(\infty)$, i.e., final value

④ Determine time constant τ $\Rightarrow \tau = \frac{L}{R_{eq}}$ for RL ckt

& $\tau = R_{eq}C$ for RC ckt, where R_{eq} is the equivalent resistance "seen" by L or C.

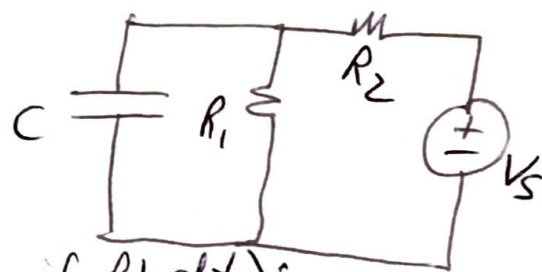
Req? Consider the following example: Suppose this is the ckt you want to analyze after switch has been closed/open to determine time constant τ :



\Rightarrow Deactivate independent source(s),
& determine resistance "seen" by C (or L, if RL ckt):

$\Rightarrow R_{eq} = R_1 \parallel R_2$, so

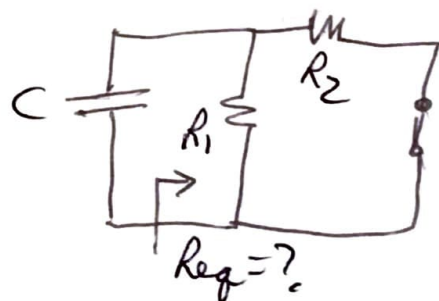
$$\tau = R_{eq}C = (R_1 \parallel R_2)C$$



Note if the deactivated ckt for determining τ contains dependent source(s), then you need to remove C (or L) & replace with test source & compute $R_{eq} = V_T / I_T$.

Example¹ for HW 12 | ELEN 2425

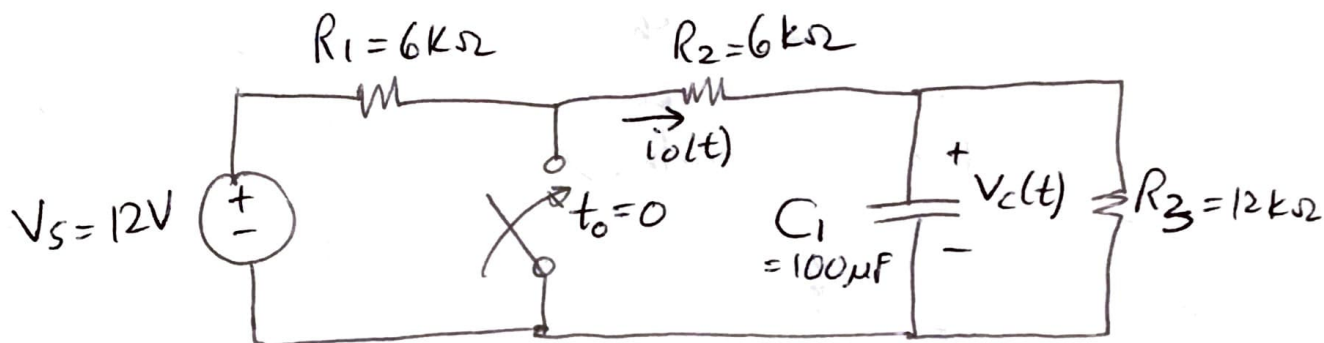In the following circuit, find $i_o(t)$ and $v_c(t)$ for $t > 0$.




We know that $i_o(t)$ & $v_c(t)$ have the following forms:

$$i_o(t) = i_o(\infty) + [i_o(t_0^+) - i_o(\infty)]e^{-(t-t_0)/\tau}, \quad t > 0 \quad (1)$$

$$\text{and } v_c(t) = v_c(\infty) + [v_c(t_0^+) - v_c(\infty)]e^{-(t-t_0)/\tau}, \quad t \geq 0 \quad (2)$$

⇒ Note that (1) is only valid for $t > 0$, and that (2) is valid for $t \geq 0$ (why? look in your notes from class).

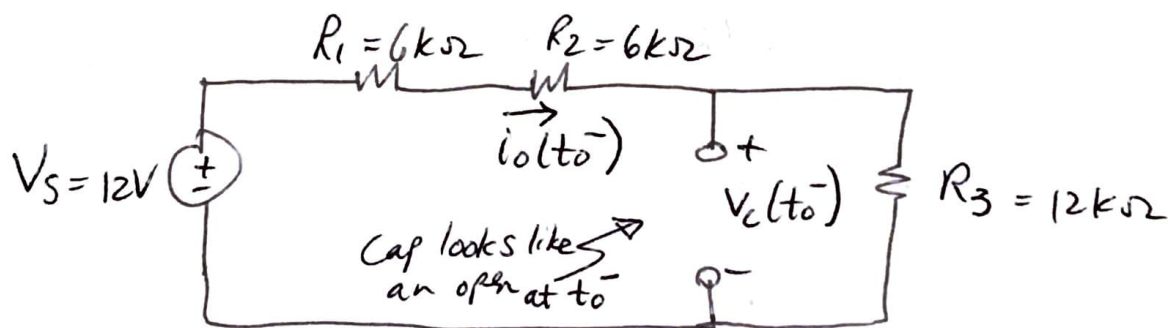① Analyze the above circuit at $t = t_0^-$:




$$\text{Thus } i_o(t_0^-) = \frac{V_S}{R_1 + R_2 + R_3} = 500 \mu\text{A}, \text{ and}$$

$$v_c(t_0^-) = \left(\frac{R_3}{R_1 + R_2 + R_3} \right) V_S = 6\text{V}$$


cont'd

II Analyze the circuit at $t = t_0^+$:

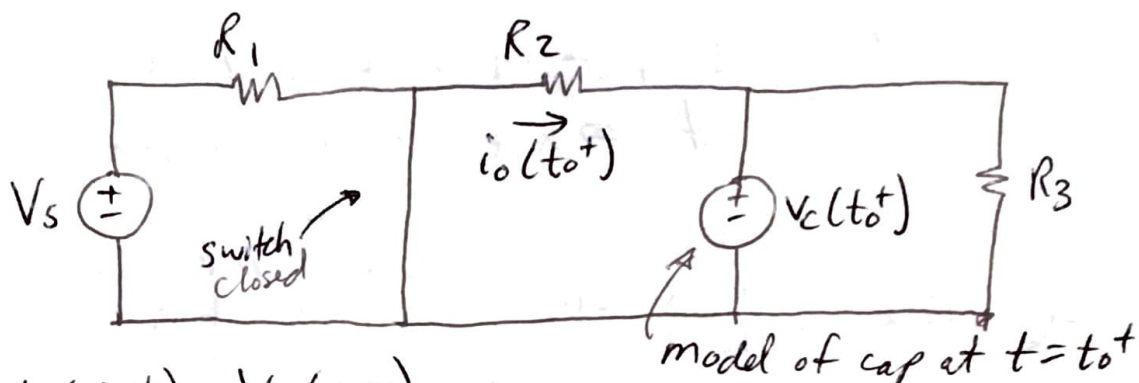


→ $V_c(t_0^+) = V_c(t_0^-)$, since cap voltage cannot change instantaneously. $\Rightarrow V_c(t_0^+) = V_c(t_0^-) = 6V$,

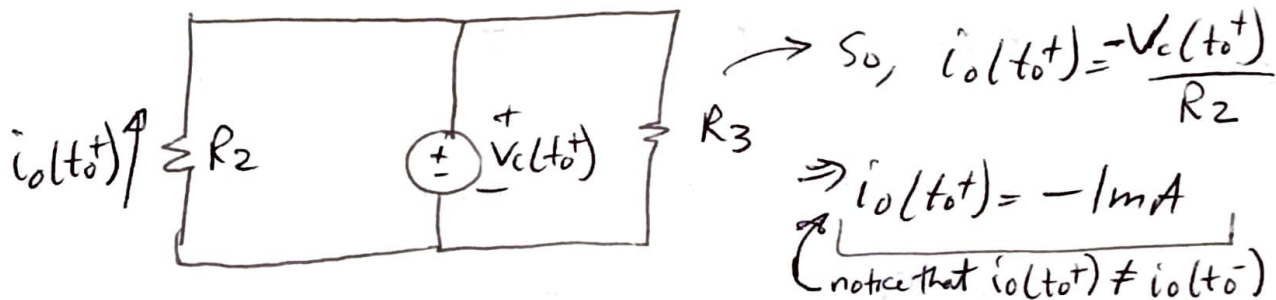→ $i_o(t_0^+) = ?$ Let's redraw the circuit, removing those parts that do not affect operation anymore:



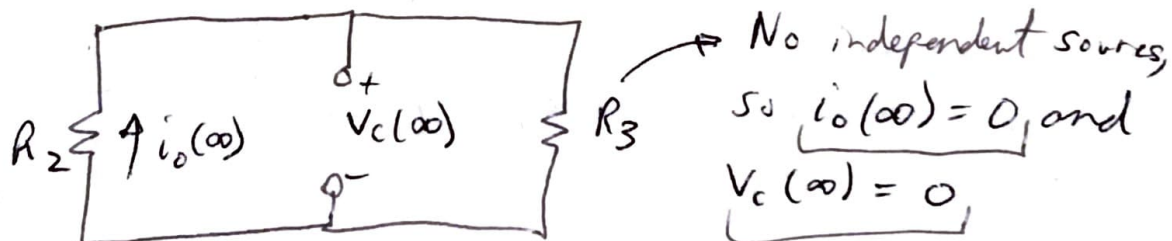III Analyze the circuit for $t > t_0^+$ to find values as $t \rightarrow \infty$:




Cont'd



Find τ :

$\tau = R_{eq} C_1$, what is R_{eq} ?

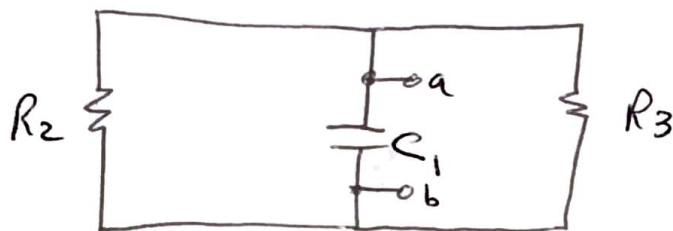

R_{eq} is the equivalent resistance ^{seen} by the capacitor, or, equivalently, at terminals a & b. [Note, that if the circuit had sources, you would need to handle those the way you would in doing a Thevenin/Norton equivalent resistance calculation.]

$$\Rightarrow R_{eq} = R_2 \parallel R_3 = 6k \parallel 12k = 4k\Omega,$$

$$\tau = R_{eq} C_1 = (4k\Omega)(100\mu F) = 400ms$$

(also note that $1/\tau = 2.5s^{-1}$)

So, $t_0 = 0s$ and


$$\begin{aligned} V_c(t) &= 6e^{-2.5t} \text{ V}, \quad t \geq 0, \text{ and} \\ i_o(t) &= -e^{-2.5t} \text{ mA}, \quad t > 0 \end{aligned}$$

Example 2 starts on the next page

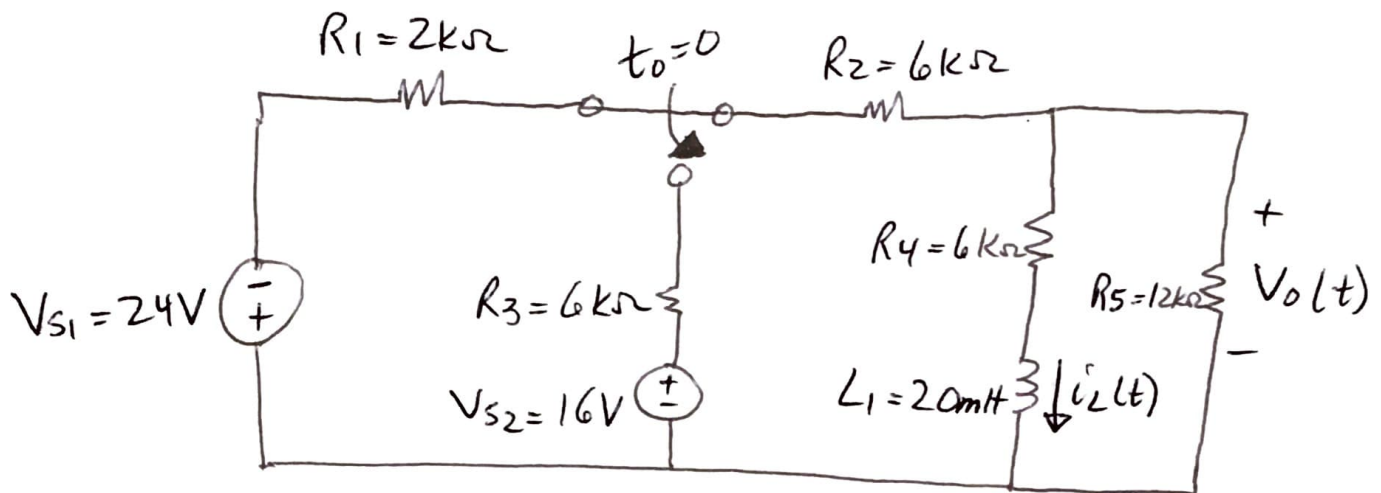Example 2 for Hw12

ELEN 2425

In the following circuit, find $i_L(t)$ and $V_o(t)$ for $t > 0$.




We know that $i_L(t)$ and $V_o(t)$ have the following forms:

$$i_L(t) = i_L(\infty) + [i_L(t_0^+) - i_L(\infty)]e^{-[t-t_0]/\tau}, t \geq 0 \quad (1)$$

$$V_o(t) = V_o(\infty) + [V_o(t_0^+) - V_o(\infty)]e^{-[t-t_0]/\tau}, t > 0 \quad (2)$$


\Rightarrow Note that (2) is only valid for $t > 0$, while (1) is valid for $t \geq 0$ (why? review your notes from class).

I Analyze $t = t_0^-$ circuit:

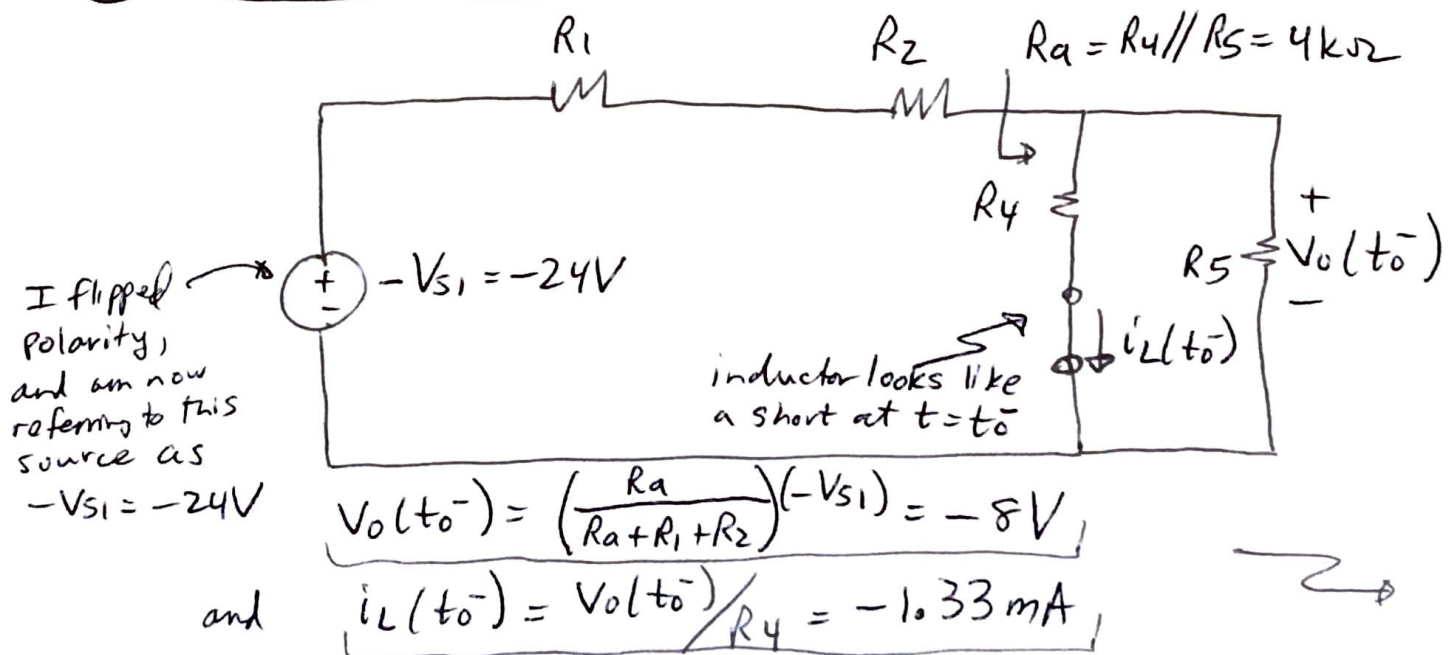


cont'd

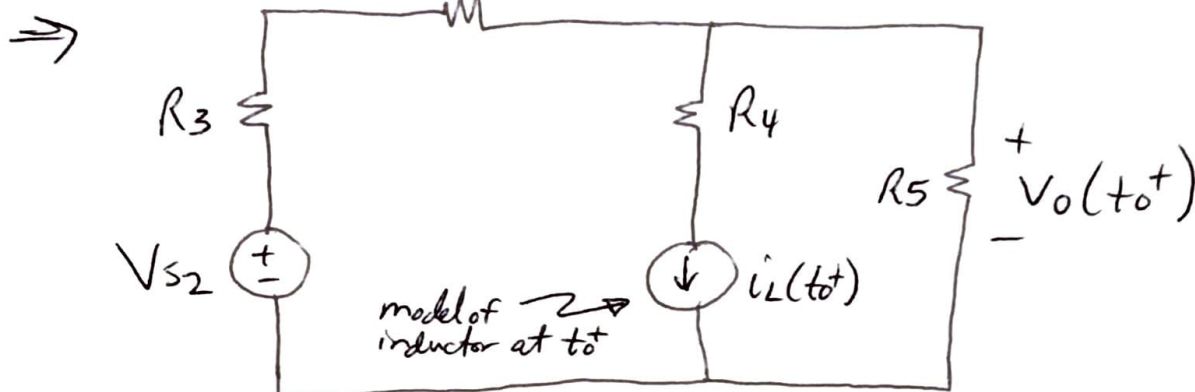II Analyze $t = t_0^+$ circuit: V_{S1} and R_1 are effectively removed at t_0^+



→ $i_L(t_0^+) = i_L(t_0^-)$, since inductor current cannot change instantaneously ⇒ $i_L(t_0^+) = i_L(t_0^-) = -1.33\text{mA}$

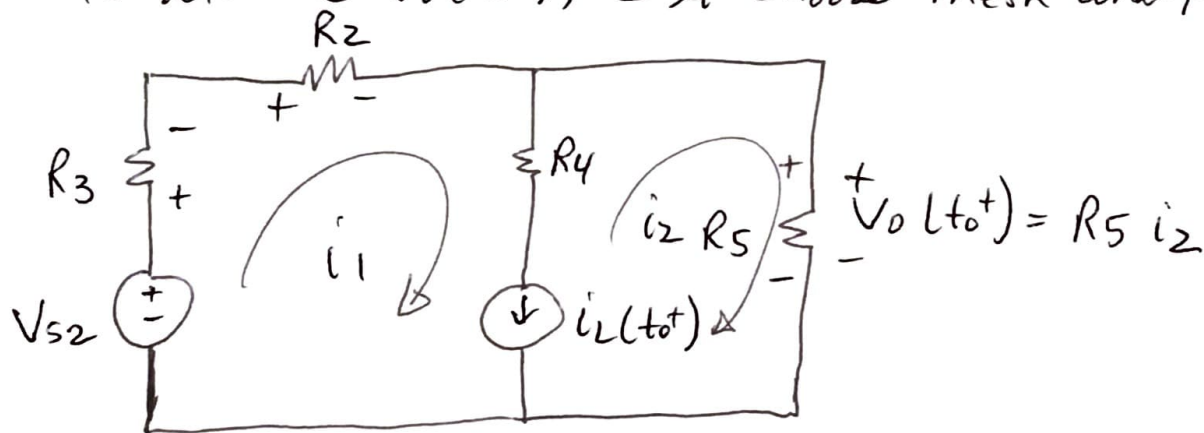→ $V_0(t_0^+) = ?$ We can choose mesh or nodal analysis to determine $V_0(t_0^+)$; I'll choose mesh analysis:



→ $i_1 - i_2 = i_L(t_0^+) = -1.33\text{mA}$ (3)

→ KVL, supermesh: $-V_{S2} + R_3 i_1 + R_2 i_1 + R_5 i_2 = 0$

⇒ $(R_2 + R_3) i_1 + R_5 i_2 = V_{S2}$ (4)


Solving (3) & (4) yields $i_1 = 0$, $i_2 = 1.33\text{mA}$, and so

$V_0(t_0^+) = R_5 i_2 = 16\text{V}$

cont'd

III

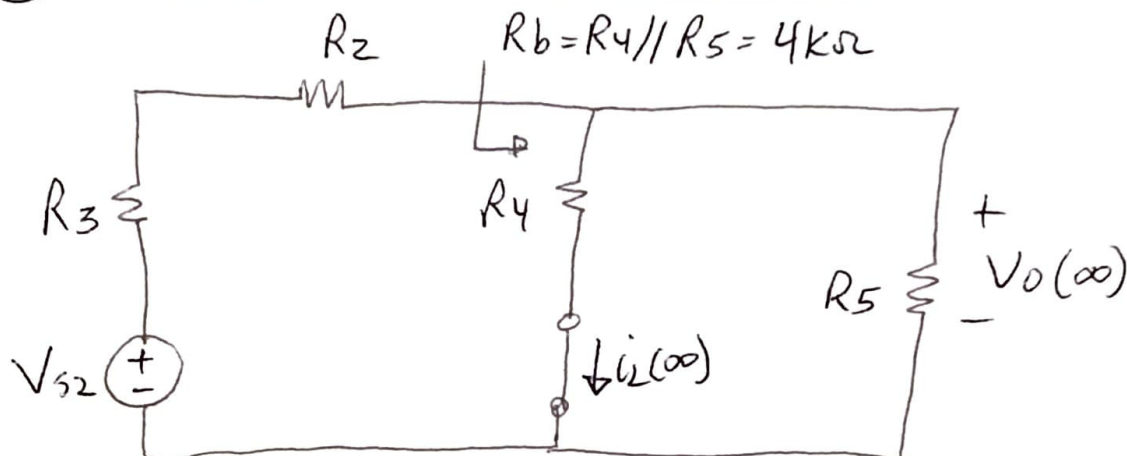Analyze $t > t_0^+$ circuit to find values as $t \rightarrow \infty$:



$$\Rightarrow V_o(\infty) = \left(\frac{R_b}{R_b + R_3 + R_2} \right) V_{s2} = 4V \quad \text{and} \quad i_L(\infty) = \frac{V_o(\infty)}{R_4} = 666.67 \mu A$$



IV

Find τ :

$$\tau = \frac{L_1}{R_{eq}}$$

, what is R_{eq} ? R_{eq} is the equivalent resistance seen by L_1

Deactivate independent sources

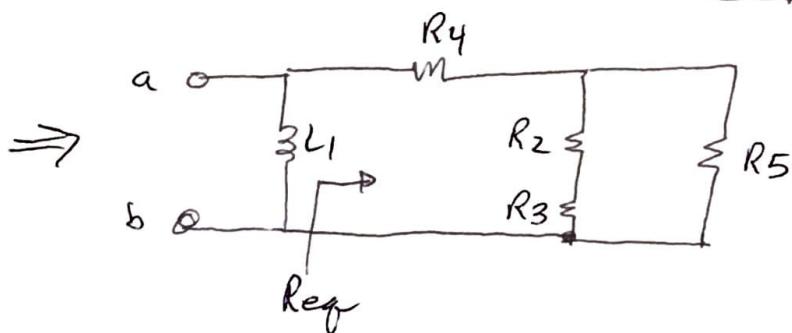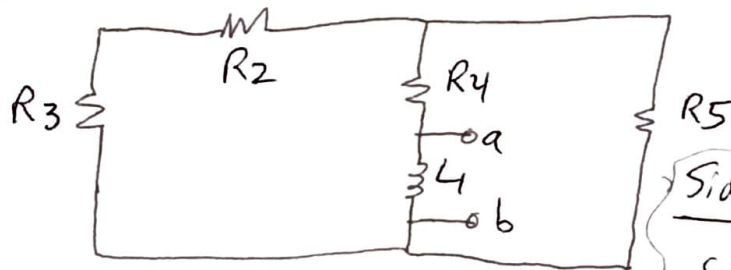

Side Note: If circuit contained dependent sources, you would need to drive terminals a & b with a test voltage or current, and find R_{eq} that way; if you needed to do this, you remove L_1 from the analysis.

$$\text{So, } R_{eq} = R_4 + [(R_2 + R_3) || R_5] = 12k\Omega$$

$$\text{and so } \tau = \frac{L_1}{R_{eq}} = \frac{20mH}{12k\Omega} \approx 1.67\mu s \quad (\text{also note that } \frac{1}{\tau} = 600k s^{-1})$$

this says s^{-1}

cont'd

So, $t_0 = 0s$ and

$$\begin{aligned} i_L(t) &= i_L(\infty) + [i_L(t_0^+) - i_L(\infty)]e^{-t/\tau} \\ &= 666.67\mu A + [-1.33mA - 666.67\mu A]e^{-600kt} \end{aligned}$$

$$\Rightarrow i_L(t) = 666.67\mu A - 2e^{-600kt} mA, t \geq 0$$

$$\begin{aligned} \text{and } V_o(t) &= V_o(\infty) + [V_o(t_0^+) - V_o(\infty)]e^{-t/\tau} \\ &= 4 + [16 - 4]e^{-600kt} \end{aligned}$$

$$\Rightarrow V_o(t) = 4V + 12e^{-600kt}V, t > 0$$