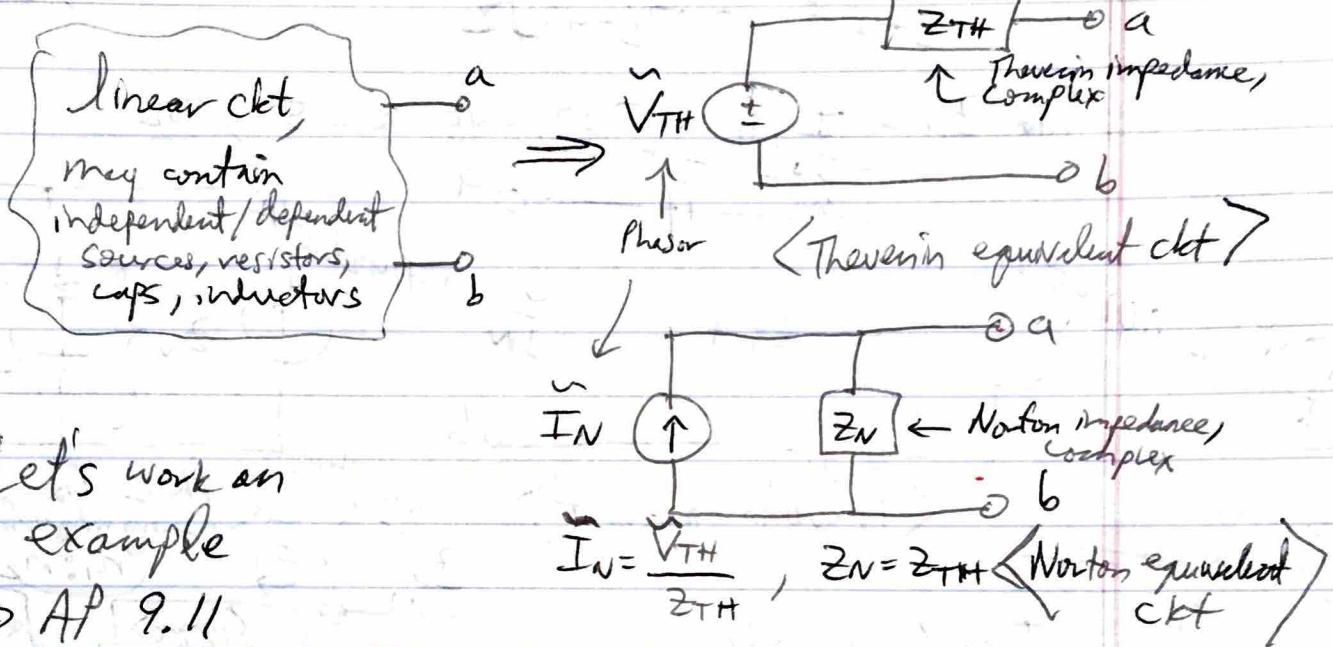


# Thevenin & Norton Equivalent Ckt Models

33


In the Phasor/Frequency Domain  $\Rightarrow$  Same Story!



Let's work on an example  
⇒ AP 9.11

Determine phasor Thevenin & Norton equivalent ckt models wrt nodes  $a$  &  $b$ :

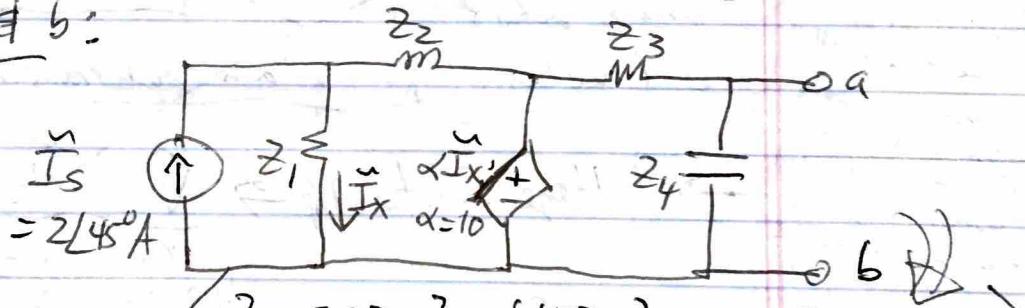
First, find  $\tilde{V}_{TH}$   
→ determine open-ckt voltage  $\tilde{V}_{out}$



$$z_1 = 20\Omega, z_2 = j10\Omega, z_3 = 10\Omega, z_4 = -j10\Omega$$

→ I'll use mesh analysis to determine  $\tilde{V}_{out} = \tilde{V}_{TH}$
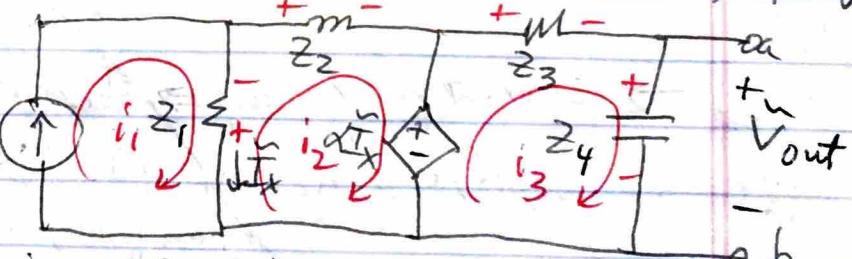
$$i_1 = \tilde{I}_S, i_2 = i_1 - i_3, \tilde{I}_S \xrightarrow{\text{solved}}$$



$$\text{KVL, mesh 2: } z_1(i_2 - i_1) + z_2 i_2 + \alpha(i_1 - i_2) = 0 \Rightarrow (1)$$

$$i_1 = \tilde{I}_S, \text{ so } (z_1 + z_2 - \alpha)i_2 = (z_1 - \alpha)\tilde{I}_S \quad (\alpha - z_1)i_1 + (z_1 + z_2 - \alpha)i_2 = 0$$

$$\text{KVL, mesh 3: } -\alpha(i_1 - i_2) + z_3 i_3 + z_4 i_3 = 0 \Rightarrow \alpha i_2 + (z_3 + z_4)i_3 = \alpha \tilde{I}_S \quad (2)$$

→ Can now solve for  $i_2$  w/ (1)  $\Rightarrow i_2 = \frac{(z_1 - \alpha)\tilde{I}_S}{z_1 + z_2 - \alpha} \rightarrow$  (cont'd)

$$i_2 = \frac{(20 - 10)(2 \angle 45^\circ)}{20 + j(0 - 10)} = \frac{10(2 \angle 45^\circ)}{10 + j10} = \frac{20 \angle 45^\circ}{14.1421 \angle 45^\circ}$$

34

$$\Rightarrow i_2 = 1.4142 \angle 0^\circ = 1.4142 = 1.4142 + j0 \Rightarrow \text{Now, use (2) to solve for } i_3:$$

$$i_3 = \frac{\alpha i_s - \alpha i_2}{z_3 + z_4} = \frac{10(2 \angle 45^\circ) - (10)(1,4142)}{10 - j10} = \frac{20 \angle 45^\circ - 14,1422}{14,1421 \angle -45^\circ}$$

$$= \frac{14,1422 + j14,1422 - 14,1422}{14,1421 \angle -45^\circ} = \frac{14,1422 \angle 90^\circ}{14,1421 \angle -45^\circ}$$

$$\approx 1 \angle 135^\circ \Rightarrow i_3 = 1 \angle 135^\circ = -0,7071 + j0,7071$$

(c) t15  
Solved.

clct is  
Solved.

Now, compute  $V_{out} = V_{TH} \Rightarrow V_{out} = Z_4 i_3 = (-j10)(1L135^\circ)$

$$\Rightarrow \tilde{V}_{out} = (10L - 90^\circ)(1L 135^\circ) = 10L 45^\circ \Rightarrow \tilde{V}_{TH} = \tilde{V}_{out} = 10L 45^\circ V \\ \approx 7.0711 + j7.0711 V$$

~~Before computing  $Z_{out} = Z_T + jX$ , more on impedance:~~  $Z = R + jX$  [S]

$\Rightarrow \text{Re}\{Z\} = R$ ,  ~~$\text{Im}\{Z\} = 0$~~   $\text{Im}\{Z\} = 0 \times \Rightarrow$  the real part of an impedance is called resistance, and the imaginary part of ~~is called~~

$\Rightarrow$  if reactance  $< 0$ , then impedance is said to be capacitive and if reactance  $> 0$ , then impedance is said to be inductive.

$\Rightarrow$  if reactance = 0, the impedance is said to be purely real or resistive  
 $\Rightarrow$  An analogy to  $G = 1/R$  in phasor domain  $\Rightarrow Y = 1/Z$  is called admittance

$\Rightarrow Y = G + jB \Rightarrow \operatorname{Re}\{Y\} = G[V]$  is called conductance &  
 $\operatorname{Im}\{Y\} = B[V]$  is called susceptance.

$\Rightarrow$  if susceptance  $> 0$ , then admittance & if susceptance  $< 0$ , then admittance is said to be capacitive is said to be inductive - if suscep

⇒ Finally, note that  $Z = X_1 + jY_1$  and  $Y = Y_2 - jX_2$  are not phasors

~~Now, compute  $Z_{out} = Z_{TH}$~~   $\Rightarrow$  deactivate independent sources  $\Rightarrow I_S$  is replaced w/ open circuit

deactivated circuit contains dependent source, so attach a test source

$Z_{out} = \frac{\tilde{V}_T}{\tilde{I}_T}$

$\tilde{V}_T = 120^\circ$  { I'll use nodal analysis. }  
 $\Rightarrow \tilde{V}_i = \alpha \tilde{I}_x$

(contd)

35

$$\Rightarrow \tilde{I}_x = \frac{\tilde{V}_i}{z_1 + z_2} = Y_x \tilde{V}_i = Y_x \alpha \tilde{I}_x \quad \text{admittance} \Rightarrow Y_x = \frac{1}{z_1 + z_2} \Rightarrow \tilde{I}_x = Y_x \alpha \tilde{I}_x$$

$$\Rightarrow \text{So, } \tilde{I}_x = 0 \text{ & } \tilde{V}_i = \alpha \tilde{I}_x = 0 \Rightarrow \text{effective ckt} \quad (\text{since } \tilde{V}_i = 0)$$

KCL @  $\tilde{V}_T$  in the effective ckt:

$$\Rightarrow \tilde{I}_T = i_1 + i_2 \quad (1) \quad \text{admittances}$$

$$\Rightarrow i_1 = Y_4 \tilde{V}_T, i_2 = Y_3 \tilde{V}_T \Rightarrow \text{Back to (1)}: \tilde{I}_T = Y_4 \tilde{V}_T + Y_3 \tilde{V}_T$$

$(= Y_{24}) \quad (= Y_{23}) \quad \Rightarrow \tilde{I}_T = (Y_4 + Y_3) \tilde{V}_T$

$$\Rightarrow Z_{\text{out}} = \frac{\tilde{V}_T}{\tilde{I}_T} = \frac{1}{Y_3 + Y_4} = \frac{1}{100mV + j100mV} = \frac{1}{141.4214m \angle 45^\circ}$$


$$= \frac{1}{141.4214m \angle 45^\circ} = 7.0711 \angle -45^\circ \Omega = 5-j5\Omega \quad (\text{ohms})$$

$$\Rightarrow [Z_{TH} = Z_{\text{out}} = 7.0711 \angle -45^\circ = 5-j5\Omega] \leftarrow \text{capacitive why? Because } \text{Im}\{Z_{TH}\} < 0$$


$$\text{Now, Compute } \tilde{I}_N = \frac{\tilde{V}_{TH}}{Z_{TH}} = \frac{10 \angle 45^\circ V}{7.07 \angle -45^\circ \Omega} = 1.4142 \angle 90^\circ A \neq$$

$$Z_N = Z_{TH} = 7.07 \angle -45^\circ = 5-j5\Omega \Rightarrow \text{we can now draw}$$

the models:

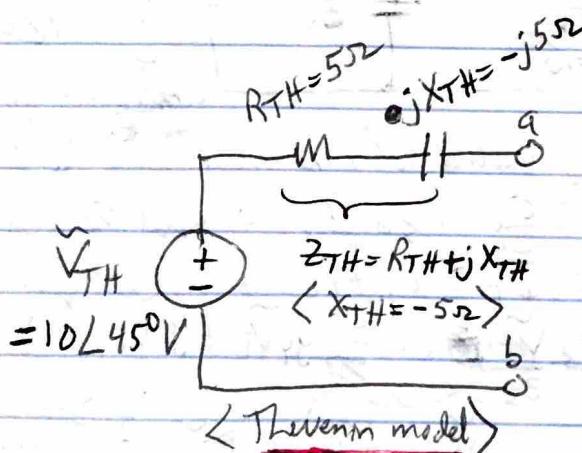

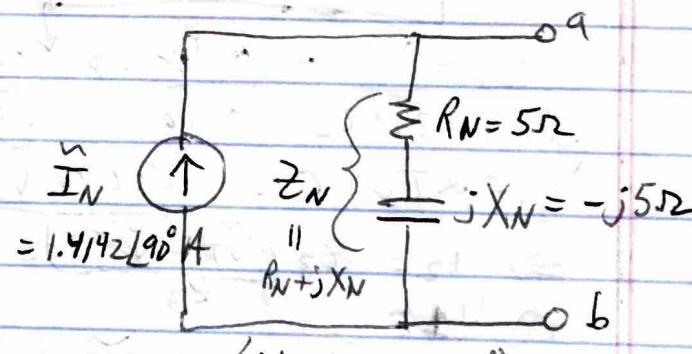Note that  $\text{Im}\{Z_{TH}\} < 0$ ,  
so  $Z_{TH}$  is capacitive



Note that  $\text{Im}\{Z_N\} = X_N = -5\Omega < 0$ ,  
so  $Z_N$  is capacitive

# Complex Power

(See Sections 10.4 & 10.5 for more details)

37.1

In the phasor/frequency domain, the complex power  $S$  is defined as

$$S = P + jQ,$$

where  $P$  is the real power &  $Q$  is the reactive power; units?

real power  
is sometimes  
referred to  
as average  
power

$S \Rightarrow$  complex power  $\Rightarrow$  units of volt-amps [VA]  
 $P \Rightarrow$  <sup>average of</sup> real power  $\Rightarrow$  units of watts [W]  $\Leftrightarrow$  if  $P < 0 \Rightarrow$  avg. real power is being delivered  
 $Q \Rightarrow$  reactive power  $\Rightarrow$  units of volt-amps reactive [VAR]  $\Leftrightarrow$  if  $Q < 0 \Rightarrow$  reactive power is being delivered  
 Note that apparent power is  $|S|$ :  $|S| = \sqrt{P^2 + Q^2}$  magnitude of  $S$   $\Leftrightarrow$  else if  $P > 0 \Rightarrow$  dissipated/absorbed  
 else if  $Q > 0 \Rightarrow$  dissipated/absorbed

How to compute  $S$ ?

#1  $S = \frac{1}{2} \tilde{V} \tilde{I}^*$  ( $= \frac{\tilde{V}}{\sqrt{2}} \frac{\tilde{I}^*}{\sqrt{2}} = \tilde{V}_{rms} \tilde{I}_{rms}^*$ )

#2  $S = \frac{1}{2} Z |\tilde{I}|^2$  ( $= Z \frac{\tilde{I}}{\sqrt{2}} \frac{\tilde{I}^*}{\sqrt{2}} = \underbrace{Z \tilde{I}_{rms} \tilde{I}_{rms}^*}_{\tilde{V}_{rms}} = Z |\tilde{I}_{rms}|^2$ )

#3  $S = \frac{1}{2} \frac{|\tilde{V}|^2}{Z^*}$  ( $= \frac{\tilde{V}}{\sqrt{2}} \left( \frac{\tilde{V}}{\sqrt{2}} \right)^* = \tilde{V}_{rms} \underbrace{\left( \frac{\tilde{V}_{rms}}{Z} \right)^*}_{\tilde{I}_{rms}^*} = \frac{1}{2} \frac{\tilde{V}_{rms}^2}{Z^*}$ )


Let's work through an example to show how to do power checks in the phasor/frequency domain:

Example 10.7

Given:  $\tilde{V}_s = 150 \angle 0^\circ V$ ,  $\tilde{V}_1 = 78 - j104 V$ ,

$\tilde{V}_2 = 72 + j104 V$ ,  $\tilde{V}_3 = 150 - j130 V$ ,

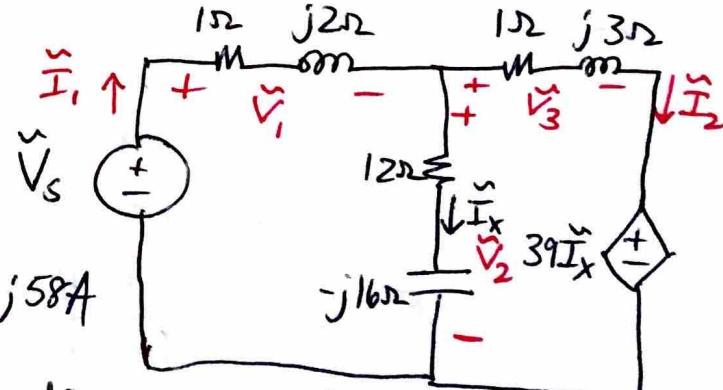$\tilde{I}_1 = -26 - j52 A$ ,  $\tilde{I}_x = -2 + j6 A$ ,  $\tilde{I}_2 = -24 - j58 A$



(a) Calculate the total average & reactive power delivered to each impedance.

(cont'd) ↗

(example, cont'd)

(a) The complex power delivered to the  $1+j2\Omega$  impedance is 37.2

$$\rightarrow S_1 = \frac{1}{2} \tilde{V}_1 \tilde{I}_1^* = \frac{1}{2} \underbrace{(78-j104)}_{1\Omega \text{ resistor}} \underbrace{(-26+j52)}_{j2\Omega \text{ inductor}} = 1690 + j3380 \text{ VA}$$

*Note that passive sign convention is being adhered to here*

$\Rightarrow$  Thus the impedance is dissipating/absorbing an average/real power of  $P_1 = \underline{1690 \text{ W}}$  & a reactive power of  $\underline{j3380 \text{ VAR}}$

(the sign of  $\text{Im}\{S_1\} = Q_1$  is ~~positive~~, so the  $j3380 \text{ VAR}$  term is being dissipated/absorbed by the  $j2\Omega$  inductor)

$$\rightarrow S_2 = \frac{1}{2} \tilde{V}_2 \tilde{I}_x^* = \frac{1}{2} \underbrace{(72+j104)}_{1\Omega \text{ resistor}} \underbrace{(-2-j6)}_{j16\Omega \text{ capacitor}} = 240 - j320 \text{ VA}$$

*inductors always have  $Q > 0$*

$\Rightarrow$  Therefore the impedance in the vertical branch is dissipating/absorbing an average/real power of  $P_2 = \underline{240 \text{ W}}$  & is delivering/supplying  $\underline{-j320 \text{ VAR}}$

*$-j16\Omega \text{ cap}$*

(the sign of  $\text{Im}\{S_2\} = Q_2$  is negative, so the  $-j320 \text{ VAR}$  term is being delivered/supplied by the  $-j16\Omega$  capacitor)

$$\rightarrow S_3 = \frac{1}{2} \tilde{V}_3 \tilde{I}_2^* = \frac{1}{2} \underbrace{(150-j130)}_{1\Omega \text{ resistor}} \underbrace{(-24+j58)}_{j3\Omega \text{ inductor}} = 1970 + j5910 \text{ VA}$$

*Caps always have  $Q < 0$*

$\Rightarrow$  This impedance is dissipating/absorbing  $\underline{1970 \text{ W} = 1.97 \text{ kW}}$

of average/real power & dissipating/absorbing a reactive power of  $\underline{5910 \text{ VAR} = 5.91 \text{ kVAR}}$

*$j3\Omega \text{ inductor}$*

(cont'd)


(example, cont'd)

37.3

(b) Determine the complex power terms for the sources:

independent source,  $\tilde{V}_S$

$$S_S = ? \Rightarrow$$

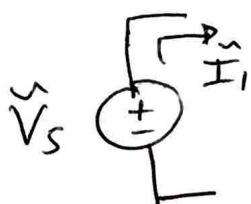

here, to be consistent with passive sign convention, we'll compute  $S_S$  as

$$S_S = -\frac{1}{2} \tilde{V}_S \tilde{I}_1^*$$


$$\Rightarrow S_S = -\frac{1}{2} \tilde{V}_S \tilde{I}_1^* = -\frac{1}{2} \underbrace{(150)}_{\tilde{V}_S} \underbrace{(-26+j52)}_{\tilde{I}_1^*} = 1950 - j3900 \text{ VA}$$
$$= P_S + j Q_S$$

$\Rightarrow \operatorname{Re}\{S_S\} = P_S > 0$ , so  $\tilde{V}_S$  is absorbing ("dissipating")  $1950 \text{ W} = 1.95 \text{ kW}$

of real/avg. power, & since  $\operatorname{Im}\{S_S\} = Q_S < 0$ ,  $\tilde{V}_S$  is delivering/supplying ~~absorbing/dissipating~~

$3900 \text{ VAR} = 3.9 \text{ kVAR}$  of reactive power.

dependent source,  $39\tilde{I}_x$

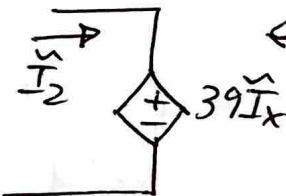

here, to be consistent with passive sign convention,  $S_x$  is computed as

$$S_x = \frac{1}{2} 39\tilde{I}_x \tilde{I}_2^*$$

$$\Rightarrow S_x = \frac{1}{2} (39\tilde{I}_x) \tilde{I}_2^* = \frac{1}{2} \underbrace{(39)}_{39\tilde{I}_x} \underbrace{(-2+j6)(-24+j58)}_{\tilde{I}_2^*}$$

$$\Rightarrow S_x = -5850 - j5070 \text{ VA} = P_x + j Q_x$$

$\Rightarrow \operatorname{Re}\{S_x\} = P_x < 0$ , so  $39\tilde{I}_x$  source is delivering/supplying

an average/real power of  $5850 \text{ W} = 5.85 \text{ kW}$ , & since

$\operatorname{Im}\{S_x\} = Q_x < 0$ , the  $39\tilde{I}_x$  source is delivering/supplying a reactive power of  $5070 \text{ VAR} = 5.07 \text{ kVAR}$ .

(c) Verify that the average/real power delivered equals the average/real power dissipated, and the magnetizing reactive power delivered equals the magnetizing reactive power absorbed/"dissipated"

(cont'd)  $\rightarrow$

(example, cont'd)

(c) → The total average/real power being dissipated/absorbed is:

$$P_{dis} = P_1 + P_2 + P_3 + P_S = 5850W = 5.85kW$$

37.4

→ The total average/real power being delivered is:

$$P_{del} = |P_{\times}| = 5850W = 5.85kW$$

⇒ Thus,  $P_{dis} = P_{del} = 5.85kW$  ✓

⇒ For phasor ckt's, we are not done with a power check until we also verify that  $Q_{dis} = Q_{del}$  ↗

→ Magnetizing reactive power is being absorbed/dissipated by the two horizontal branches in the ckt:  
inductors in the

$$Q_{dis} = Q_1 + Q_3 = 9290 \text{ VAR} = 9.29 \text{ kVAR}$$

→ Magnetizing reactive power is being delivered by the independent voltage source, the capacitor, & the dependent voltage source?


$$Q_{del} = |Q_S| + |Q_2| + |Q_X| = 9290 \text{ VAR} = 9.29 \text{ kVAR}$$

⇒ Thus  $Q_{dis} = Q_{del} = 9.29 \text{ kVAR}$  ✓

⇒ The power check is now complete. ✓

→ How to accomplish max power transfer in phasor domain? Consider 2 cases:

$$P_{RL} = \frac{1}{2} R_L |I_L|^2 = \left(\frac{1}{2} R_L\right) \frac{|V_{TH}|^2}{(R_{TH}+R_L)^2 + (X_{TH}+X_L)^2}$$

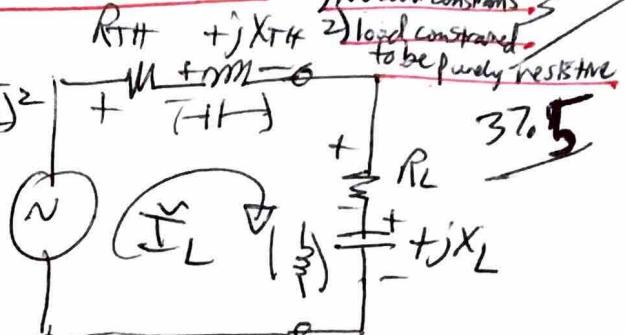

$$\tilde{I}_L = ? \quad \tilde{I}_L = \frac{\tilde{V}_{TH}}{(R_{TH}+jX_{TH})+jX_L}$$

$$\Rightarrow \tilde{I}_L = \frac{\tilde{V}_{TH}}{(R_{TH}+R_L)+j(X_{TH}+X_L)}$$

$$|\tilde{I}_L| = \frac{|\tilde{V}_{TH}|}{\sqrt{(R_{TH}+R_L)^2 + (X_{TH}+X_L)^2}} \Rightarrow |\tilde{I}_L|^2 = \frac{|\tilde{V}_{TH}|^2}{(R_{TH}+R_L)^2 + (X_{TH}+X_L)^2}$$

(i)

Want to maximize  $P_{RL}$  w/ no constraints on the load:  $\Rightarrow$  two variables (not just one as before)

$$\Rightarrow \frac{\partial P_{RL}}{\partial R_L} \stackrel{(i)}{=} 0 \text{ and } \frac{\partial P_{RL}}{\partial X_L} \stackrel{(ii)}{=} 0 \Rightarrow \text{To maximize } P_{RL} \text{ due to the } X_L \text{ term,}$$

$$\Rightarrow \text{so, to get } \frac{\partial P_{RL}}{\partial X_L} = 0, \text{ set } X_L \stackrel{(iii)}{=} -X_{TH} \quad \text{ie, if } X_{TH} < 0 \text{ (i.e., capacitive), set } X_L \text{ to be inductive.}$$

\* What about (i),  $\frac{\partial P_{RL}}{\partial R_L} = 0$ ?  $\Leftarrow$  we'll now assume that  $X_L = -X_{TH}$ :

$$\Rightarrow \text{so, } P_{RL} = \frac{1}{2} R_L \left( \frac{|\tilde{V}_{TH}|^2}{(R_{TH}+R_L)^2} \right) \quad \text{or this is essentially the same form of } P_{RL} \text{ that we had before...}$$

$\Rightarrow$  we already know that  $P_{RL}$  above is maximized when  $R_L \stackrel{(2)}{=} R_{TH}$

$$\$ P_{RL,\max} = \frac{1}{2} R_{TH} \left| \tilde{V}_{TH} \right|^2 = \frac{1}{2} R_{TH} / \left| \tilde{V}_{TH} \right|^2$$

$$\Rightarrow P_{RL,\max} = \frac{|\tilde{V}_{TH}|^2}{8R_{TH}} \quad \begin{array}{l} \text{no constraints max} \\ \text{are power delivered to load} \end{array}$$

What about the scenario where we have a constraint on the load, e.g.,


of load is purely resistive?

$$\text{If we use } \tilde{V}_{TH,\text{rms}} = \frac{1}{2} \tilde{V}_{TH}, \text{ then } P_{RL,\max} = \frac{|\tilde{V}_{TH,\text{rms}}|^2}{4R_{TH}}$$

II Want to maximize  $P_{RL}$  subject to the constraint that the load is purely resistive.

37.6

$$\tilde{I}_L = \frac{\tilde{V}_{TH}}{R_{TH} + R_L + jX_{TH}}, P_{RL} = \frac{1}{2} R_L |\tilde{I}_L|^2$$

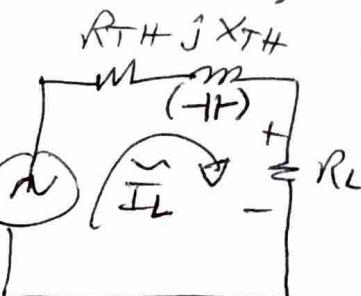

$$\Rightarrow P_{RL} = \left( \frac{1}{2} R_L \right) \frac{|\tilde{V}_{TH}|^2}{(R_{TH} + R_L)^2 + X_{TH}^2} \quad \text{to maximize, set } \frac{dP_{RL}}{dR_L} = 0$$

$$\frac{dP_{RL}}{dR_L} = \left( \frac{1}{2} |\tilde{V}_{TH}|^2 \right) \left\{ \left[ (R_{TH} + R_L)^2 + X_{TH}^2 \right] \frac{d}{dR_L} - R_L \left( \frac{d}{dR_L} [(R_{TH} + R_L)^2 + X_{TH}^2] \right) \right\} \\ \left[ (R_{TH} + R_L)^2 + X_{TH}^2 \right]^2$$

$$\Rightarrow \frac{dP_{RL}}{dR_L} = 0 \text{ when numerator } \left\{ \frac{dP_{RL}}{dR_L} \right\} = 0 \Rightarrow \frac{d}{dR_L} [(R_{TH} + R_L)^2 + X_{TH}^2] = \dots$$

$$\dots = \frac{d}{dR_L} [R_{TH}^2 + 2R_{TH}R_L + R_L^2 + X_{TH}^2] = 2R_L + 2R_{TH} \Rightarrow \text{so, the num } \left\{ \frac{dP_{RL}}{dR_L} \right\} \text{ is equal to zero when } (R_{TH} + R_L)^2 + X_{TH}^2 - R_L(2R_L + 2R_{TH}) = 0$$

$$\Rightarrow R_{TH}^2 + 2R_{TH}R_L + R_L^2 + X_{TH}^2 = 2R_L^2 + 2R_{TH}R_L \Rightarrow 2R_L^2 - R_L^2 = R_{TH}^2 + X_{TH}^2$$

$$\Rightarrow R_L = \pm \sqrt{R_{TH}^2 + X_{TH}^2} \quad \text{as } R_L = -\sqrt{R_{TH}^2 + X_{TH}^2} \text{ is infeasible since } R_L \text{ cannot be negative, so}$$

$$R_L = \sqrt{R_{TH}^2 + X_{TH}^2} = |\tilde{V}_{TH}| \quad (3)$$

Yields  $P_{RL, \max}$  when the load is constrained to be purely resistive

$$\& P_{RL, \max} = \frac{1}{2} R_L |\tilde{I}_L|^2 \quad R_L = \sqrt{R_{TH}^2 + X_{TH}^2}$$


$$\frac{1}{2} \sqrt{R_{TH}^2 + X_{TH}^2} / |\tilde{V}_{TH}|^2 = P_{RL, \max}$$

$\checkmark$  purely real constraint max avg power delivered to load

$\Rightarrow$  if we use  $\tilde{V}_{TH, \text{rms}} = \sqrt{2} \tilde{V}_{TH}$ ,


$$\text{then } P_{RL, \max} = \frac{\sqrt{R_{TH}^2 + X_{TH}^2}}{(R_{TH} + \sqrt{R_{TH}^2 + X_{TH}^2})^2 + X_{TH}^2} |\tilde{V}_{TH, \text{rms}}|^2$$

In-class discussion  
Sep. 2022

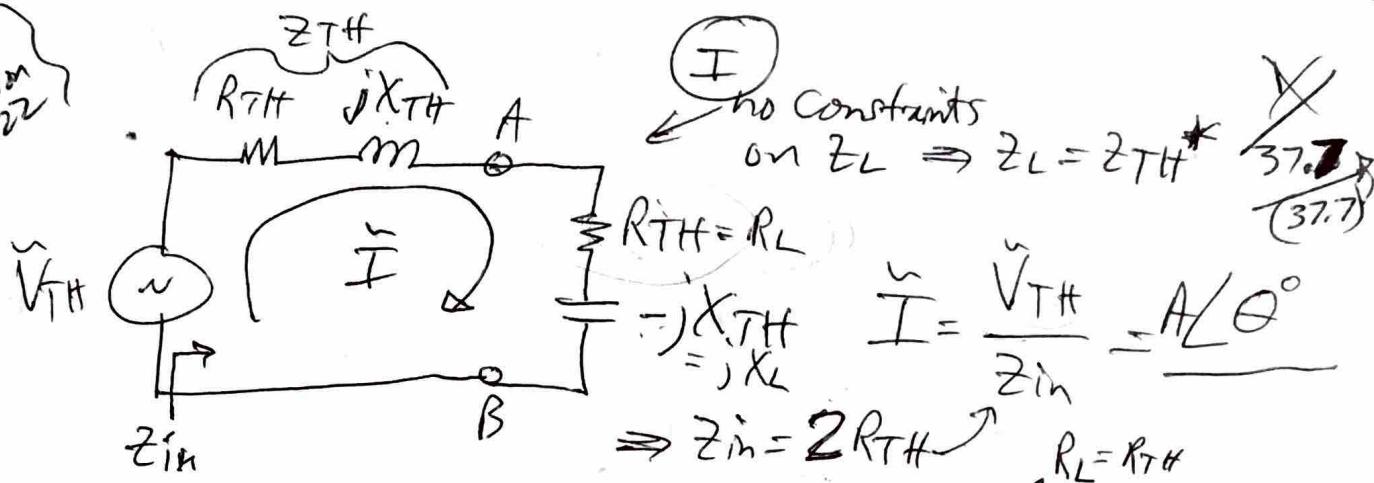

$\Rightarrow$  avg/real power dissipated by  $Z_L = ?$   $P_{RL} = \frac{1}{2} |Z| \tilde{I}^2 = \frac{1}{2} R_{TH} A^2$

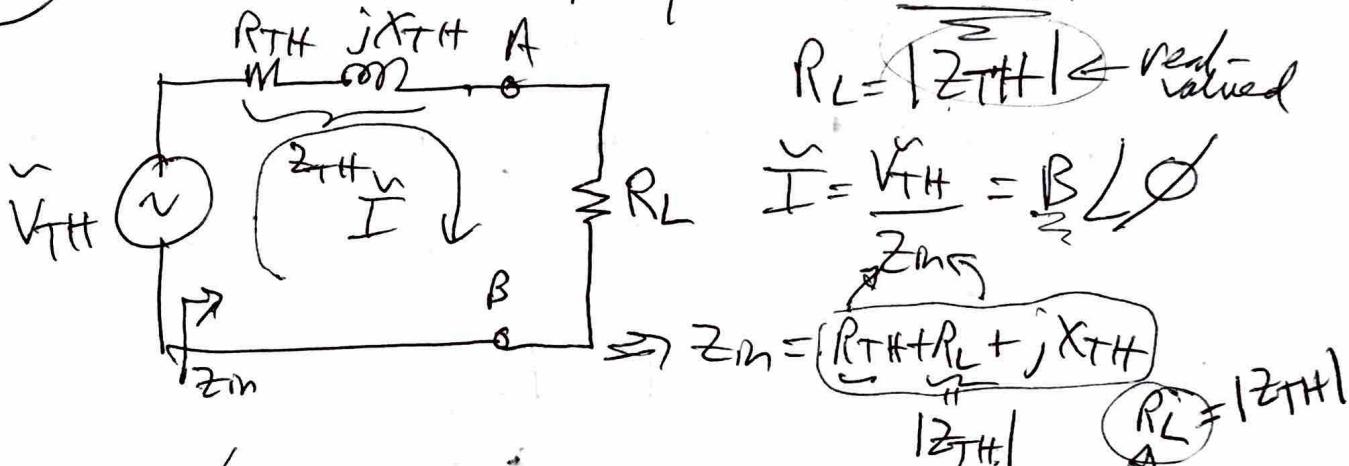(II)  $Z_L$  constrained to be purely real  $\Rightarrow Z_L = R_L$ :




$\Rightarrow$  avg/real power dissipated by  $R_L = ?$   $P_{RL} = \frac{1}{2} Z \tilde{I}^2$

Note that  $\frac{1}{2} R_{TH} A^2$  should be  $> \frac{1}{2} |Z_{TH}| B^2$

$$\Rightarrow P_{RL} = \frac{1}{2} |Z_{TH}| B^2$$

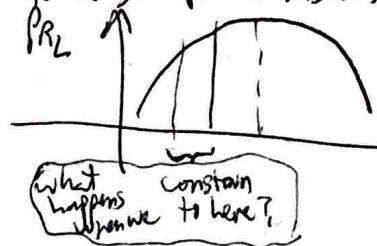Why? Because constraining a maximization problem leads to a suboptimal result, in general.



More hints on back!  $\rightarrow$

Prob 7

v for parts (c) & (d)

37.8

Wrong answers ~~formats~~ that you want to avoid:

Note: These  
are not the  
correct  
answers  
for part(a)!!

Suppose that you get  $\tilde{V}_{TH} = 5 \angle 52^\circ V$  &  $\tilde{Z}_{TH} = 4.2 + j 2.3 \Omega$   
 $\cong 4.79 \angle 28.71^\circ \Omega$   
for part (a); now, for part (b), what kind of mistakes can we make?  
(no constraints!)

Part(b) Find  $Z_L$  to maximize avg. power delivery to load  $\Rightarrow$  set  $Z_L = Z_{TH}$

$$\text{So, } Z_L = Z_{TH}^* = \{4.2 + j 2.3\}^* = 4.2 - j 2.3 \Omega$$

WRONG!  $\Rightarrow$  not  $Z_L = Z_{TH} = 4.2 + j 2.3$ !  $\Leftarrow$  WRONG!

Part(c) Find  $R_L$  (real valued constraint!) to maximize avg. power delivery to load:

$$\text{WRONG!} \Rightarrow R_L = \text{Re}\{\tilde{Z}_{TH}\} = 4.2 \Omega \text{ WRONG!}$$

$$\text{Correct approach} \Rightarrow R_L = |\tilde{Z}_{TH}| = |4.2 + j 2.3| = \sqrt{4.2^2 + 2.3^2} \cong 4.79 \Omega$$
  
$$= |4.79 \angle 28.71^\circ| \left( \frac{\sqrt{17.64 + 5.29}}{\sqrt{22.93}} \right) \cancel{\Omega}$$

Part(d)

P<sub>max</sub> for parts (b) & (c)?

Correct way!

WRONG!

$$P_{max} = \frac{V_{TH}^2}{4R_L} = \frac{5^2}{4 \cdot 4.2} \cancel{W}$$

WRONG!

Correct way?  $\Rightarrow$  use procedure covered on previous page!

Also, wrong!

No discussion!

WRONG!

"


Correct way?  $\Rightarrow$  discuss  $\Rightarrow P_{max, part(b)} \text{ should be} > P_{max, part(c)}$

~~Summary~~
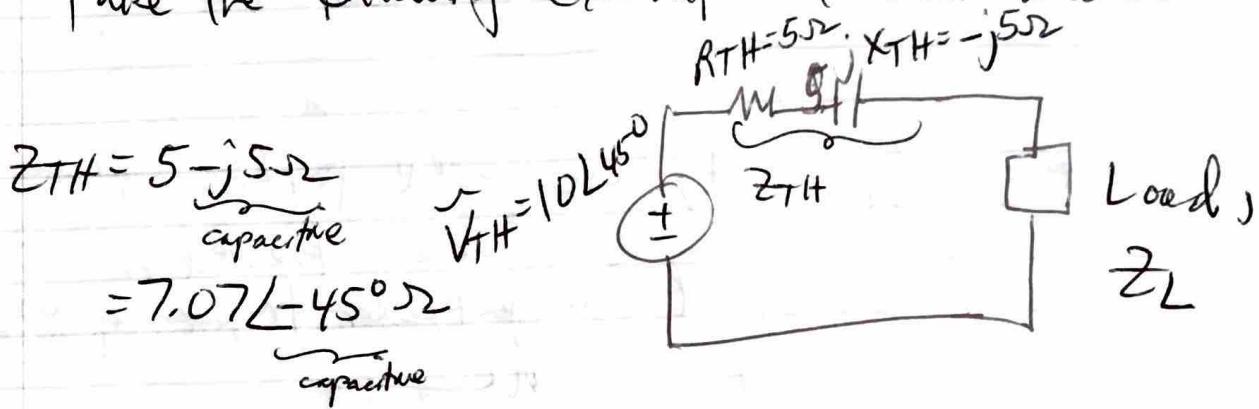
## Max Power delivery in the phasor domain:

38

Take the following example Thevenin model :



(I) → Suppose we want to determine  $Z_L$  for max real/average power transfer to the load.

⇒ If there are no constraints on  $Z_L$ ,

then set  $\underline{Z_L = Z_{TH}}$

i.e., if  $Z_{TH} = R_{TH} + jX_{TH}$  is capacitive w.r.t  $X_{TH} < 0$ , then attach load  $Z_L = R_{TH} - jX_{TH}$  inductive & vice versa

⇒ In this example, we'd set  $\underline{Z_L = Z_{TH}}$

$$\Rightarrow Z_L = (5 - j5)^* = 5 + j5\Omega \Rightarrow Z_L = 5 + j5\Omega$$

for max <sup>real</sup> power transfer, no  $Z_L$  constraints.

(II) → Now, suppose we want to maximize power transfer to  $Z_L$  under the constraint that  $Z_L$  be purely real. How to design  $Z_L$  in this case?

⇒ Here, we'd set  $\underline{Z_L = |Z_{TH}|}$

i.e., attach load  $Z_L$  equal to the magnitude of  $Z_{TH} = \sqrt{R_{TH}^2 + X_{TH}^2}$

⇒ In this case,  $Z_L = R_L = |5 - j5| = |7.07 e^{-j45^\circ}|$

See chpt 10  
for more on  
phasor-domain  
power calculations

$$\Rightarrow Z_L = R_L = 7.07\Omega \text{ for max power transfer under the constraint that } Z_L \text{ be purely real}$$


**\* Purely-real Impedance**

Dvedo  
36-37

Example:

$$R = 500\Omega, L = 50\text{mH} \quad \leftarrow \text{don't use these for part(a)!}$$

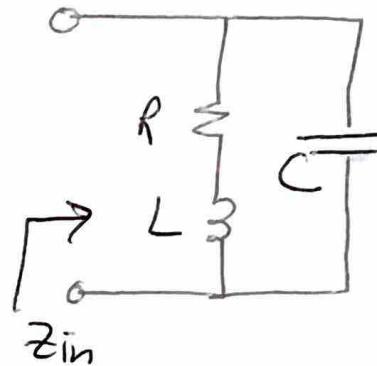(a) Derive an expression for C such that the impedance  $Z_{in}$  is purely real (or purely resistive) at a frequency of  $f = 1\text{kHz}$ .




- (b) Evaluate expression of part(a) for given R, L values, & determine  $Z_{in}$ .  
(c) Sketch  $Z_{in}$  vs. f & highlight the result at  $f = 1\text{kHz}$  on sketch.

Sol<sup>ln</sup>  
(a) Consider phasor-transformed circuit  $\rightarrow$

$$Z_{in} = (Z_R + Z_L) // Z_C, \quad Z_R = R, \quad Z_L = j\omega L, \quad Z_C = \frac{1}{j\omega C}$$
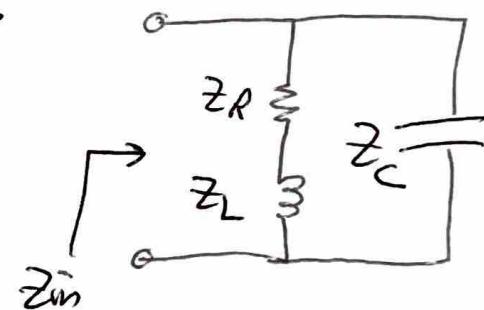
$$\Rightarrow Z_R + Z_L = R + j\omega L \neq 0$$



$$Z_{in} = (Z_R + Z_L) // Z_C = \frac{(Z_R + Z_L)(Z_C)}{Z_R + Z_L + Z_C} = \frac{\left( (R + j\omega L) \left( \frac{1}{j\omega C} \right) \right) (j\omega C)}{\left( R + j\omega L + \frac{1}{j\omega C} \right) (j\omega C)}$$

$$= \frac{R + j\omega L}{1 + \underbrace{(j\omega L)(j\omega C)}_{= -\omega^2 LC} + j\omega RC} = \frac{R + j\omega L}{(1 - \omega^2 LC) + j\omega RC} \quad \leftarrow \text{we want } Z_{in} \text{ purely real; let's multiply by complex conjugate of denom. to get all j terms into numerator.}$$

$$\Rightarrow Z_{in} = \frac{(R + j\omega L) (1 - \omega^2 LC - j\omega RC)}{(1 - \omega^2 LC + j\omega RC) (1 - \omega^2 LC - j\omega RC)} = \frac{R(1 - \omega^2 LC) + \omega^2 RLC - j\omega RC^2 + j\omega L(1 - \omega^2 LC)}{(1 - \omega^2 LC)^2 + (\omega RC)^2}$$

$$\Rightarrow Z_{in} = \frac{R - \cancel{\omega^2 RLC} + \omega^2 RLC + j[WL - \cancel{\omega R^2 C} - \omega^3 L^2 C]}{(1 - \omega^2 LC)^2 + (\omega RC)^2}$$

$$\Rightarrow Z_{in} = \frac{R + j\omega [L - R^2 C - \omega^2 L^2 C]}{(1 - \omega^2 LC)^2 + (\omega RC)^2} \Rightarrow$$

we want  $\text{Im}\{Z_{in}\} = 0$ , so set

$$\text{Im}\{Z_{in}\} = \frac{\omega [L - R^2 C - \omega^2 L^2 C]}{(1 - \omega^2 LC)^2 + (\omega RC)^2} = 0 \quad (\text{cont'd}) \rightarrow$$

(a) (cont'd)  $\text{Im}\{\mathbf{z}_{in}\}$  will equal zero if  $\omega [L - R^2 C - \omega^2 L^2 C]$  equals zero.

② redo  
36-37

$$\Rightarrow \omega [L - R^2 C - \omega^2 L^2 C] = 0 \Rightarrow L = C [R^2 + \omega^2 L^2]$$

$$\Rightarrow C = \frac{L}{R^2 + \omega^2 L^2} \quad \leftarrow \text{this equation gives the value of } C \text{ needed to make } \mathbf{z}_{in} \text{ purely resistive (i.e., } \text{Im}\{\mathbf{z}_{in}\} = 0\}$$



$$(b) C = \frac{L}{R^2 + \omega^2 L^2} = \frac{50\text{m}}{(500)^2 + [(2\pi)(1\text{k})]^2 (50\text{m})^2} \Rightarrow C = 143.39\text{nF}$$

$$\begin{aligned} \mathbf{z}_{in} &= R + j\omega [L - R^2 C - \cancel{\omega^2 L^2 C}] \\ &= \frac{R}{(1 - \omega^2 LC)^2 + (\omega RC)^2} \\ &= \frac{500}{[1 - (2\pi 1\text{k})^2 (50\text{m}) (143.39\text{n})]^2 + [(2\pi 1\text{k})(500) (143.39\text{n})]^2} \end{aligned}$$

$$\Rightarrow \mathbf{z}_{in} = 697.39\Omega \quad \leftarrow \text{Note that (1) } \mathbf{z}_{in} \text{ is purely resistive } (\text{Im}\{\mathbf{z}_{in}\} = 0) @ 1\text{kHz} \text{ & (2) } \mathbf{z}_{in} > R = 500\Omega @ f = 1\text{kHz}.$$

(c) Sketch  $\mathbf{z}_{in}$  vs. frequency  $\leftarrow \mathbf{z}_{in}$  is complex, in general, so plot  $|\mathbf{z}_{in}|$  vs.  $f$  &

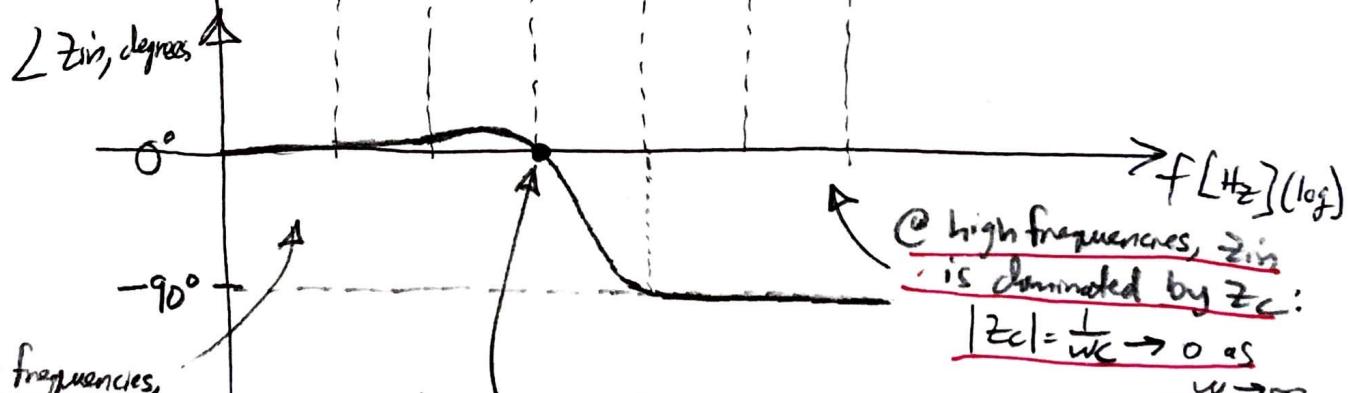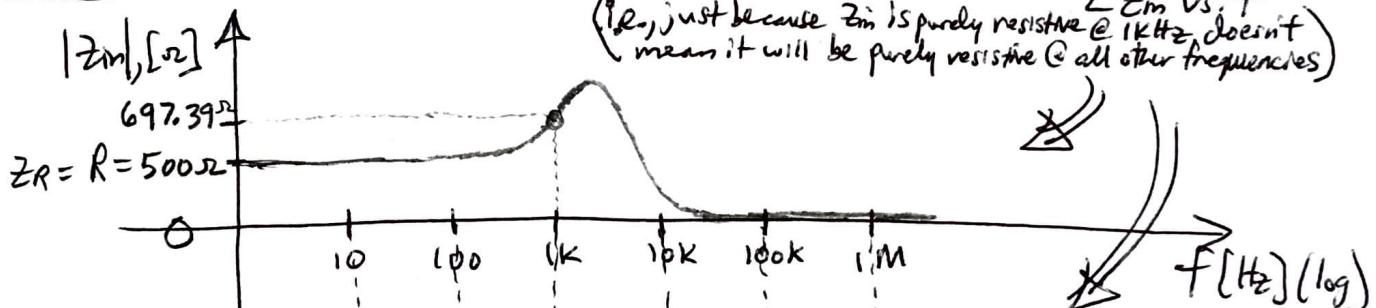(i.e., just because  $\mathbf{z}_{in}$  is purely resistive @ 1kHz doesn't mean it will be purely resistive @ all other frequencies)



@ low frequencies,  $\mathbf{z}_{in}$  is dominated by  $Z_R$ ;  $|Z_L|$  is small &  $|Z_C|$  is large compared to  $Z_R$ .

$\angle z_{in} = 0^\circ @ f = 1\text{kHz} \Rightarrow \mathbf{z}_{in} \text{ is purely real}$

$@ \text{high frequencies, } \mathbf{z}_{in} \text{ is dominated by } Z_C: |Z_C| = \frac{1}{\omega C} \rightarrow 0 \text{ as } \omega \rightarrow \infty$

$\text{Im}\{\mathbf{z}_{in}\} = 0 @ f = 1\text{kHz}$